

WIRELESS MICROPHONE

Audio in the ISM band

Ton Giesberts

When the ISM frequency band was made available in Europe for audio applications, Circuit Design, a manufacturer of professional RF modules, decided to develop suitable high-quality transmitters and receivers with a wide dynamic range: these are ideal for use in wireless microphones.



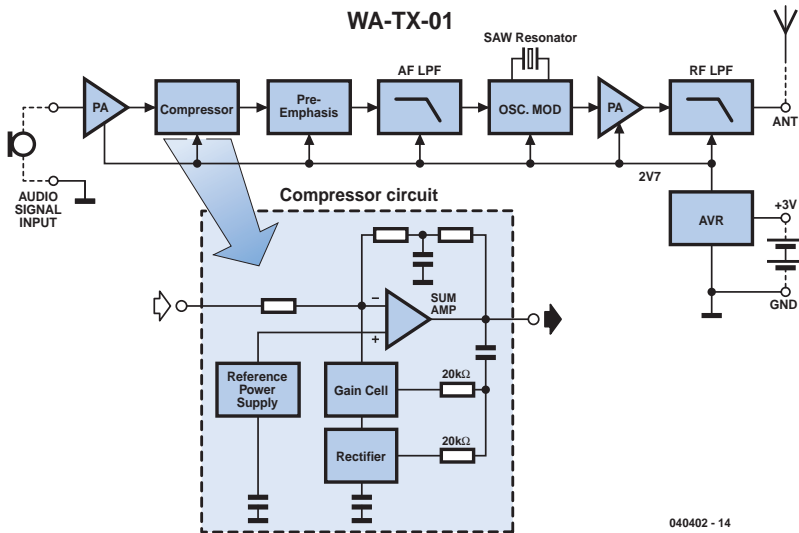


Figure 2. Block diagram of the transmitter module...

Compressor

The audio signal from the buffer stage is compressed using a ratio of 2:1. The compressor consists of a reference generator, a full-wave rectifier and a summing amplifier. The reference generator provides a bias voltage and a constant current to the other parts of the circuit.

The full-wave rectifier circuit rectifies the incoming signal with the aid of an external capacitor. The output current of the rectifier controls the gain cell amplifier. The time constant of the control loop is set, in part, using an external filter capacitor and an internal 10 kΩ resistor. The summing amplifier adds the incoming signal and the signal

from the gain cell amplifier together. The summing amplifier used in the compressor needs different properties from the one used in the expander, and so different components are used in the transmitter and in the receiver.

Pre-emphasis

To reduce noise at the upper end of the audio frequency range, which is a particular problem when using frequency modulation, this circuit boosts higher frequencies using a time constant of 50 μs.

AF low-pass filter (AF LPF)

This circuit limits the bandwidth of the audio signal in order to ensure that

interference to adjacent channels is kept within the permitted limits.

Oscillator and modulator

In order to operate directly in the 800 MHz band, a crystal-based SAW (surface acoustic wave) filter resonator with good temperature stability is used as the oscillating element. Frequency modulation is achieved using a varicap diode that forms part of the oscillator circuit.

RF power amplifier (PA)

This circuit steps the RF output of the oscillator up to the transmit power of about 5 mW.

RF low-pass filter (RF LPF)

This circuit attenuates the second and higher harmonics of the transmitted signal and provides antenna impedance matching.

Voltage regulator (AVR)

This circuit provides a stable 2.7 V supply for the whole circuit. It operates from a battery supply of between 3 V and 9 V.

The receiver

The block diagram of the WA-RX-01 receiver module shown in Figure 3 is practically the mirror image of the transmitter, using similar components.

RF band-pass filter (SAW)

The 800 MHz frequency band used in this wireless audio system is extracted using this filter. A high-selectivity SAW

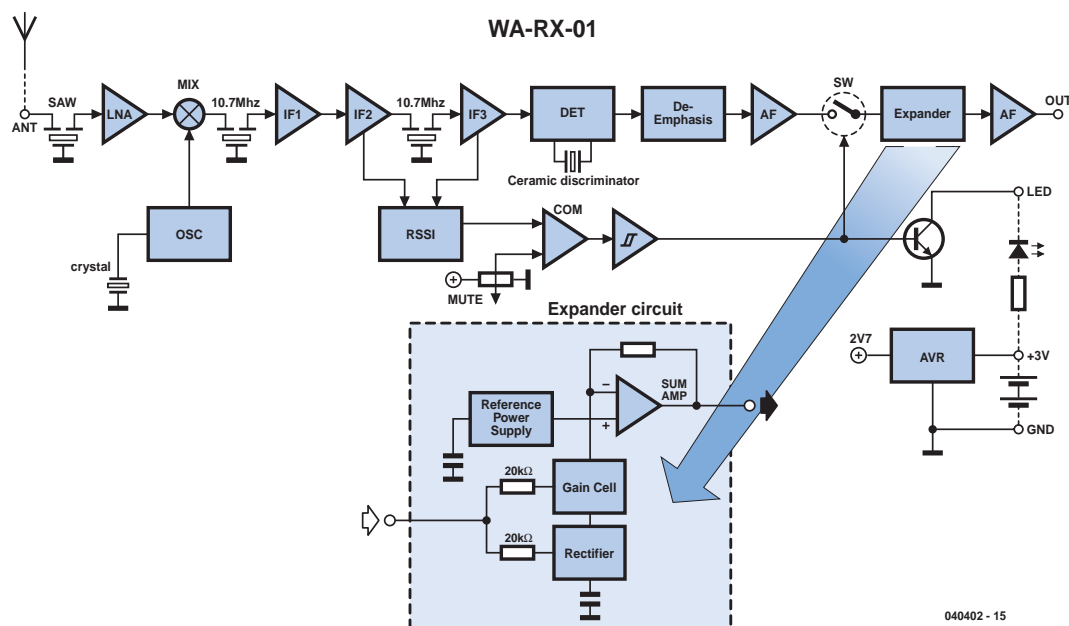


Figure 3. ... and of the receiver module.

filter is used to ensure that frequencies outside the band are eliminated.

Oscillator (OSC)

A quartz crystal oscillator is used to mix the incoming signal down to an intermediate frequency of 10.7 MHz.

RF amplifier (LNA)

A low-noise amplifier is used to amplify the 800 MHz frequency band by 10 dB.

Mixer (MIX)

This circuit creates an intermediate frequency of 10.7 MHz, produced by mixing the amplified received signal in the 800 MHz band with the output of the oscillator.

IF amplifier (IF1 to IF3)

These provide a total gain of 100 dB, the final stage acting as a limiter. Before and after the amplifier chain, 10.7 MHz ceramic filters are fitted to provide selectivity.

FM detector (DET)

This circuit demodulates the frequency-modulated IF signal.

RSSI detector (RSSI)

Signals from the middle of the IF amplifier chain are rectified producing a DC voltage proportional to the signal strength.

Muting comparator (COM)

The RSSI signal is compared to a preset voltage which can be adjusted using a potentiometer. If the level at

the antenna input falls to 17 dB μ V or less, the output signal is turned off.

De-emphasis

This compensates for the 50 μ s pre-emphasis, making the overall frequency response of the system flat.

AF amplifier (AF)

This circuit amplifies the demodulated audio signal before it is passed to the expander.

Analogue switch (SW)

If the signal strength falls too far, the audio signal is muted using this switch. An LED indicates when this muting occurs.

Expander

The dynamic range of the audio signal is doubled by this circuit, which operates in much the same way as the compressor.

AF output amplifier (AF)

The output of the expander circuit is amplified again for output.

Voltage regulator (AVR)

This circuit provides the entire circuit with a stable 2.7 V supply from a battery voltage of between 3 V and 12 V.

Interface

Thanks to these complex modules that include almost all the necessary electronics, what remains is straightforward. **Figure 4** shows the two parts of the circuit. In the transmitter we can

either connect a microphone or any other desired audio source with a maximum output level of -15 dBV. In most cases, however, an electret microphone will be used. There is a small offset voltage present at the AF input with P1 adjusted to maximum: in our prototype we measured about 0.15 V. If a dynamic microphone is to be connected, it is essential to add a coupling capacitor. Alternatively, omit R1 and connect the dynamic microphone in place of the electret microphone. P1 can be used to attenuate microphone signals that are too high, so that the radio module is not overdriven.

The receiver circuit is slightly less simple. The receiver module has two outputs, one for the signal itself and one which indicates whether the signal strength is adequate or whether the muting circuit has been triggered. Since we have plenty of power to spare at the receiver (battery operation here is not essential) we can afford an extra indicator in the form of LED D1.

In order to amplify the output of the receiver module (which, at 10 k Ω , is not exactly low impedance, we have added a buffer amplifier. This is a classical non-inverting AC amplifier built around a rail-to-rail opamp which can operate from a voltage of between 2.7 V and 12 V, almost the same range as for the module. We have shown a supply voltage of 5 V, although 3 V or 12 V would do just as well. If a different (non-rail-to-rail) opamp were used, a supply voltage of 5 V would be required. Many opamps will only operate correctly with a symmetric power supply of ± 5 V or

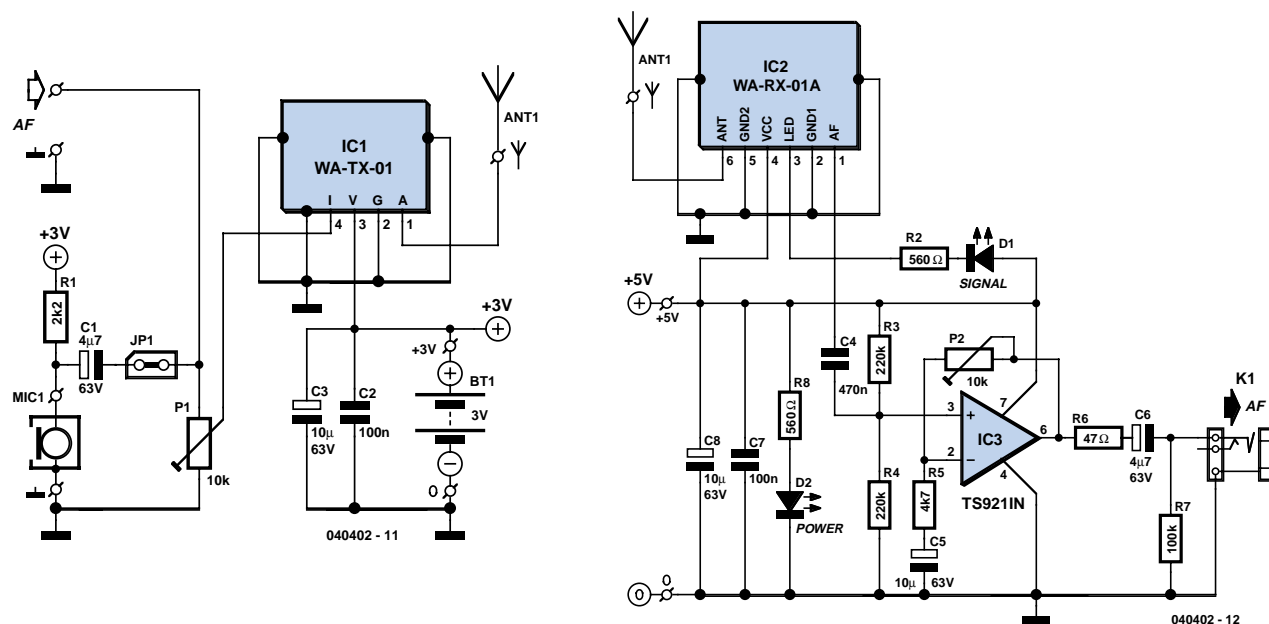


Figure 4. Interfaces for the radio modules.

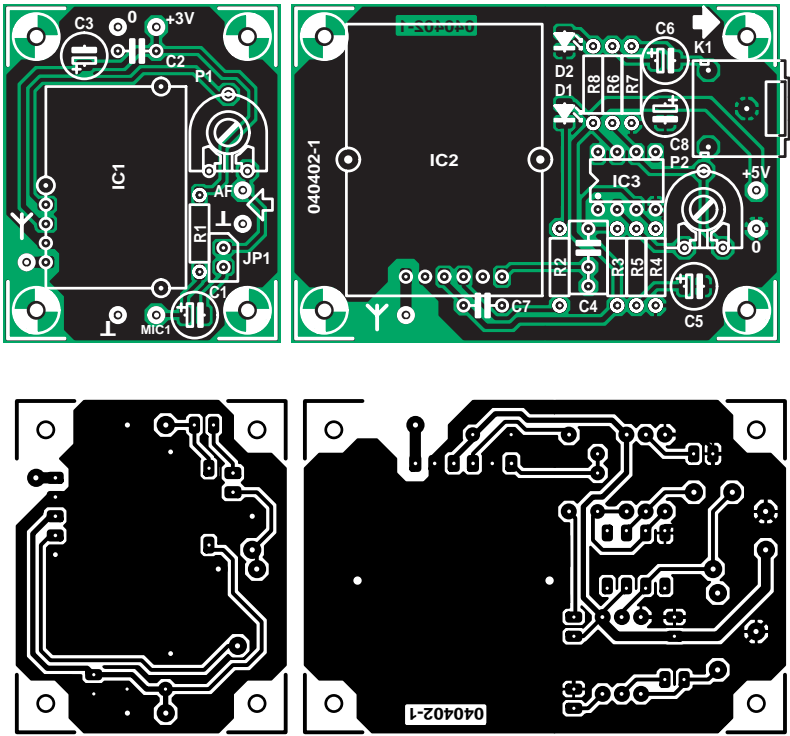


Figure 5. Two circuit boards make one radio link.

COMPONENTS LIST

Resistors:

R1 = 2k Ω
 R2,R8 = 560 Ω *
 R3,R4 = 220k Ω
 R5 = 4k Ω
 R6 = 47 Ω
 R7 = 100k Ω
 P1,P2 = 10 k Ω preset

Capacitors:

C1,C6 = 4 μ F 63V radial
 C2,C7 = 100nF
 C3,C5,C8 = 10 μ F 63V radial
 C4 = 470nF

Semiconductors:

D1 = LED, 3mm, green, low current
 D2 = LED, 3mm, red, low current
 IC1 = WA-TX-01 (Circuit Design)
 IC2 = WA-RX-01A (Circuit Design)
 IC3 = TS9211N (or equivalent rail-to-rail-opamp)

Miscellaneous:

JP1 = 2-way pinheader with jumper (angled if necessary)
 K1 = 3.5-mm jack socket, PCB mount (e.g. Conrad Electronics # 732893)
 BT1 = battery holder for two 1.5V batteries
 MIC1 = electret microphone PCB, no. 040402-1, available from the PCBShop



with an asymmetric 10 V supply. A further advantage of the TS921 used here is its high output drive capability: it can directly drive headphones or even two 32 Ω headphone transducers wired in parallel, although in this case C6 should be replaced by a 100 μ F 10 V type. The 47 Ω output resistor protects the opamp from the inductive load of a shielded cable and from short circuits. Trimmer potentiometer P2 allows the gain to be adjusted from unity (P2 at minimum resistance) to 10 dB (P2 at maximum resistance). C6 removes any DC component from the output and R7 ensures that there is always a load at the output. Since the opamp has asymmetrical supplies, a capacitor (C5) is also required in the feedback circuit. R3 and R4 set the operating point of the opamp at half the supply voltage. C7 and C8 provide extra power supply decoupling. At higher supply voltages it is necessary to increase the current-limiting resistors for the low-current LEDs so that the current through them does not exceed about 2 mA.

We have designed a two-part printed circuit board to accommodate the radio modules and the few external components (Figure 5). The layout is designed for optimum audio performance.

The components should be fitted to the board, observing that the transmitter module can only be fitted to the copper side. An ordinary 3.5 mm jack socket provides the audio output.

All that remains are the antennas. In principle a stiff piece of wire with length $1/4 \lambda$ (78 mm at 860 MHz) will do the job; more professional antennas can be found on the Circuit Design website at <http://www.cdt21.com/>.

(040402-1)

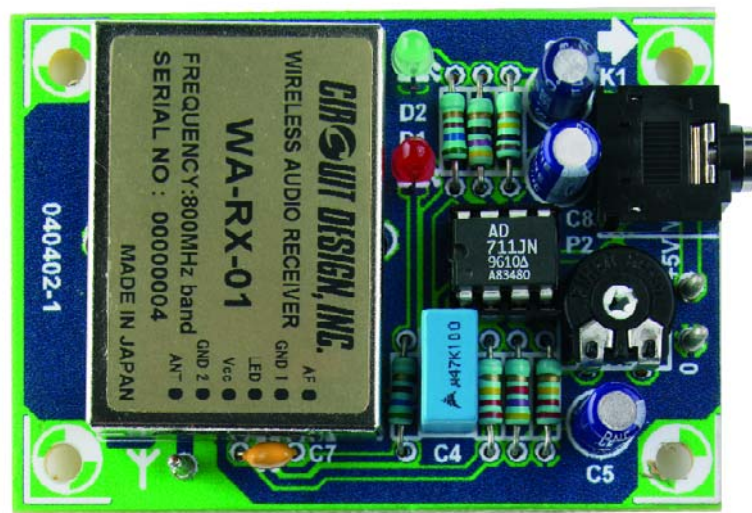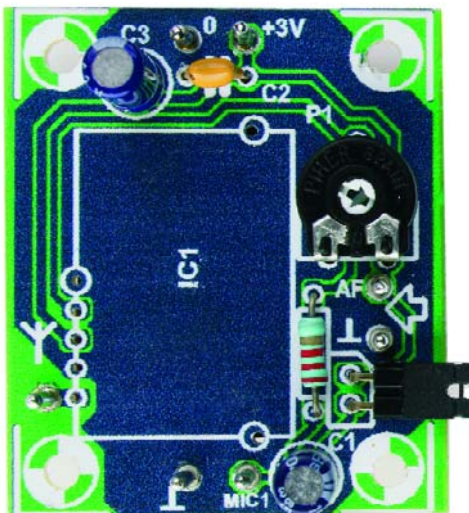

Frequency	863.125 MHz; 863.625 MHz; 864.500 MHz; 864.875 MHz
RF channels	one (fixed)
Emission code	F3E
Range	approx. 50 m line-of-sight
Signal-to-noise ratio	90 dB (with IHF-A filter)
Audio frequency range	50 Hz to 15 kHz \pm 3.5 dB (output level -50 dBV \pm 3 dB)
THD	2 % (@ AF 1 kHz, deviation = 15 kHz or 7.5 kHz)
Pre-emphasis	50 μ s
Operating temperature	0 °C to 50 °C

Transmitter

Oscillator	SAW oscillator, crystal-based
RF power	2 mW
Frequency stability	\pm 10 kHz
Pre-emphasis	50 μ s
Noise reduction	Compressor
Spurious emission	1 μ W maximum
Deviation	15 kHz (1 kHz @ -25 dBV)
Audio input level	-115 dBV to -15 dBV (1 kHz)
Audio input impedance	5 k Ω
Supply voltage	3 V to 9 V
Maximum module current consumption	25 mA
Measured current consumption	17 mA @ 3 V

Receiver




Receiver type	Superheterodyne
Mixer oscillator	Crystal-controlled
Intermediate frequency	10.7 MHz
Noise reduction	Expander
Sensitivity	21 dB μ V (@ THD 2 %)
Squelch sensitivity	17 dB μ V \pm 4 dB
Audio output level (at module)	-20 dBV (deviation = 15 kHz) Maximum -10 dBV (deviation = 30 kHz)
Audio output impedance (at module)	10 k Ω
Supply voltage	3 V to 12 V
Maximum module current consumption	30 mA
Measured current consumption (D2 on, R2 = R3 = 560 Ω)	32 mA @ 3 V 40 mA @ 5 V 52 mA @ 9 V


Note: 0 dBV = 0.775 V

Curve A shows the overall transfer characteristic of the entire radio link, measured at minimum gain (green) and maximum gain (red). The input signal to the transmitter was at -46 dBV (approximately 5 mV). The output signal at maximum gain was at -31 dBV. The output signal of the receiver is 5 dB above the input level to the transmitter. With a higher input signal level the response falls off somewhat at higher frequencies, but the amplitude at 5.5 kHz is up to 3 dB higher than that at 1 kHz.


Curve B shows the distortion (plus noise) at the output of the receiver against signal level, measured over the frequency range from 22 Hz to 22 kHz. The optimum value appears to occur with an input signal level at the transmitter of 5 mV. In this case the input signal is raised from -70 dBV to -15 dBV with the gain at the receiver is at a maximum. This is more than adequate for speech signals.

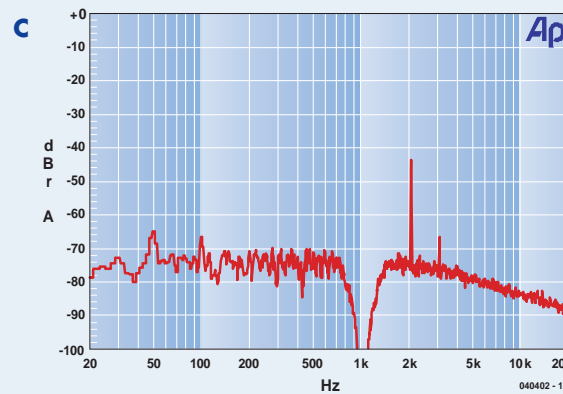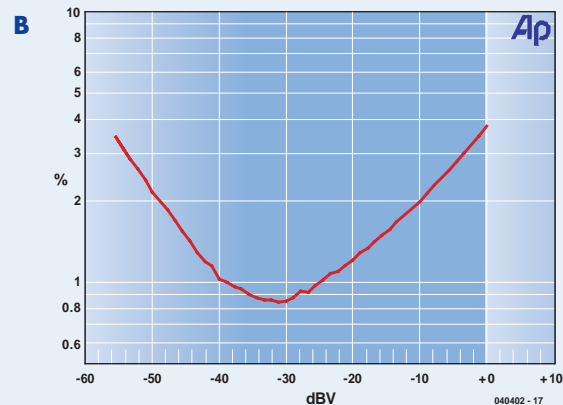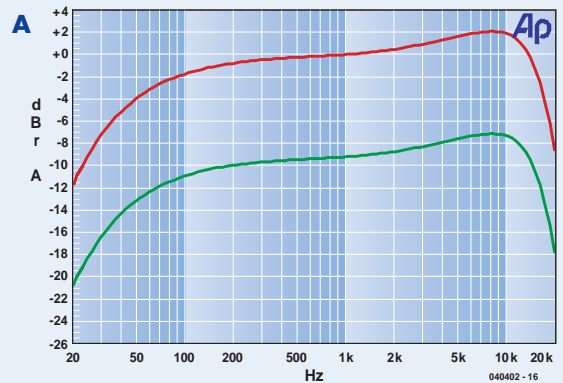Curve C shows the frequency spectrum with an input signal level at the transmitter of 5 mV. Most of the distortion is at the second harmonic. In this case the THD+N figure is 0.85 % (over the frequency range from 22 Hz to 22 kHz).



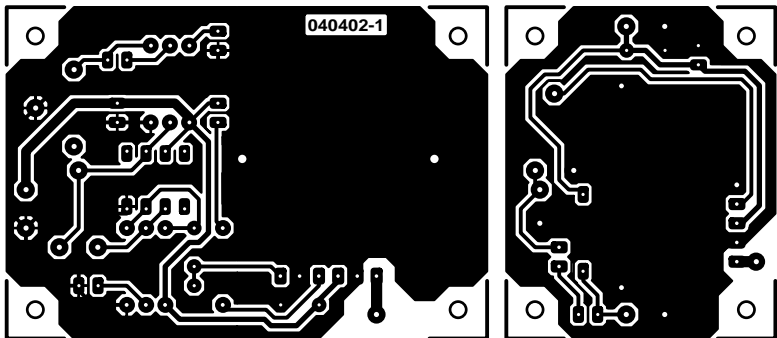

non reflected

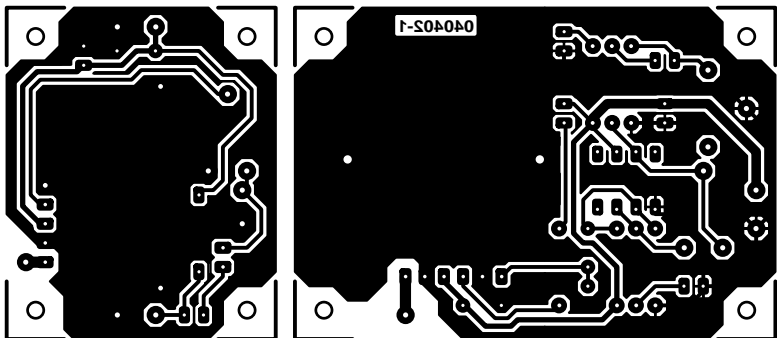

reflected