



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at

www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

Comparison of MM74HC to 74LS, 74S and 74ALS Logic

Fairchild Semiconductor
Application Note 319
June 1983



Comparison of MM74HC to 74LS, 74S and 74ALS Logic

The MM54HC/MM74HC family of high speed logic components provides a combination of speed and power characteristics that is not duplicated by bipolar logic families or any other CMOS family. This CMOS family has operating speeds similar to low power Schottky (54LS/74LS) technology. MM54HC/MM74HC is approximately half as fast (delays are twice as long) as the 54ALS/74ALS and 54S/74S logic. Compared to CD4000 and 54C/74C, this is an order of magnitude improvement in speed, which is achieved by utilizing an advanced 3.5 micron silicon gate-recessed oxide CMOS process. The MM54HC/MM74HC components are designed to retain all the advantages of older metal gate CMOS, plus provide the speeds required by today's high speed systems. Another key advantage of the MM54HC/MM74HC family is that it provides the functions and pin outs of the popular 54LS/74LS series logic components. Many functions which are unique to the CD4000 metal gate CMOS family have also been implemented in this high speed technology. In addition, the MM54HC/MM74HC family contains several special functions not previously implemented in CD4000 or 54LS/74LS.

Although the functions and the speeds are the same as 54LS/74LS, some of the electrical characteristics are different from either LS-TTL, S-TTL or ALS-TTL. The following discusses these differences and highlights the advantages and disadvantages of high speed CMOS.

AC PERFORMANCE

As mentioned previously, the MM54HC/MM74HC logic family has been designed to have speeds equivalent to LS-TTL, and to be 8–10 times faster than CD4000B and MM54C/MM74C logic. *Table 1* compares high speed CMOS to the bipolar logic families. HC-CMOS gate delays are typically the same as LS-TTL, and ALS-TTL is two to three times faster. S-TTL is also about twice as fast as HC-CMOS. Flip-flop and counter speeds also follow the same pattern.

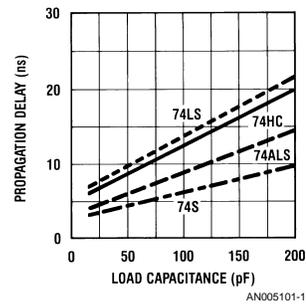


FIGURE 1. HC, LS, ALS, S Comparison of Propagation Delay vs Load for a NAND Gate

TABLE 1. Comparison of Typical AC Performance of LS-TTL, S-TTL, ALS-TTL and HC-CMOS

| Gates | LS-TTL | ALS-TTL | HC-CMOS | S-TTL | Units |
|---------------------------|--------|---------|---------|-------|-------|
| 74XX00 Propagation Delay | 8 | 5 | 8 | 4 | ns |
| 74XX04 Propagation Delay | 8 | 4 | 8 | 3 | ns |
| Combinational MSI | | | | | |
| 74XX139 Propagation Delay | | | | | |
| Select | 25 | 8 | 25 | 8 | ns |
| Enable | 21 | 8 | 20 | 7 | ns |
| 74XX151 Propagation Delay | | | | | |
| Address | 27 | 8 | 26 | 12 | ns |
| Strobe | 26 | 7 | 17 | 12 | ns |
| 74XX240 Propagation Delay | 12 | 3 | 10 | 5 | ns |
| Enable/Disable Time | 20 | 7 | 17 | 10 | ns |
| Clocked MSI | | | | | |
| 74XX174 Propagation Delay | 20 | 7 | 18 | 13 | ns |
| Operating Frequency | 40 | 50 | 50 | 100 | MHz |
| 74XX374 Propagation Delay | 19 | 7 | 16 | 11 | ns |
| Enable/Disable Time | 21 | 9 | 17 | 11 | ns |
| Operating Frequency | 50 | 50 | 50 | 100 | MHz |

Also, HC logic's propagation delay variation due to changes in capacitive loading is very similar to LS-TTL. *Figure 1* illustrates this by plotting delay versus loading for the various bipolar logic families and MM54HC/MM74HC. HC-CMOS has virtually the same speed and load-delay variation as LS-TTL and, as is expected, is slower than ALS and S-TTL logic. The

slopes of these lines indicate the amount of variation in speed with loading, and are dependent on the output impedance of the particular logic gate. The delay variation of LS-TTL and HC-CMOS is similar whereas ALS-TTL and S-TTL have slightly less variation.

AN-319

POWER DISSIPATION

CD4000B and MM54C/MM74C CMOS devices are well known for extremely low quiescent power dissipation, and high speed CMOS retains this feature. Table 2 compares typical HC static power consumption with LS, ALS and S-TTL. Even CMOS MSI dissipation is well below 1 μ W while LS-TTL dissipation is many milliwatts. This makes MM54HC/MM74HC ideal for battery operated or ultra-low power systems where the system may be put to "sleep" by shutting off the system clock.

TABLE 2. Comparison of Typical Quiescent Supply Current for Various Logic Families

| | HC-CMOS | LS-TTL | ALS-TTL | S-TTL |
|-----------|----------------|---------|---------|--------|
| SSI | 0.0025 μ W | 5.0 mW | 2.0 mW | 75 mW |
| Flip-Flop | 0.005 μ W | 20.0 mW | 10 mW | 150 mW |
| MSI | 0.25 μ W | 90 mW | 40 mW | 470 mW |

CMOS dissipation increases proportionately with operating frequency. Doubling the operating frequency doubles the current consumption. This is due to currents generated by charging internal and load capacitances. Figure 3 shows power dissipation versus frequency for a completely unloaded NAND gate, flip-flop and counter implemented in all 4 technologies.

The LS, S and ALS curves are essentially flat because the quiescent currents mask out capacitive effects, except at very high frequencies. Capacitive effects are slightly lower for the TTL families, so that, at high frequencies, CMOS dissipation may actually be more than ALS and LS. However, the power crossover frequency is usually well above the maximum operating frequency of MM54HC/MM74HC.

The previously mentioned curves plot unloaded circuits. When considering typical system power consumption, capacitive loading should also be considered. Table 3 lists components to implement all the support logic for a small mi-

croprocessor based system. By assuming a typical load capacitance of 50 pF, the power dissipation for these devices can be calculated at various average system clock frequencies. Figure 2 plots power consumption for 74HC, 74LS, 74ALS and 74S logic implementations. Above 1 MHz, capacitive currents now also tend to dominate bipolar power dissipation as well.

TABLE 3. Hypothetical "Glue" Logic for a Typical Microprocessor System

| System Components | # of ICs |
|--------------------------------------|----------|
| Address Decoders ('138) | 10 |
| Address Comparators ('688) | 5 |
| Address/Data Buffers ('240/4) | 10 |
| Address/Data Latches ('373/4) | 20 |
| MSI Control/Gating ('00, '10) | 30 |
| Misc. Counter/Shift Reg ('161, '164) | 20 |
| Flip-Flops ('73/4) | 10 |



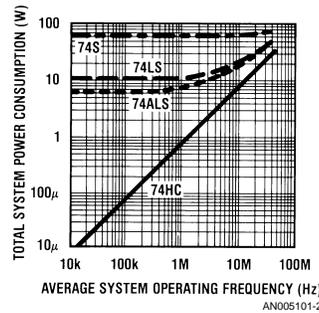



FIGURE 2. Power Consumption for Hypothetical Microprocessor System Support Logic

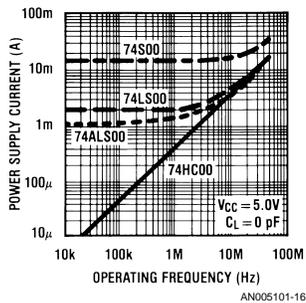

(a)

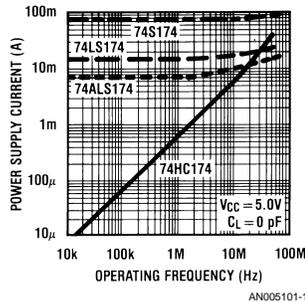

(b)

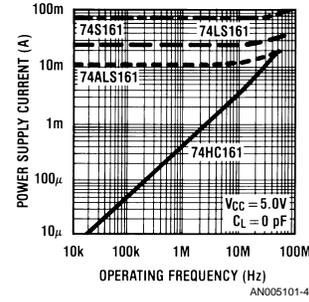

(c)

FIGURE 3. Supply Current Consumption Comparison for (a) 74XX00 (b) 74XX174 (c) 74XX161 Circuits

Since, in a typical system, some sections will operate at a high frequency and other parts at lower frequencies, the average system clock frequency is a simplification. For example, a 10 MHz microprocessor will have a bus cycle frequency of 2 to 5 MHz. Most system and memory components will be accessed a small amount of the time, resulting in effective clock frequencies on the order of 100 kHz

for these sections. Thus, the average system clock frequency would be around 1 to 2 MHz, and an 8 to 1 power savings would be realized by using CMOS.

Another simplification was made to calculate system power. CMOS circuits will dissipate much less power when 3-STATE, which would save much power since, in a given

bus cycle, only a few buffers will be enabled. LS, ALS and S, however, actually dissipate more power when their outputs are disabled.

Several interesting conclusions can be drawn from *Figure 2*. First, notice that, at higher frequencies, the bipolar logic families start to dissipate more power. This is a result of current consumption due to switching the load. As the operating frequency approaches infinity, this will be the dominant effect. So, for extremely fast low power systems, minimizing load capacitance and overall operating frequency becomes more important. As lower power TTL logic is introduced, system power will be increasingly dependent on capacitive load effects similar to CMOS.

Second, TTL logic has a slightly smaller logic voltage swing than CMOS. Thus, for a given load, TTL will actually have a lower average load current. So, similar to the unloaded example, at very high frequencies, CMOS could consume more power than TTL. As *Figure 5* indicates, these frequencies are usually far above the 30 MHz limit of HC-CMOS or LS-TTL.

INPUT VOLTAGE CHARACTERISTICS AND NOISE IMMUNITY

To maintain the advantage CMOS has in noise immunity, the input logic levels are defined to be similar to metal gate CMOS. At $V_{CC}=5V$, MM54HC/MM74HC is designed to have input voltages of $V_{IH}=3.5V$ and $V_{IL}=1.0V$. Additionally, input voltage over the operating supply voltage range is: $V_{IH}=0.7V_{CC}$ and $V_{IL}=0.2V_{CC}$. This compares to $V_{IH}=2.0V$ and $V_{IL}=0.8V$ specified for LS-TTL over its supply range. *Figure 4* illustrates the input voltage differences, and the greater noise immunity HC logic has over its supply range. Maintaining wide noise immunity gives HC-CMOS an advantage in many industrial, automotive, and computer applications where high noise levels exist.

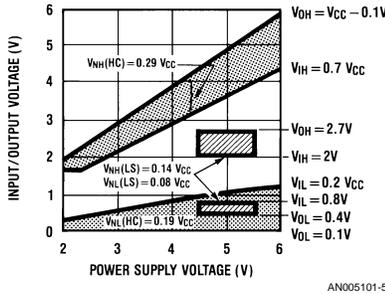


FIGURE 4. Worst-Case Input and Output Voltages Over Operating Supply Range for HC and LS Logic

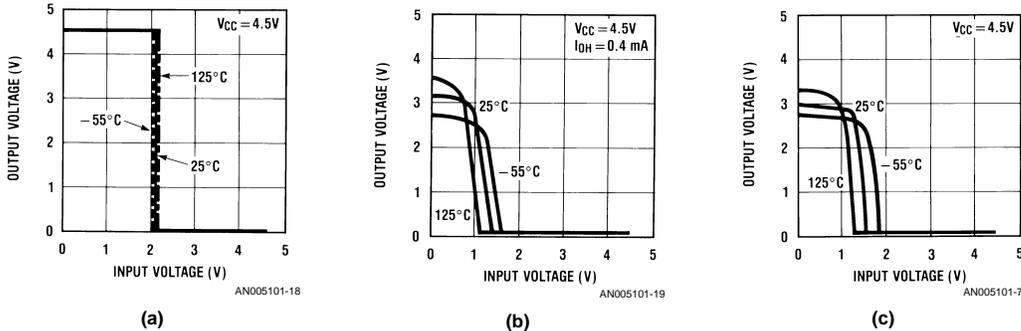


FIGURE 5. Input-Output Transfer Characteristics for 74XX00 NAND Gate Implemented in (a) HC-CMOS (b) LS-TTL (c) ALS-TTL

Another indication of DC noise immunity is the typical transfer characteristics for the logic families. *Figure 5* shows the transfer function of the 74XX00 NAND gate for HC-CMOS, LS-TTL and ALS-TTL. High speed CMOS has a very sharp transition typically at 2.25V, and this transition point is very stable over temperature. The bipolar logic transfer functions are not as sharp and vary several hundred millivolts over temperature. This sharp transition is due to the large circuit gains provided by triple buffering the HC-CMOS gate com-

pared to the single bipolar gain stage. *Figure 6* compares the transfer function of the 'HC08 and the 'ALS08, both of which are double buffered. The 'ALS08 has a sharper transition, but the CMOS gate still has less temperature variation and a more centered trip point. However, the TTL trip point is not dependent on V_{CC} variation as CMOS is.

The high speed CMOS input levels are not totally compatible with TTL output voltage specifications. To make them com-

patible would compromise noise immunity, die size, and significant speed. The designer may improve compatibility by adding a pull-up resistor to the TTL output. He may also utilize a series of TTL-to-CMOS level converters which are being provided to ease design of mixed HC/LS/ALS/S systems. These buffers have 0.8V and 2.0V TTL input voltage specifications, and provide CMOS compatible outputs. When mixing logic, the noise immunity at the TTL to CMOS interface is no better than LS-TTL, but a substantial savings in power will occur when using MM54HC/MM74HC logic.

INPUT CURRENT

The HC family maintains the ultra-low input currents typical of CMOS circuits. This current is less than $1\ \mu\text{A}$ and is caused by input protection diode leakages. This compares to

the much larger LS-TTL input currents of 0.4 mA for a low input and $40\ \mu\text{A}$ for a high input. ALS-TTL input currents are 0.2 mA and $20\ \mu\text{A}$ and S-TTL input currents are 3.2 mA and $100\ \mu\text{A}$. Figure 7 tabulates these values. The near zero input current of CMOS eases designing, since a typical input can be viewed as an open circuit. This eliminates the need for fanout restrictions which are necessary in TTL logic designs.

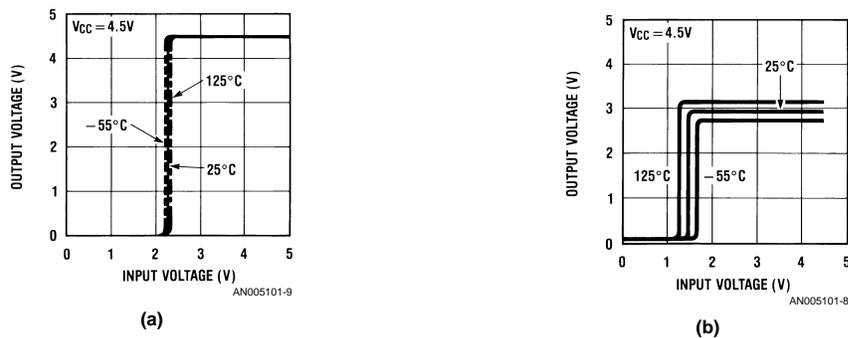


FIGURE 6. Input-Output Transfer Characteristics for 74XX08 AND Gate Implemented in (a) HC-CMOS (b) ALS-TTL

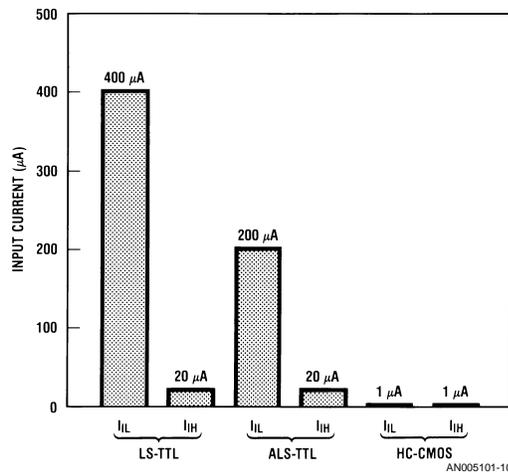


FIGURE 7. Comparison of Input Current Specifications for Various Logic Families

POWER SUPPLY RANGE

Figure 4 also compares the supply range of MM54HC/MM74HC logic and LS-TTL. The high speed CMOS family is specified to operate at voltages from 2V to 6V. 54LS, 54S and 54ALS logic is specified to operate from 4.5V to 5.5V,

and 74LS and 74S will operate from 4.75V to 5.25V. 74ALS is specified over a 4.5V to 5.5V supply range. This wider operating range for the HC family eases power supply design by eliminating costly regulators and enhances battery operation capabilities.

OUTPUT DRIVE

Since there was no speed, noise immunity, or power trade-off, standard HC-CMOS was designed to have similar high current output drive that is characteristic of LS-TTL and ALS-TTL. Schottky TTL has about 5 times the output drive of MM54HC/MM74HC. Thus HC-CMOS has an output low current specification of 4 mA at an output voltage of 0.4V. In keeping with CD4000B series and 54C/74C series logic, the source and sink currents are symmetrical. Thus HC logic can source 4 mA as well. This large increase in output current for high speed CMOS over CD4000B also has the added advantage of reducing signal line crosstalk which can be of greater concern in high speed systems. Figure 8 compares HC, LS, and ALS specified output currents.

Since TTL logic families do have significant input currents they have a limited fanout capability. Table 4 illustrates the limitations of these families, based on their input and output currents. High speed CMOS is also included. MM54HC/MM74HC has the same CMOS-to-CMOS fanout characteristics as CD4000B, virtually infinite.

TABLE 4. Fanout of HC-CMOS, LS-TTL, ALS-TTL, S-TTL

| From, To | 74HC | 74LS | 74ALS | 74S |
|----------|------|------|-------|-----|
| 74HC | 4000 | 10 | 20 | 2 |
| 74LS | * | 20 | 40 | 4 |
| 74ALS | * | 20 | 40 | 4 |
| 74S | * | 50 | 100 | 10 |

As another indication of the similarity of HC-CMOS to LS-TTL, Figure 9 plots typical output currents versus output voltage for LS and HC. The output sink current curves are very similar, but LS source current is somewhat different, due to its emitter-follower output circuitry.

MM54HC/MM74HC bus driving circuits, namely the 3-STATE buffers and latches, have half again as much output current drive as standard outputs. These components have a 6 mA output drive. The 6 mA was chosen based on a trade-off of die size and speed-load variations. This current is less than the 12 mA or more specified for LS and ALS bus driver circuits, because the bus fanout limitations of these families do not apply in CMOS systems. S-TTL bus output sink current is 48 mA.



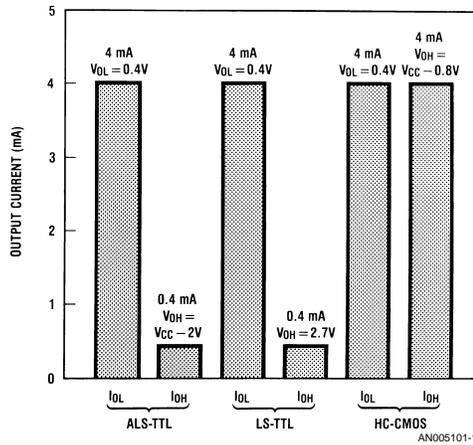


FIGURE 8. Output Current Specifications for ALS-TTL, S-TTL and HC-CMOS

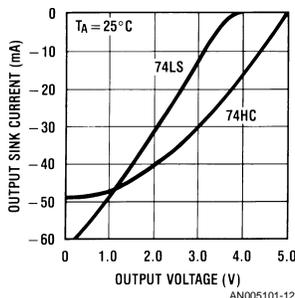

(a)

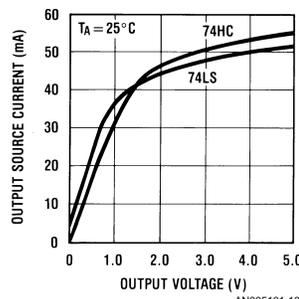

(b)

FIGURE 9. Comparison of Standard LS-TTL and HC-CMOS Output (a) Source (b) Sink Currents

OPERATING TEMPERATURE RANGE

The operating temperature range and temperature effects on various HC-CMOS operating parameters differ from bipolar logic. The recommended temperature range for 74LS, 74S, and 74ALS is 0°C to 70°C, compared to -40°C to 85°C for the 74HC family. 54 series logic is specified from -55°C to 125°C for all four families.

Temperature variation of operating parameters for the MM54HC/MM74HC family behaves very predictably and is due to the gain decreasing of MOSFET transistors as temperature is increased. Thus the output currents decrease and propagation delays increase at about 0.3% per degree centigrade.

Figure 10 shows typical propagation delays for the 74XX00 over the -55°C to +125°C temperature range. The 'HC00's speed increases almost linearly with temperature, whereas the LS and ALS behave differently.

A WORD ABOUT PLUG-IN REPLACEMENT OF TTL

MM54HC/MM74HC logic implements TTL equivalent functions with the same pin outs as TTL. HC is not designed to be directly plug-in replaceable, but, with some care, some TTL systems can be converted to MM54HC/MM74HC with little or no modification. The replaceability of HC is determined by several factors.

One factor is the difference in input levels. In systems where all TTL is not being replaced and TTL outputs feed CMOS inputs, the input high voltages, as specified, are not totally compatible. Although TTL outputs will typically drive HC inputs correctly, an external pull-up resistor should be added to the TTL outputs, or an MM54HCT/MM74HCT TTL compatible circuit should be used. This incompatibility tends to limit the designer's ability to intermingle TTL and HC-CMOS.

Note, though, that HC outputs are completely compatible with the various TTL family's input specifications; therefore, there is no problem when HC is driving TTL.

Another source of possible problems can occur when the LS design floats device inputs. This practice is not recommended when using LS-TTL, but it is sometimes done. Usually, TTL inputs float high; however, CMOS inputs may float either high or low depending on the static charge on the input. It is therefore important to always tie unused CMOS inputs to either V_{CC} or ground to avoid incorrect logic functioning.

A third factor to consider when replacing any TTL logic is AC performance. The logic functions provided by 54HC/74HC are equivalent to LS-TTL, and the propagation delay, set-up and hold times are similar to LS. However, there are some differences in the way CMOS circuits are implemented which will cause differences in speed. For the most part, these differences are minor, but it is important to verify that they do not affect the design.

CONCLUSION

The MM54HC/MM74HC family represents a major step forward in CMOS performance. It is a full line family capable of being designed into virtually any application which now uses LS-TTL with substantial improvement in power consumption. ALS and S-TTL primarily offer faster speeds than HC-CMOS, but still do not have the input and output advantages or the lower power consumption of CMOS. Because of its high input impedance and large output drive, HC logic is actually easier to use. This, coupled with continued expansion of the 54HC/74HC, will make it an increasingly popular logic family.


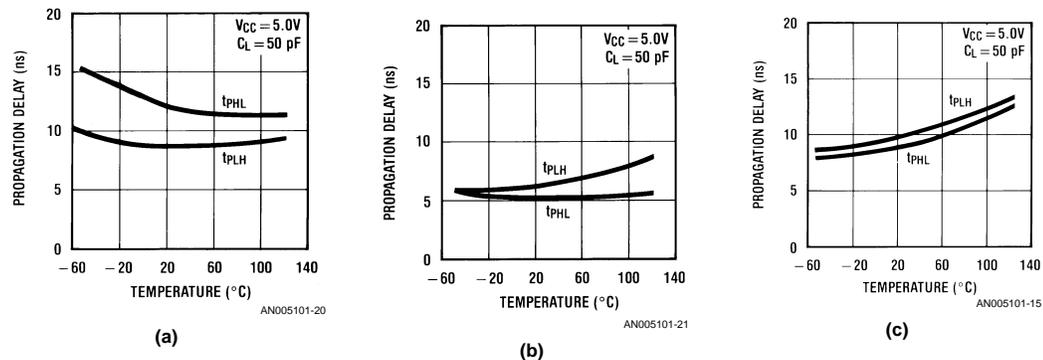


FIGURE 10. Propagation Delay Variation Across Temperature for (a) 74LS00 (b) 74ALS00 and (c) 74HC00

 

| | | | |
|---|---|--|---|
| <p>LIFE SUPPORT POLICY</p> <p>FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:</p> <ol style="list-style-type: none">1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness. | | | |
| <p>Fairchild Semiconductor Corporation Americas Customer Response Center Tel: 1-888-522-5372</p> | <p>Fairchild Semiconductor Europe Fax: +49 (0) 1 80-530 85 86 Email: europe.support@nsc.com Deutsch Tel: +49 (0) 8 141-35-0 English Tel: +44 (0) 1 793-85-68-56 Italy Tel: +39 (0) 2 57 5631</p> | <p>Fairchild Semiconductor Hong Kong Ltd. 13th Floor, Straight Block, Ocean Centre, 5 Canton Rd. Tsimshatsui, Kowloon Hong Kong Tel: +852 2737-7200 Fax: +852 2314-0061</p> | <p>National Semiconductor Japan Ltd. Tel: 81-3-5620-6175 Fax: 81-3-5620-6179</p> |
| <p>www.fairchildsemi.com</p> | | | |

Fairchild does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and Fairchild reserves the right at any time without notice to change said circuitry and specifications.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative