



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at
www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

AN-4158

Symmetric Dual N-Channel Shielded Gate PowerTrench® MOSFETs for Half-Bridge DC-DC Converter in Telecommunication Brick Module Application

Abstract

This application note presents symmetric dual N-channel shielded gate PowerTrench® MOSFETs optimized for the primary switches of a half-bridge DC-DC converter. A well-balanced $R_{DS(ON)}$ and Q_g of a shielded gate PowerTrench® MOSFET technology improves the Figure of Merit (FOM) ($R_{DS(ON)} \times Q_g$) factor is selected to achieve the highest efficiency with a well-balanced ratio between conduction loss and switching losses. A symmetric dual N-channel Power56 package containing two identical dies for primary high-side and low-side switches is able to increase the power density. The validity of symmetric dual N-channel shielded gate PowerTrench® MOSFETs is tested on a 100 W half-bridge DC-DC converter in a telecommunication quarter-brick size module.

Introduction

A brick DC-DC converter with a 48 V DC voltage bus in a telecommunication and network application needs higher power within the limited standard area, so higher efficiency and power are required. Internet facilities and telecommunication systems require sophisticated infrastructure and functionality. To design a highly efficient brick DC-DC converter, it is important to select the proper MOSFET because it generates most of power losses. MOSFET power losses consist of conduction and switching losses. Conduction loss is dominated by on-state resistance ($R_{DS(ON)}$). Switching losses are dominated by the gate charge (Q_g). To reduce power losses of a MOSFET, a well-balanced $R_{DS(ON)}$ and Q_g combination should be selected due to their trade-off relationship. Excellent thermal performance and compact size package is also essential to increase power density because the brick size of DC-DC converters is standardized regardless of power requirements.

This application note is organized as follows. In Section I, a basic operation of the half-bridge DC-DC converter and MOSFET power loss analysis in primary switch are performed. In Section II, shielded gate PowerTrench® MOSFET technology is shown and the power loss of

different $R_{DS(ON)}$ - Q_g combinations of the given technology are examined. Experimental results of Power56 symmetric dual N-channel shielded gate PowerTrench® MOSFETs in 100 W half-bridge DC-DC converter ($V_{IN}=36\text{ V}\sim 48\text{ V}$, $V_{OUT}=3.3\text{ V}$, $I_{OUT}=30\text{ A}$) are provided in Section III.

Section I

Telecommunication Brick DC-DC Converter

As telecommunication and network systems require a higher power due to the complex infrastructure support, their power architecture has been changed from Distributed Power Architectures (DPAs) to Intermediate Bus Architectures (IBAs) to increase the total system efficiency. Front-end isolated converters in Figure 1 were utilized in traditional DPAs to supply all required voltage levels from higher input, such as 48 V, to lower voltages required by each load. In some cases, these architectures cause high current circulating on the boards, along with fairly large voltage drop; therefore increasing power consumption. In IBA, the front-end converter would be similar to DPA, but the intermediate bus converter produces a bus line voltage and then Point of Load (POL) converters change it into the required voltages. Sharing this bus line means POLs can be synchronous buck or boost converters that can achieve the greatest efficiency and minimize the system size. An intermediate brick DC-DC module needs a higher efficiency and more power density as it increases its power coverage.

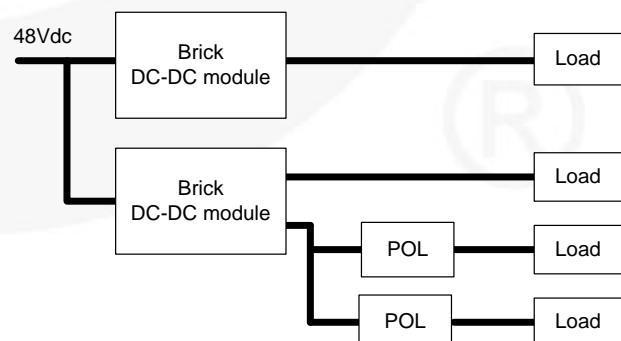


Figure 1. Distributed Power System Architecture

 


Figure 2. Power System Intermediate Bus Architecture

Basics of Half-Bridge DC-DC Converter

Along with reducing the brick DC-DC module size and increasing power density, the half-bridge topology offers high efficiency and good power handling capability up to 200 W. It is a good choice in isolated step-down DC-DC topologies. Figure 3 shows waveforms of the primary QH and QL for each time interval and Figure 4 - Figure 7 show the equivalent circuit of the half bridge DC-DC converter with a transformer center-tapped rectifier for each time interval. Each time interval is determined by switching of both primary high-side and low-side MOSFETs.

[$T_0 - T_1$]: Primary high-side MOSFET (QH) and secondary synchronous MOSFET (QS1) are ON and primary low-side MOSFET (QL) and other secondary synchronous MOSFETs (QS2) are OFF. The voltage across the primary transformer (V_p) is a half of input voltage (V_{IN}) and the secondary transformer voltage (V_s) is V_p / N . N is turn ratio of the transformer. The voltage across the output inductor is $V_s - V_O$ and the inductor charges the current.

[$T_1 - T_2$]: Primary QH and QL are OFF and QS1 and QS2 are ON. V_p and V_s are zero voltage. The voltage across the output inductor is $-V_O$ and the output inductor is discharged through QS1 and QS2.

[$T_2 - T_3$]: Primary QL and QS2 are ON and primary QH and QS1 are OFF. The voltage across the primary transformer (V_p) is a negative half of V_{IN} and the secondary transformer voltage (V_s) is V_p / N . The voltage across the output inductor is $V_s - V_O$ and the inductor charges the current.

[$T_3 - T_4$]: Primary QH and QL are OFF and QS1 and QS2 are ON. V_p and V_s are zero voltage. The voltage across the output inductor is $-V_O$ and the output inductor is discharged through QS1 and QS2.

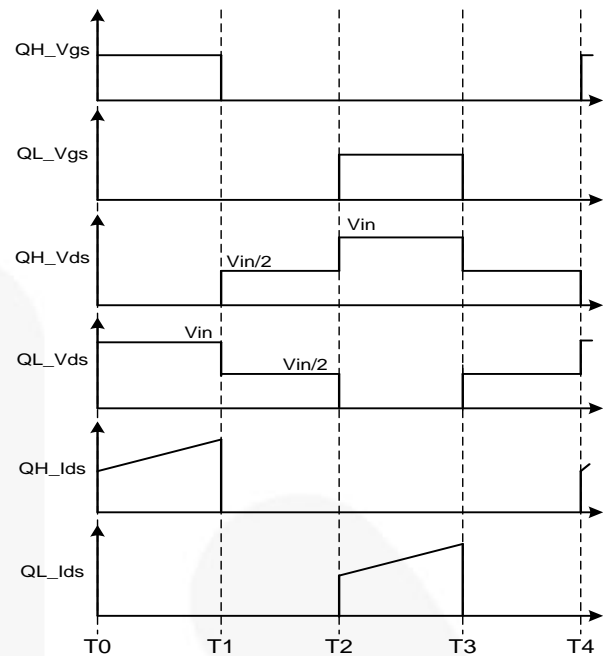


Figure 3. Primary MOSFETs Waveforms in Half-Bridge

 


Figure 4. Half-Bridge Equivalent Circuit for Operation Time Interval; [$T_0 - T_1$] QH:ON, QL:OFF, QS1:ON, QS2:OFF

 


Figure 5. Half-Bridge Equivalent Circuit for Operation Time Interval [$T_1 - T_2$] QH:OFF, QL:OFF, QS1:ON, QS2:ON

 


Figure 6. Half-Bridge Equivalent Circuit for Operation Time Interval $[T_2 - T_3]$ QH:OFF, QL:ON, QS1:OFF, QS2:ON

 


Figure 7. Half-Bridge Equivalent Circuit for Operation Time Interval $[T_3 - T_4]$ QH:OFF, QL:OFF, QS1:ON, QS2:ON

Power Losses in Primary MOSFETs of Half-Bridge DC-DC Converter

Power losses in primary QH and QL MOSFETs of the half-bridge topology consist of the conduction loss and switching losses. The conduction loss is dominated by the $R_{DS(ON)}$ of the MOSFET, increased by a drain-to-source current.

$$\text{Conduction loss} = I_{RMS}^2 \times R_{DS(ON)} \quad (1)$$

Switching losses are dominated by gate charge (Q_g) and it increases by drain-to-source voltage. Switching losses can be broken into turn-on and off crossover losses, an output capacitance loss, and a gate-driving loss. Figure 8 shows gate-to-source voltage (V_{gs}) and a turn-on crossover loss when a MOSFET turns on in an inductive load.

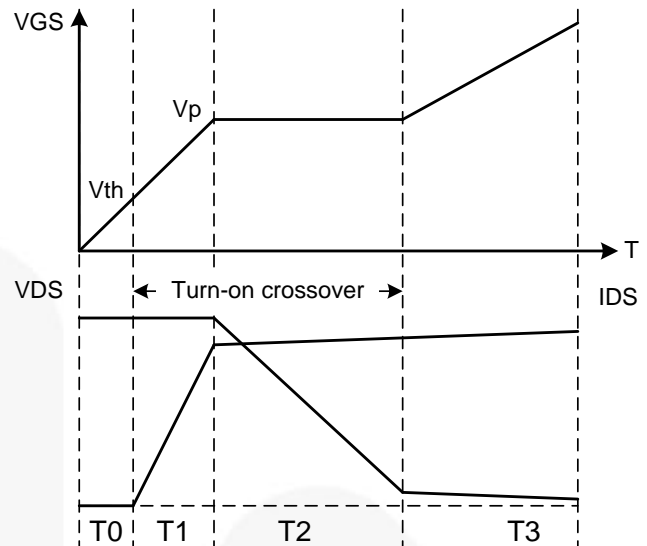


Figure 8. Gate to Source Voltage and Turn-on Crossover Loss

MOSFET switching starts by charging the MOSFET's input capacitance (C_{iss}). During T_0 , there is no change in drain-to-source voltage (V_{DS}) and drain-to-source current (I_{ds}). Once V_{gs} reaches V_{th} , a MOSFET starts conducting and I_{ds} rises during T_1 . V_{DS} is still clamped. During T_2 , V_{DS} begins fall. Drain-to-gate voltage takes on negative values, so the reverse transfer capacitance (C_{rss}) increases hugely. Due to the dramatic rise in C_{rss} , V_{gs} is held at the plateau voltage (V_p). In T_3 , the MOSFET is fully enhancing the channel to obtain its rated $R_{DS(ON)}$ at V_{gs} . Turn-on crossover loss occurs in T_1 and T_2 of turn-on crossover time ($\text{Turn-on}_{crossover}$). The turn-off crossover loss occurs in the same manner as the turn-on crossover.

$$\text{Crossover loss} = 0.5 \times (V_{DS} \times I_{ds}) \times (\text{Turn-on}_{crossover} + \text{Turn-off}_{crossover}) \times f_{sw} \quad (2)$$

where f_{sw} is a switching frequency.

The stored charge in the output capacitance (C_{oss}) is dissipated as shown in the below equation:

$$\text{Output capacitance loss} = 0.5 \times (C_{oss} \times V_{ds}^2 \times f_{sw}) \quad (3)$$

Gate driving loss at driver is related to the gate charge as:

$$\text{Gate driving loss} = Q_g \times V_{gs} \times f_{sw} \quad (4)$$

To reduce power losses of a MOSFET, $R_{DS(ON)}$ and Q_g must improve, but $R_{DS(ON)}$ and Q_g have a trade-off relationship.

Section II


Shielded Gate PowerTrench® MOSFET Technology

Figure 9(a) shows the vertical structure of the conventional PowerTrench. To reduce $R_{DS(ON)}$ of the conventional PowerTrench, the pitch between gate trenches is reduced to make more cells in the limited die size, but it causes increased reverse transfer capacitance (C_{rss}), resulting in increased switching losses.

Table 1. Components of $R_{DS(ON)}$ for Conventional Trench, $R_{DS(ON)}$ $V_g = 10$ V, 200 A/cm²

	$V_{DS} = 30$ V	$V_{DS} = 100$ V
$R_{Channel}$	47%	16%
$R_{Epitaxial}$	29%	78%
$R_{Substrate}$	24%	6%

Table 1 shows the $R_{DS(ON)}$ components, comparing a 30 V-rated with a 100 V-rated conventional trench MOSFET. The $R_{DS(ON)}$ contribution from the epitaxial drift region is a much larger percentage for the 100 V MOSFET because a high blocking voltage requires a relatively thick and low-doped epitaxial drift region. Fairchild’s shielded gate PowerTrench® MOSFET employs the shield electrode connected to source for the charge balance in epitaxial drift region, as shown in Figure 9(b).^[1] The electric field in epitaxial is plated by the charge balance, so the doping concentration in epitaxial can be increased, resulting in a reduced epitaxial resistance. It leads reduced conduction loss of a MOSFET.

 

(a) Conventional PowerTrench (b) Shielded Gate PowerTrench

Figure 9. (a) Conventional vs. (b) Shielded-Gate Vertical Structure PowerTrench® MOSFET

The shield electrode resides below the gate electrode, converting most of the gate-to-drain capacitance (C_{gd} or C_{rss}) at the bottom of the conventional trench MOSFET to gate-to-source capacitance (C_{gs}). The shield electrode wraps the gate electrode from the drain potential.

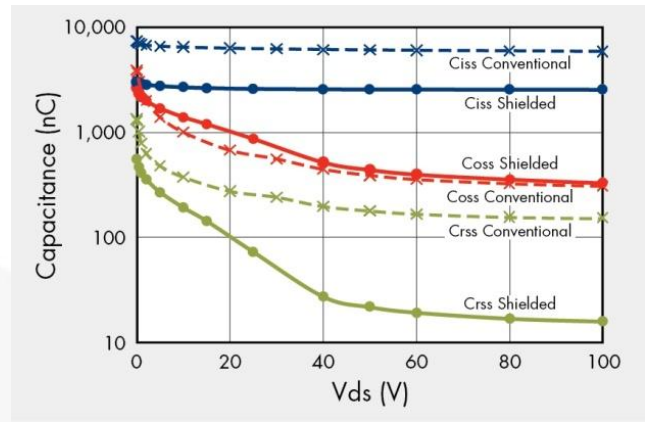


Figure 10. Comparison of Capacitive Components for Conventional and Shielded-Gate Trench with Equivalent 20 A $R_{DS(ON)}$ 5.7 mΩ

Figure 10 compares the capacitive components of a conventional and a shielded-gate trench MOSFET with equivalent $R_{DS(ON)}$. By reducing C_{rss} , turn-on and turn-off crossover losses are minimized by shortening the T_2 period in Figure 8.

Optimized $R_{DS(ON)}$ and Q_g for High-Efficiency Half-Bridge DC-DC Converter

Telecommunication brick DC-DC converters request the wide input voltage range from 36 V to 75 V. At the minimum input voltage of 36 V, the conduction loss has the larger portion of the maximum input voltage of 75 V due to higher current in Equation (1). The switching losses are reduced at the minimum input voltage since drain-to-source voltage (V_{DS}) is reduced in equation (2) and (3). Table 2 shows the electrical specification of the quarter brick DC-DC converter in this application note.

Table 2. Electrical Specification of Quarter Brick DC-DC Module

Brick DC-DC Module Size	Quarter Brick
Topology	Half-Bridge
Input Voltage	36 V ~ 75 V
Output Voltage	3.3 V
Maximum Output Current	30 A
Switching Frequency	200 kHz

Table 3 shows different $R_{DS(ON)}$ and Q_g combinations of shielded gate PowerTrench® MOSFET.

Table 3. Measured Electrical Parameters

MOSFETs	$R_{DS(ON)}$ [mΩ] at 10 V_{gs}	Q_g [nC] at 10 V_{gs}
A	6.3	39.0
B	11	19
C	20.0	11.7
D	27.0	7.5

Figure 11 shows the evaluated efficiency graph at 100 W of output power with the various $R_{DS(ON)}$ and Q_g combinations.


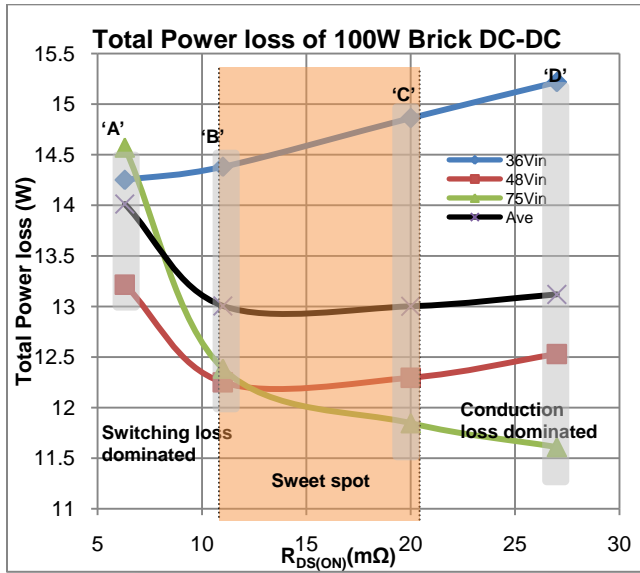


Figure 11. Efficiency & Power Loss, Varied $R_{DS(ON)}$ at $V_{IN}=48\text{ V}$, $V_{OUT}=3.3\text{ V}$, $I_{OUT}=30\text{ A}$, $T_A=25^\circ\text{C}$, Natural Convention

Because MOSFET Q_g and $R_{DS(ON)}$ have an inverse relationship, the switching losses of a MOSFET with a lower $R_{DS(ON)}$ tend to increase even if the conduction loss is decreased. On the other hand, the conduction loss of a higher $R_{DS(ON)}$ MOSFET is increased, but the switching losses are reduced. Figure 11 shows that the power loss tendency at the maximum 75 V input voltage is reduced by decreasing Q_g rather than $R_{DS(ON)}$, even though, in the minimum voltage of 36 V, the lowest $R_{DS(ON)}$ MOSFET has the lowest power loss. Each switching loss and condition loss ratios depends on the input voltage. In the case of ‘B’ in Figure 11, the total power loss at 36 V, 48 V, and 75 V of input voltage is 14.38 W, 12.24 W, and 12.38 W, respectively. The average power loss according to the input voltage from 36 V to 75 V is calculated to 13 W. By using the average power loss graph, an optimized $R_{DS(ON)}$ and Q_g combination can be found. To achieve the highest efficiency in all the input voltage coverage, a well-balanced $R_{DS(ON)}$ and Q_g MOSFET should be selected. The well-balanced ratio between switching losses and conduction loss can be found in the “sweet spot” of Figure 11.

Symmetric Dual Power56 Package

Because the telecommunication brick DC-DC module size is standardized and limited, the MOSFET package plays a critical role in power density. The symmetric dual N-channel Power56 package contains two identical dies for high-side and low-side MOSFETs for the half-bridge’s primary side switch, replacing two separate Power56 MOSFETs. The Power56 symmetric dual package occupies only half the footprint compared with two separate single packages. Therefore, it increases power density for half-bridge DC-DC converters.

 

Notes:
1. $R_{\theta JA}$ is determined with the device mounted on a 1 in² pad 2 oz copper pad on a 1.5 x 1.5 in. board of FR-4 material. $R_{\theta JC}$ is guaranteed by design while $R_{\theta JA}$ is determined by the user's board design.

Figure 12. Symmetric Dual Power 5x6 Package

Section III

FDMS8090 Performance in Quarter Brick DC-DC Converter

The FDMS8090 offers a well-balanced $R_{DS(ON)}$ and Q_g combination for the primary switch of the half-bridge DC-DC converter. and the thermally enhanced symmetric dual Power56 package saves PCB space. Table 4 shows the electrical characteristics of FDMS8090.

Table 4. FDMS8090 Electrical Characteristics

Package	MOSFET	BV_{DSS} (V)	$R_{DS(ON)}$ [mΩ]@ 10V _{gs}	Q_g [nC]@ 10V _{gs}	Q_{gd} [nC]
			Typ.	Typ.	Typ.
Power 5x6 Symmetric Dual N-ch	Q1	100	11	19	4.1
	Q2	100	11	19	4.1

The performance of FDMS8090 is tested on the 100 W quarter brick DC-DC converter specified in the Table 2. Figure 13 and Figure 14 show the total efficiency and thermal performance, respectively.

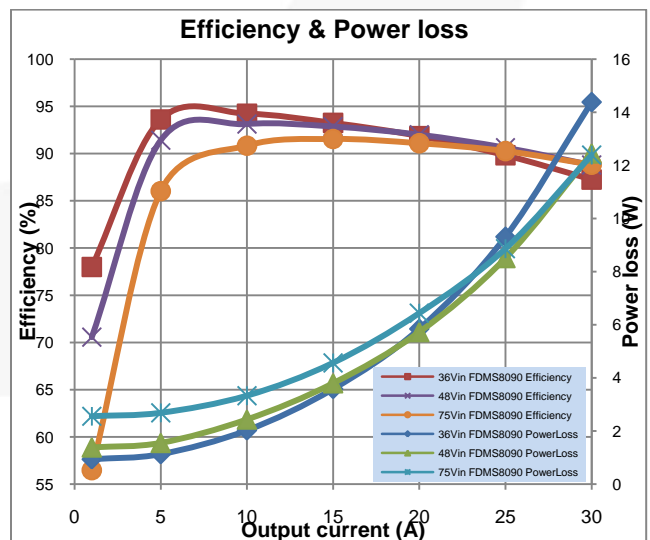


Figure 13. Efficiency and Power Loss at $V_{IN}=36 \sim 75\text{ V}$, $V_{OUT}=3.3\text{ V}$, $f_{SW}=200\text{ KHz}$, $T_A=25^\circ\text{C}$, Natural Convention

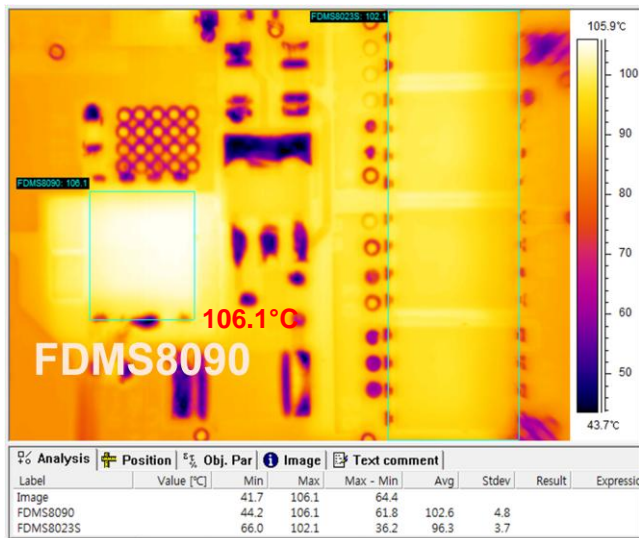


Figure 14. Thermal Performance at $V_{IN}=48$ V, $V_{OUT}=3.3$ V, $I_{OUT}=30$ A, $f_{SW}=200$ KHz, $T_A=25^\circ\text{C}$ and Natural Convection

Telecommunication brick DC-DC converters require the wide input voltage from 36 V to 75 V, so selecting a well-balanced $R_{DS(ON)}$ and Q_g MOSFET is the critical design step. The maximum load efficiencies of the FDMS8090, with input voltages 36 V, 48 V, and 75 V are 87.25%, 88.78%, and 88.82%, respectively.

Conclusion

It is essential that telecommunication brick DC-DC converters have higher efficiency and more power density. Shielded-gate PowerTrench[®] MOSFETs, such as the FDMS8090 with its well-balanced $R_{DS(ON)}$ and Q_g in the symmetric dual N-channel Power56 package, are able to improve the efficiency and power density of half-bridge DC-DC converter in the limited size.

Authors

SungJin Kuen - Applications Engineer (Sungjin.Kuen@fairchildsemi.com)

Dongsup Eom - Applications Engineer (Dongsup.Eom@fairchildsemi.com)

References

[1] SungJin Kuen, Dongsup Eom, Joe Yedinak; "Mid-Voltage Shielded PowerTrench[®] MOSFET in High Step-Up DC-DC for Edge-Lit LED TV Backlighting" Fairchild Application Note AN-9763.

Related Resources

[FDMS8090 — PowerTrench[®] Power Stage 100 V Symmetric Dual N-Channel MOSFET: 100 V, 10 A, 13 mΩ N-Channel](#)
[AN-9763 — Mid-Voltage Shielded PowerTrench[®] MOSFET in High Step-Up DC-DC for Edge-Lit LED TV Backlighting](#)

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative