



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.


## Designing with Bushold

### What is Bushold?

The bushold feature is an innovative approach to solving the problem of floating inputs. This circuitry maintains a valid logic state on an unloaded input and eliminates the need for external conditioning components for floating or undriven inputs.

Bushold circuitry is designed to tolerate floating input conditions. If non-bushold devices were used, these floating input conditions would lead to increased leakage, oscillations, and compromises in system data integrity.


Another feature of bushold circuitry is the ability to hold an undriven data-bus line in a valid logic state. Through the bus, the bushold device can condition the other inputs on the bus.

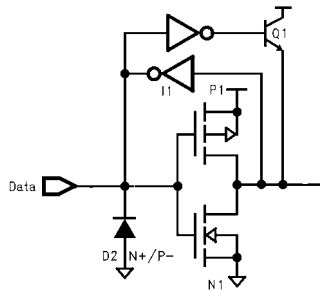

**FIGURE 1.**  
Simplified Schematic Diagram of Bushold Circuitry

### How Does It Work?

Bushold circuitry works by using a low drive inverter in the device input stage that provides feedback to the input of the device and the bus (see Figure 1). When the signal driving the input is removed, the inverter will maintain the last received valid signal level on the device input and bus line until it is overdriven by the next in-coming signal.

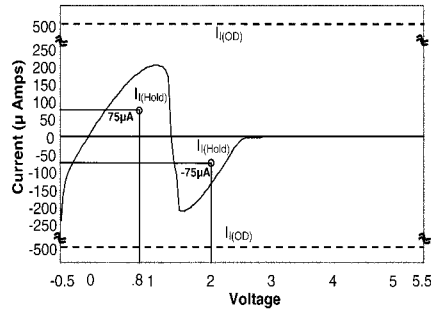

**FIGURE 2.** Voltage-In versus Current-In Sweep of CROSSVOLT LVT Device with Bushold (74LVTHxxx)

Fairchild Semiconductor provides two types of bushold inverter specifications (see Figure 2).  $I_{i(HOLD)}$  is the bushold input minimum drive. This is the minimum amount of current the circuit is capable of supplying.  $I_{i(OD)}$  is the bushold input over-drive current to change state. This is the minimum amount of current that is necessary to overcome the bushold circuit, and cause the input to change states (See Table 1).

**TABLE 1.** Bushold Specifications

| Family          | Symbol        | V <sub>CC</sub> (V) | Conditions       | Min  | Units   |
|-----------------|---------------|---------------------|------------------|------|---------|
| LVT<br>(Note 1) | $I_{i(HOLD)}$ | 3.0                 | $V_{IN} = 0.8V$  | 75   | $\mu A$ |
|                 |               | 3.0                 | $V_{IN} = 2.0V$  | -75  | $\mu A$ |
|                 | $I_{i(OD)}$   | 3.6                 | (Note 2)         | 500  | $\mu A$ |
|                 |               | 3.6                 | (Note 3)         | -500 | $\mu A$ |
| VCX<br>(Note 4) | $I_{i(HOLD)}$ | 3.0                 | $V_{IN} = 0.8V$  | 75   | $\mu A$ |
|                 |               | 3.0                 | $V_{IN} = 2.0V$  | -75  | $\mu A$ |
|                 |               | 2.3                 | $V_{IN} = 0.7V$  | 45   | $\mu A$ |
|                 |               | 2.3                 | $V_{IN} = 1.6V$  | -45  | $\mu A$ |
|                 |               | 1.65                | $V_{IN} = 0.57V$ | 25   | $\mu A$ |
|                 |               | 1.65                | $V_{IN} = 1.07V$ | -25  | $\mu A$ |
|                 |               | 3.6                 | (Note 2)         | 450  | $\mu A$ |
|                 |               | 3.6                 | (Note 3)         | -450 | $\mu A$ |
|                 |               | 2.7                 | (Note 2)         | 300  | $\mu A$ |
|                 |               | 2.7                 | (Note 3)         | -300 | $\mu A$ |
|                 |               | 1.95                | (Note 2)         | 200  | $\mu A$ |
|                 |               | 1.95                | (Note 3)         | -200 | $\mu A$ |

**Note 1:** Designated as 74LVTHxxx

**Note 2:** An external driver must source at least the specified current to switch from LOW-to-HIGH

**Note 3:** An external driver must sink at least the specified current to switch from HIGH-to-LOW

**Note 4:** Designated at 74VCXHxxx

CROSSVOLT™ is a trademark of Fairchild Semiconductor

### When is Bushold Used?

Devices with bushold are designed for use in systems where devices or data-bus lines will be left in an undriven condition. As noted, bushold circuitry will maintain a floating input or data-bus line in a valid state.

Non-bushold inputs must be maintained in a valid logic state. Leaving an input floating will allow it to oscillate and cause invalid data on the output. False data problems can lead to bus contention, high current draw, and device or system damage.

System data-buses must be maintained in a valid logic state for the same reasons that individual device inputs require conditioning.

Data integrity problems and device or system damage can occur if a bus is allowed to float. With a data-bus however, the number of device inputs on the bus multiplies the problem.

Fairchild's *CROSSVOLT* products with bushold work especially well on boards where spacing is tight. Here the bushold feature eliminates the need to have additional pads for conditioning resistors as well as added trace lines for ground or power.


By holding the device or bus at the last received valid logic high or low, devices with bushold can also serve a pseudo memory function. In contrast, a conditioning resistor will always pull the bus to the same state.

When designing a data-bus using devices with bushold, consideration must be given to the bushold drive and current requirements. With  $I_{(HOLD)}$  specified at  $\pm 75\mu A$ , a single device with bushold will hold a large data-bus, with power dissipation held at a low level. Calculations for the  $I_{IN}$  (Input current) of all device inputs on the bus must be taken into consideration.  $I_{IN}$  is typically in the range of  $1\mu A$  to  $5\mu A$  for CMOS devices.

With  $I_{(OD)}$  specified at  $\pm 500\mu A$ , the data-bus will still switch easily. CMOS devices typically have drives in the  $\pm 24mA$  range or greater.

### When Should Bushold Not Be Used?

There are design applications where bushold technology is either not appropriate or should not be overly used. In these designs, use of an equivalent performance device without bushold circuitry is recommended. Fairchild Semiconductor offers *CROSSVOLT* devices (see Figure 3) that have the same drive and AC specifications as the *CROSSVOLT* products with bushold, but without the bushold circuit on the inputs.

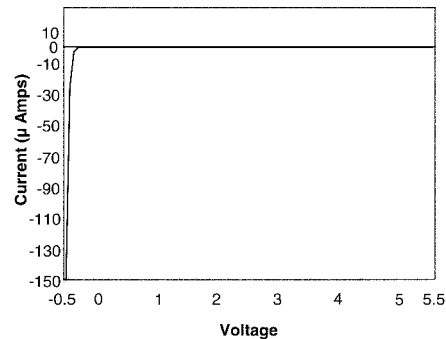

**FIGURE 3. Voltage-In versus Current-In Sweep of *CROSSVOLT* Device without Bushold**

Bushold circuitry on all system or data bus inputs can create problems. On a data-bus with multiple receiver drops, bushold circuitry should be used on the minimum number of devices that are needed to hold the data-bus in a valid state. The  $I_{(OD)}$  specification is additive for every bushold circuit on the data-bus. For example, using LVT with an  $I_{(OD)}$  specification of  $\pm 500\mu A$ , if 10 inputs on a data-bus have bushold circuitry, it will take at least 5mA to overcome and switch the data-bus. Using LVT with an  $I_{(HOLD)}$  specification of  $\pm 75\mu A$ , 750 $\mu A$  of drive will be available to hold this theoretical 10-input bus. This much drive is not required on an all-CMOS-input bus, and unnecessarily adds to the power budget needed for the system.

The bushold circuit is designed for use in place of conditioning pull-up or pull-down resistors. Using bushold inputs in conjunction with conditioning resistors can cause high power dissipation. If the load of the conditioning resistors and bushold inputs is high enough, the driver may not be able to switch the load in the required time.

Although not recommended, there are instances when systems with bushold use input conditioning resistors.

An example of this is when a device with bushold may be powered down, but the bus still needs to be held in a valid state, a 50 k $\Omega$  or greater value is recommended here. This will allow the bushold circuit to operate correctly when powered up, with a minimum of extra power dissipation. See appendix A for a formulaic explanation.

On a system data-bus with Thevenin or parallel termination designs, power and speed requirements must be accurately calculated if bushold inputs are to be used. Otherwise, the same high power dissipation and switching problems experienced using bushold with conditioning resistors may be seen.

Mixed-voltage buses may also experience problems if devices with bushold are not used appropriately. A device with bushold cannot pull a bus higher than its own  $V_{CC}$ . Allowing a bus to hold at a 3-volt level with 5-volt device inputs on the bus will cause significant levels of  $\Delta I_{CC}$  and  $I_{CCT}$  due to the 5-volt inputs being held partially on.

In point-to-point data flow designs (e.g., one data output to one data input) bushold is unnecessary if the driver will not be 3-stated or disconnected from the receiver.

**Summary**

Fairchild Semiconductor's *CROSSVOLT* low-voltage logic products with the bushold feature eliminate the need for external components to place undriven inputs into a valid logic state. This allows a device or data-bus to tolerate floating input conditions that would otherwise lead to increased leakage, oscillations, and compromises in system data integrity if a non-bushold device were used.

The bushold circuit works by using an inverter in the device input stage that provides feedback to the input of the device and the bus. When the input driver signal is

removed, the bushold circuit will maintain the last received valid signal level on the device input and bus line until it is overdriven by the next in-coming signal.

Bushold is designed for systems where device inputs or data-bus lines may be left floating, and should be used in place of conditioning resistors. The system may experience high power dissipation and timing problems if used in addition to conditioning components rather than in place of them. This can also be a problem when using Thevenin and parallel termination designs, or on voltage interface buses.

**Appendix A:**

Current calculations for a bushold input conditioning resistor (LVT is used in this example).

**For a pull-up resistor:**

$$V_{CC} = 3.0V$$

$$V_{IN} = 2.0 V \text{ (0.8V is the } I_{HOLD} \text{ 75}\mu\text{A specification)}$$

$$(3.0V - 0.8V) / 0.000075A = 29 K\Omega$$

29K = (Maximum on-resistance)

Choosing a value of 50K,

$$[(3.0V - 0.8V)/50K] = 44\mu A$$

Thus, 50K reduces the minimum bushold low current from 75 $\mu$ A to (75 $\mu$ A – 44 $\mu$ A) or 31  $\mu$ A.

**For a pull-down resistor:**

$$V_{CC} = 3.0V$$

$$V_{IN} = 2.0 V \text{ (2.0V is the } I_{HOLD} \text{ – 75}\mu\text{A specification)}$$

$$2.0V / 0.000075A = 26.7 K\Omega$$

26.7K = (Maximum on-resistance)

Choosing a value of 50K,

$$2.0/50K = 40\mu A$$

Thus, 50K reduces the minimum bushold low current from 75 $\mu$ A to (75 $\mu$ A – 40 $\mu$ A) or 35  $\mu$ A.

Fairchild does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and Fairchild reserves the right at any time without notice to change said circuitry and specifications.

**LIFE SUPPORT POLICY**

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

[www.fairchildsemi.com](http://www.fairchildsemi.com)

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative