


Welcome to this presentation on Switch Mode Drivers, part of OSRAM Opto Semiconductors' LED Fundamentals series.

In this presentation we will look at:

How switch mode drivers work, switch mode driver topologies, and benefits of switch mode drivers in LED circuits and systems.

Introduction

- Proper driving of LEDs is required to address some of the fundamental variations that all LEDs may have due to manufacturing tolerances.
- There are different methods that are used to drive LEDs. These methods can be very simple or quite complicated, depending on the application.
- Some of the key parameters needed to choose a proper driver include, expected T_j (Junction Temperature), expected V_f mismatch between LEDs, color accuracy needed at the system level, and if dimming of the LEDs is required.

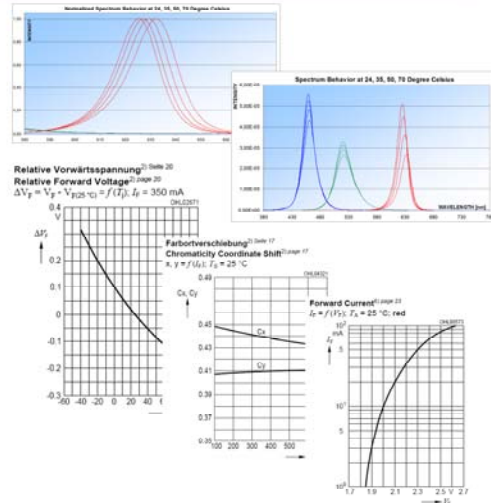

LED Fundamentals | Switch Mode Drivers | Page 2

OSRAM
Opto Semiconductors

Like any electronic component, LEDs should also be driven properly for improved efficacy, better reliability, and longer lifetime. Because some of the fundamental variations, such as v_f mismatch between LEDs and color variation within the same bin, more care needs to be taken when deciding what type of driving method is suitable for LEDs in a particular application.


Some of the key parameters that play a major role in selecting the proper driving method are expected junction temperature of the LED, expected V_f mismatch between LEDs and/or LED strings, color accuracy required, and whether dimming is required.

Need for Current Regulation in LED Systems

- The I-V characteristics of an LED plays a key role in deciding what type of regulation, current or voltage, is best suited for driving LEDs.
- Also, current regulation is required in the LED system to control and maintain:
 - » Color shift vs LED current
 - » Flux or light output vs LED current
- There are three common methods of driving LEDs: resistor based, linear regulators, and switch mode regulators.

Forward Current⁶⁾ page 23

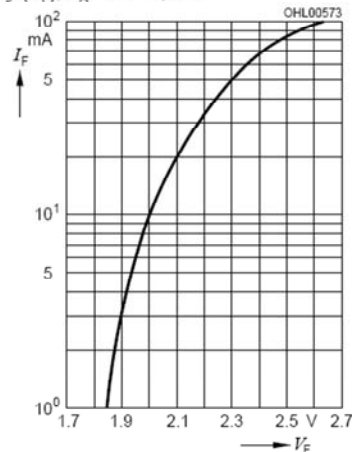
$I_F = f(V_F)$; $T_A = 25^\circ\text{C}$; red



LED Fundamentals | Switch Mode Drivers | Page 3


OSRAM
Opto Semiconductors

As mentioned earlier, understanding the electrical, optical, and thermal characteristics of an LED is required to properly select the driving method for an LED circuit or system. An I-V characteristic of an LED is similar to that of a standard diode, meaning LEDs should be driven with a constant current source. Also, optical characteristics such as color shift vs LED current and thermal characteristics such as V_f and color shift vs junction temperature, play key roles in selecting the proper driving method.

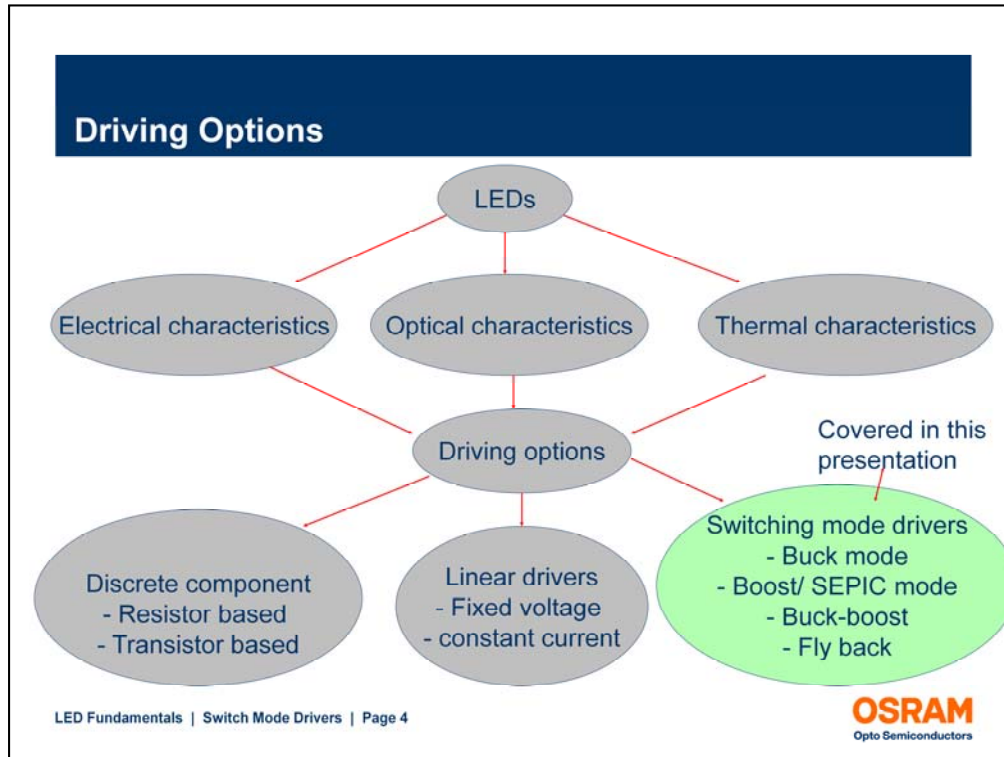

When selecting the proper driving method for an LED application, only considering electrical characteristics of an LED is not sufficient. Electrical, optical, and thermal characteristics should be considered to select the appropriate driving method for an LED system. There are three typical methods for driving LEDs.

Commonly Used Driving Options

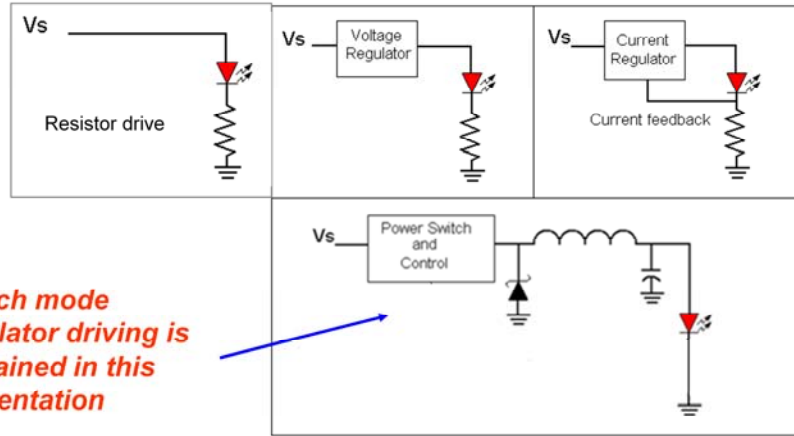

Commonly used driving options are: discrete component based drive, linear driver based drive, and switch mode driver based drive. This presentation covers switch mode driver based drive.

Advantages and Disadvantages of Each Driving Method

Before choosing a switch mode driver, refer to this table that outlines some of the advantages and disadvantages of each driving option.

	Discrete based drive Resistor/ Transistor	Linear Regulator	Switch Mode Regulator
Vf mismatch between LEDs addressed	NO/ YES	YES	YES
Vf change due to temperature addressed	NO/ YES	YES	YES
Source voltage variation addressed	NO/ YES	YES	YES
Tight current regulation	NO/ NO	YES	YES
Simple solution	YES/ YES	YES	NO
Costly solution	NO/ NO	YES (compared to resistor driver)	YES
Efficient solution	NO/ NO	NO	YES
Stable over wide-range of temperature	NO/ YES	YES	YES

LED Fundamentals | Switch Mode Drivers | Page 6

OSRAM
Opto Semiconductors

Before starting with a switch mode regulator, please take a look at the table on this slide to understand the advantages and disadvantages of each driving option. The biggest advantages of a discrete based drive are low cost and simplicity, where the major disadvantages of a switch mode based driver is the complexity of the design and the cost associated with it.


Switch Mode Regulators/Drivers

Switch mode regulators offer the advantage of increased efficiencies of power conversion, especially in high power applications.

In comparison to linear regulators, switch mode regulators may increase complexity, cost, and real estate needed for the driver circuit.

In this presentation, various topics of switch mode regulators will be examined at a very high level. This presentation is an overview of various key topics for switch mode regulators. A much more detailed look and analysis is required in an actual design.

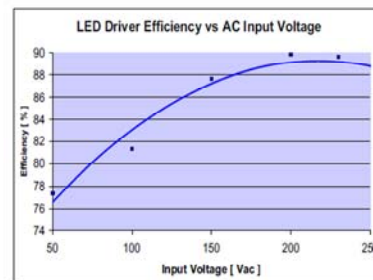Up to 90% efficiency can be achieved using switching drivers.



Efficiency characteristics of ICL8001G

Infineon

OSRAM
Opto Semiconductors


LED Fundamentals | Switch Mode Drivers | Page 7

At present, when it comes to LED systems, efficacy (lm/W) is one of the key measures that make LED systems more attractive compared to traditional lighting systems. The efficacy of an LED system can be improved by optimizing electrical, thermal, and optical efficiencies of the overall system.

This presentation reviews how an optimized driver can be used to help improve the electrical efficiency of an LED system.

Switch mode regulators offer the advantage of more efficient power conversion, especially in high power applications.

How Do Switch Mode Regulators Work?

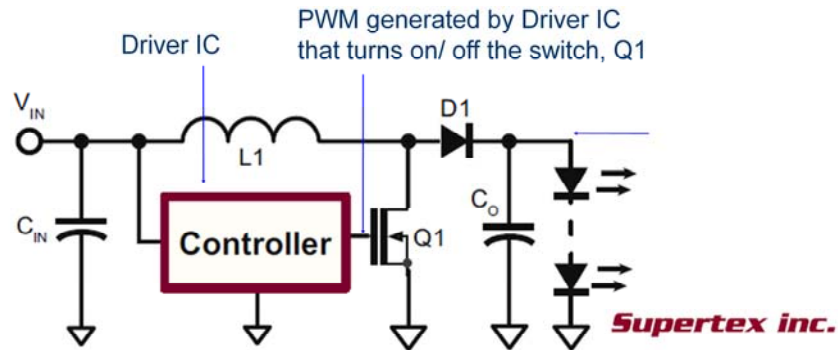

In linear regulators, the difference between the input and output voltages is burned as wasted heat. The wider the difference between the input and output voltage, the more heat is produced. With linear regulators, there are cases in which more energy is wasted as heat than delivered to the load.


LED Fundamentals | Switch Mode Drivers | Page 8

OSRAM
Opto Semiconductors


A switch mode regulator takes a small portion of energy at a time from the input voltage source and transfers it to the load or device being driven. An electrical switch, such as a transistor, is used along with a controller that regulates the rate at which the switch is turned on and off. In a switch mode driver, the driver IC is the brain of the power supply. Basically, it generates the PWM signal that turns the switch on and off so the output is maintained at a specified value.

Switch Mode Driver Topologies

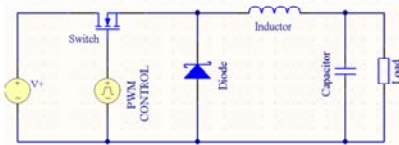
There are four main switch mode driver topologies that are commonly used in LED systems, depending on application.




Buck

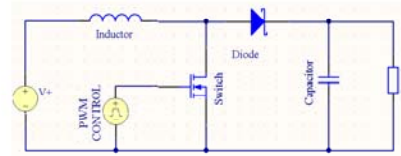

Boost

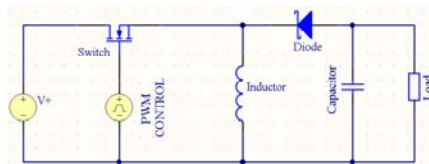

Buck-Boost

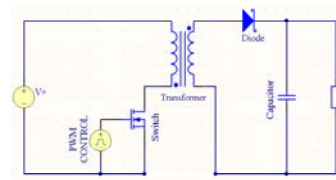

Fly-back


LED Fundamentals | Switch Mode Drivers | Page 9

OSRAM
Opto Semiconductors


There are four different topologies in which a switch mode driver can be operated. They are buck mode, boost mode, buck-boost mode, and fly back mode.

Next we will analyze each topology in greater detail.

Buck Mode Operation

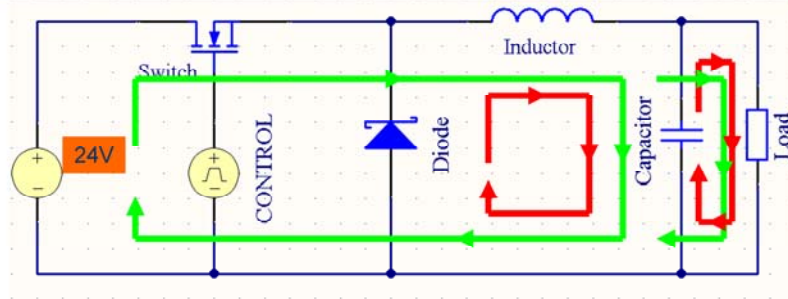

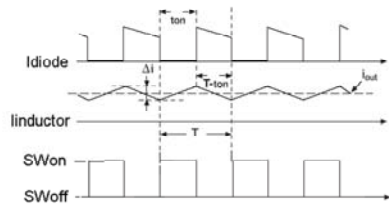Buck mode regulation is used when the input voltage or source voltage is higher than the expected output voltage.



LED Fundamentals | Switch Mode Drivers | Page 10


OSRAM
Opto Semiconductors

This example illustrates the simple circuit diagram of a buck type switch mode regulator design. The primary function of the driver IC is to generate the control signal which turns the switch on and off. When the switch is closed, there will be two current loops (shown in green). When the switch is open, current flows in the direction (shown in red).

Buck mode regulation is used when the input voltage or source voltage is higher than the expected output voltage. For instance, if a standard 24V supply is used to drive an LED system in which four 1W high power LEDs are connected in series, there needs to be a buck mode constant current driver in place to drive the LEDs.

Typical Application Circuit of HV9910B in Buck Configuration

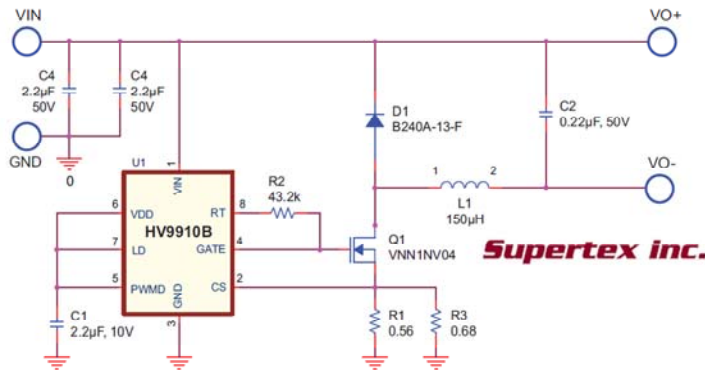This driver outputs an LED current of 700mA and can achieve up to 94% efficiency when driving OSRAM Opto Semiconductors' 6-chip OSRAM OSTAR LED with an input of 24Vdc.




LED Fundamentals | Switch Mode Drivers | Page 11

OSRAM
Opto Semiconductors


There are a number of IC manufacturers that focus on LED drivers. The brain of a power supply is the driver IC.

Shown on the right, is the schematic of a typical application circuit using Supertex's HV9910B, a buck driver IC. In many cases, the same driver IC can be configured to be operated in buck, boost, or Single Ended Primary Inductance Converter (SEPIC) configurations. The arrangement of the components is what changes in these different configurations. The basic components for all modes stay the same.

Boost Mode Operation

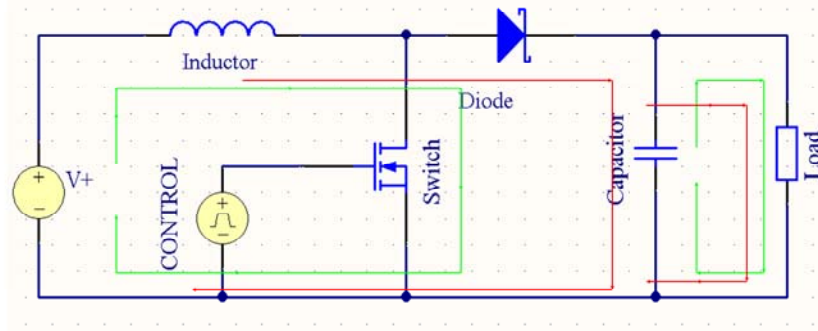

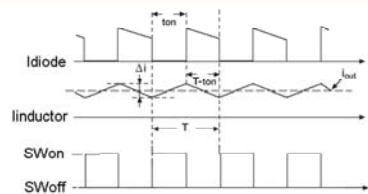The boost configuration is used when output voltage is expected to be higher than the input voltage.




LED Fundamentals | Switch Mode Drivers | Page 12

OSRAM
Opto Semiconductors

The boost topology is the second most commonly used configuration. In boost mode operation, when the switch is closed, current flows through the inductor while the capacitor supplies the load. When the switch opens, stored energy in the inductor releases, the capacitor charges, and the load is supplied.

Typical Application Circuit of Boost Configuration

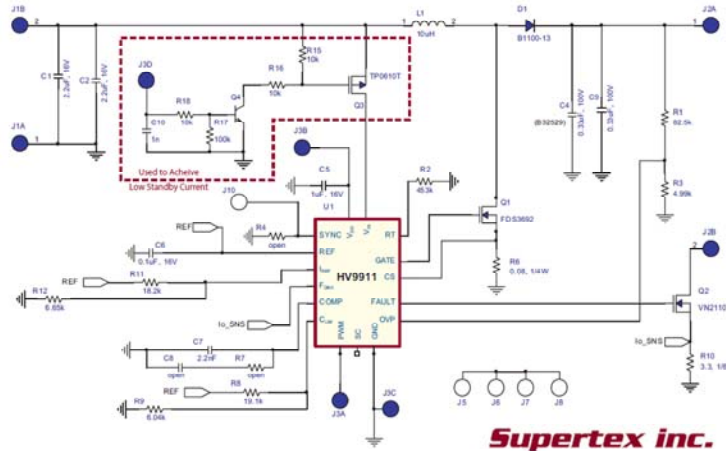As an example circuit, Supertex's HV9911 in boost mode is shown here.



LED Fundamentals | Switch Mode Drivers | Page 13

Supertex inc.

OSRAM
Opto Semiconductors


Shown here is a simple boost topology schematic using a Supertex's HV9911. Please note that the circuit enclosed in dotted lines is not part of the boost topology.

Shortcoming of Boost Mode Operation

In a boost topology, the input is less than the output. However, what will happen if the input goes above the output?

Due to circuit arrangement in a boost topology, there will be current flow (shown in red) when input goes higher than the output and the output will not be regulated. This may cause damage to the load and should be prevented.

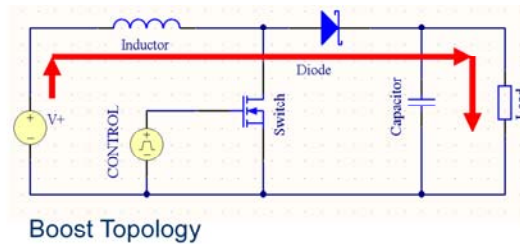
In a situation similar to the above, the SEPIC configuration helps and maintains a regulated positive output when the input is higher or lower than the output.



Ideally, boost topology is used when input voltage is lower than the output voltage. However, due to the circuit component arrangement in boost topology, there will be a direct current flow into the load when the input goes above the output voltage. This is not desired, as there will be no current regulation in this situation.

SEPIC Configuration

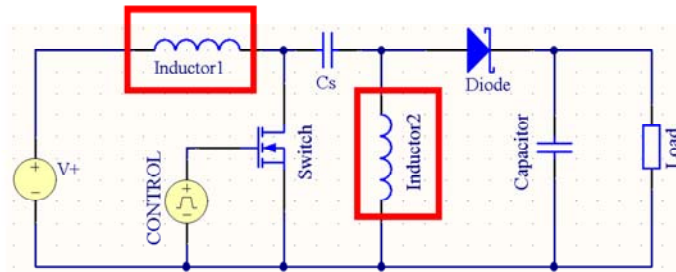In SEPIC (Single Ended Primary Inductance Converter) configuration, the output voltage can be either higher or lower than the input voltage.




To address this loop hole in boost configuration, SEPIC configuration is used. In a SEPIC configuration, the input voltage can either be higher or lower than the output voltage. Please note that there are two inductors in this configuration compared to only one inductor on the three previously explained modes. The addition of the inductor may slightly increase the cost of the driver.

Typical Circuit Schematics of SEPIC Configuration

Shown below is Supertex's HV9911 in SEPIC configuration.

Note use of two inductors

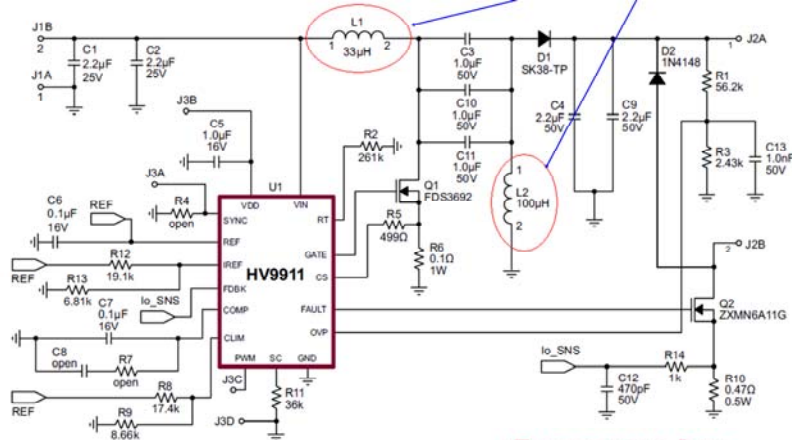

LED Fundamentals | Switch Mode Drivers | Page 16

Supertex inc.

OSRAM
Opto Semiconductors

One of the key differences between boost and SEPIC is the use of two inductors, which may add cost to the system, but is very commonly used in portable battery operated applications.

SEPIC in battery operated applications




LED Fundamentals | Switch Mode Drivers | Page 17


OSRAM
Opto Semiconductors

An ideal example for SEPIC configuration would be a device which has a single LED ($V_f \sim 3.2V$) and is operated with three AA or AAA batteries. When the batteries are new, a buck mode operation is required and when the batteries drain below 3.0V a boost mode operation is required.

Buck-Boost Mode of Operation

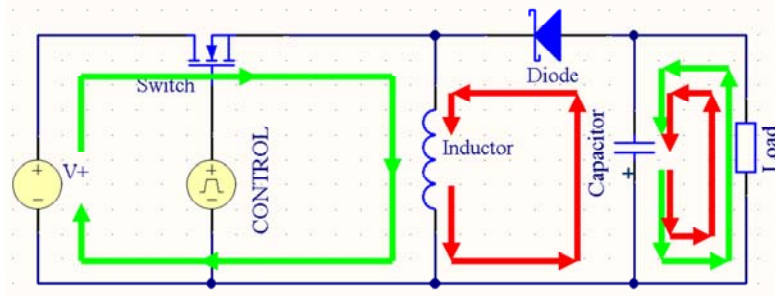

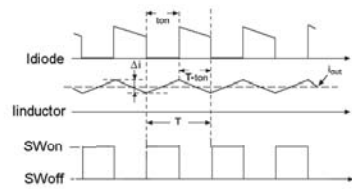In the buck-boost configuration, the output voltage can be higher or lower than the input. However, the output is inverted, due to its configuration and the way it operates.




LED Fundamentals | Switch Mode Drivers | Page 18

OSRAM
Opto Semiconductors

Buck-boost is the third commonly used topology. It is also called inverter topology because the output polarity is inverted. The operation is such that when the switch is on, current flows through the inductor and energy is stored in the inductor. During this period, the load is supplied by the capacitor. When the switch opens, stored energy in the inductor is released and the capacitor charges up while the load is also supplied.

Typical Circuit Schematic of Buck-Boost Configuration

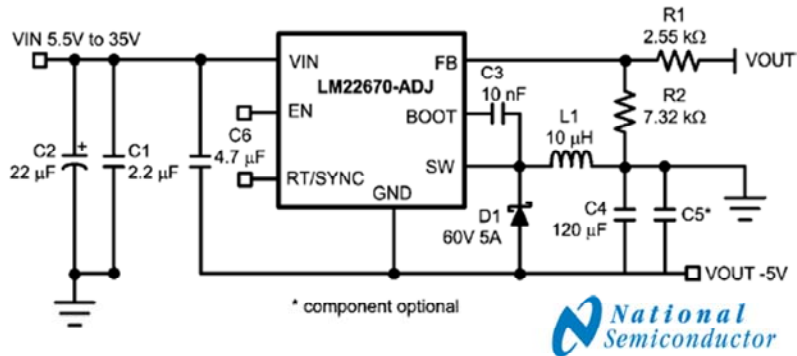
National Semiconductors' LM22670-ADJ in buck-boost configuration is shown below. Note here the polarity of the output is inverted.



As an example, a National Semiconductor's LM22670-ADJ in buck-boost mode operation is shown.

Fly Back Topology

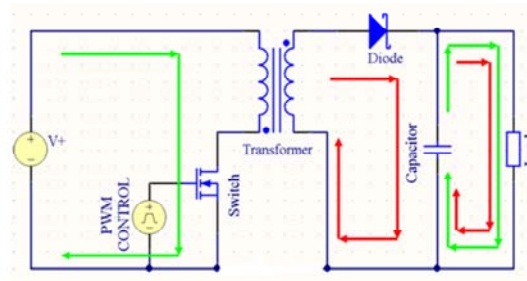
Fly back topology is the most versatile because it can have single or multiple outputs. A single output configuration is shown below.



The fly back is the fourth commonly used topology. It can be configured for single output or multiple outputs. In single output configuration, when the switch is on, the current flows through the primary side of the transformer. During this cycle, the load is supplied by the capacitor. When the switch is turned off, the voltage at the primary side is reflected on the secondary side, which causes the diode to conduct, supplying the load as well as charging the capacitor.

Fly Back Topology

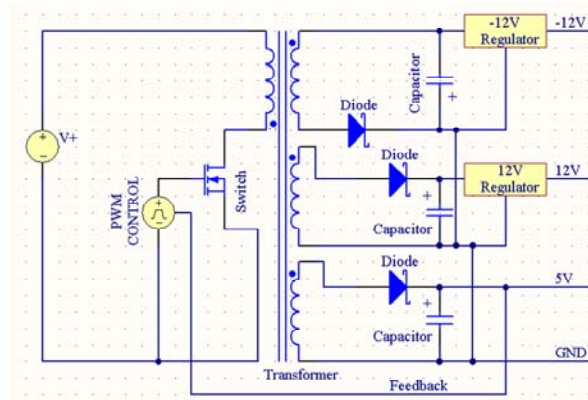A multiple output fly back topology is shown below. For more information on multiple output configuration, please consult LED Fundamental "AC-DC Power Supplies."



LED Fundamentals | Switch Mode Drivers | Page 21

OSRAM
Opto Semiconductors


This slide shows the typical configuration of a multiple output fly back topology. For more information on multiple output configuration, please consult the LED Fundamental "AC-DC Power Supplies."

Continuous and Discontinuous Conduction Modes (CCM/ DCM)


Irrespective of all different topologies explained, there are two conduction modes of operations at which any of the topologies can operate.

A continuous conduction mode is when the inductor current never reaches zero between on and off cycles of the switch, whereas in a discontinuous mode of operation the inductor current can reach zero.

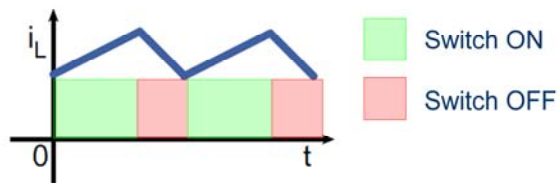There are advantages and disadvantages of each mode. For more information on each mode, please consult the LED Fundamental "AC-DC Power Supplies."



Inductor Current for CCM

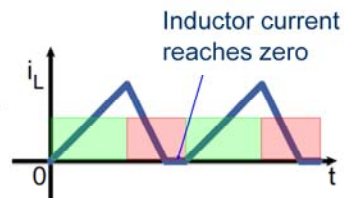

Inductor Current for DCM

LED Fundamentals | Switch Mode Drivers | Page 22

OSRAM
Opto Semiconductors

All four of the topologies explained can be operated in either continuous conduction mode or discontinuous conduction mode, depending on the current through the inductor. In continuous conduction mode, inductor current never reaches zero, but in a discontinuous conduction mode operation the inductor current does reach zero.

Summary

- There are four different switch mode driver topologies that are widely used:
Buck, Boost, Buck-Boost, and Fly back
- All of the topologies can be operated in Continuous or Discontinuous mode (CCM/DCM).
- SEPIC can be considered a variation of Boost configuration.
- Fly back topology gives the designer freedom in the design and is considered the most versatile.
- Switch mode drivers are much more efficient than discrete component based drivers or linear drivers.

In conclusion, there are four different switch mode driver topologies and the fly back topology is the most versatile and widely used because of the flexibility it offers. Irrespective of what topology is used, switch mode driver based current regulation is much more efficient than discrete or linear based regulation. On the negative side, switch mode drivers are more complex compared to a simple resistor or linear driver based designs and can also add costs to the overall system.

Disclaimer

All information contained in this document has been checked with the greatest care. OSRAM Opto Semiconductors GmbH can however, not be made liable for any damage that occurs in connection with the use of these contents.

OSRAM Opto Semiconductor GmbH makes no representations and warranties as to a possible interference with third parties' intellectual property rights in view of products originating from one of OSRAM Opto Semiconductor GmbH's partners, or in view of products being a combination of an OSRAM Opto Semiconductor GmbH's product and a product of one of OSRAM Opto Semiconductor GmbH's partners. Furthermore, OSRAM Opto Semiconductors GmbH cannot be made liable for any damage that occurs in connection with the use of a product of one of OSRAM Opto Semiconductor GmbH's partners, or with the use of a combination of an OSRAM Opto Semiconductor GmbH's product and a product of one of OSRAM Opto Semiconductor GmbH's partners.



Thank you for your attention.

Please refer to the LED Fundamental “**AC-DC Power Supplies**” on this website for additional information.

Thank you for viewing this presentation by OSRAM Opto Semiconductors.