


## Current Distribution in Parallel LED Strings

### Introduction

Many LED applications require more than one LED in a system. When multiple LEDs are used in a system, the LEDs can be arranged in series, parallel, or series-parallel configurations. Due to regulatory requirements (especially in Class II environments) there is always a limitation as to how many LEDs can be connected in series. One of the standard practices to overcome this issue is to have multiple parallel strings of series LEDs that are driven from a single constant current source. This Application Guide describes the issues and solutions that may be encountered when multiple strings are driven from a constant current source (CC source).


### Series- Parallel configuration

In series-parallel configuration, there are multiple strings of series LEDs. It is always better to limit the number of LEDs in series to minimize total  $V_f$  (threshold voltage) mismatch between strings. It is recommended to have 4 to 6 LEDs in a series so the difference in voltage between strings is not significant.

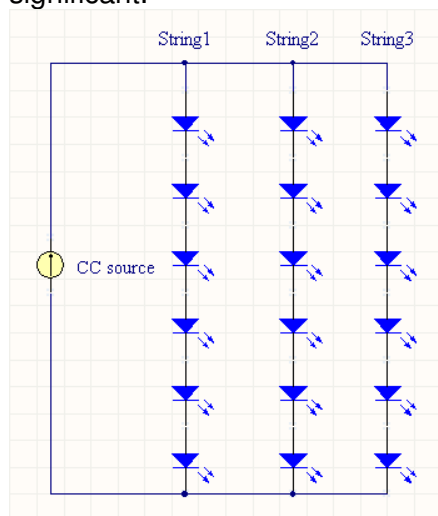

**Figure 1. Series-Parallel configuration**  
**Difference of  $V_f$  in LEDs**

In LEDs,  $V_f$  is the threshold voltage at which an LED starts to turn on. Due to manufacturing tolerances and material properties,  $V_f$  can vary between LEDs even if they are from the same wafer. Depending on the technology used, the range in difference can be a few millivolts to up to a volt. When multiple LEDs are connected in series, this  $V_f$  mismatch between LEDs adds up and becomes significant. In series-parallel configuration, if the string voltage is significantly different between strings, the current through each string will vary (become imbalanced) when a single constant current source is used. Figure 2 shows what the string currents would be if one of the strings has  $\sim 3V$  (caused by a shorted LED) less than the other two strings.

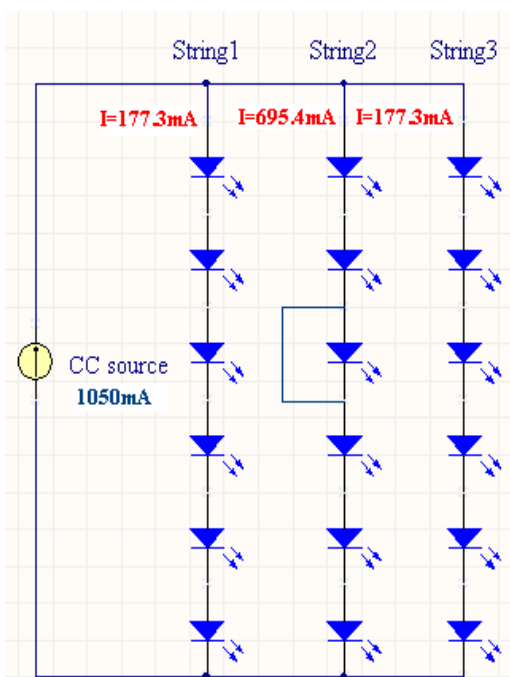

**Figure 2. String Voltage vs string current**

## Impacts of imbalanced string currents

If all of the strings in a series-parallel configuration don't have the same current going through them, there will be a number of issues that have to be dealt with during the design process. Imbalanced string current will result in lowering the overall system efficacy and this can be significant, depending on how wide the difference in string current is. It will also play a major role in LED lifetime and thermal management. Moreover, if the string current is considerably different between strings, the light output from each string would be different (Figure 3) and this difference will be visible to the naked eye. This is not desirable in a system with multiple LED strings. Displayed in Figure 3, the string with lower total  $V_f$ , due to a shorted LED, has lot more current going through it and a very small portion of the total current is split between the other two strings. Since Flux vs Current is not linear in LEDs (Figure 4), the system efficacy will be reduced when there is imbalanced string current. Also, note that the two strings with identical  $V_f$  have same current going through them. This can be witnessed by looking at the brightness of the LEDs in those two strings.

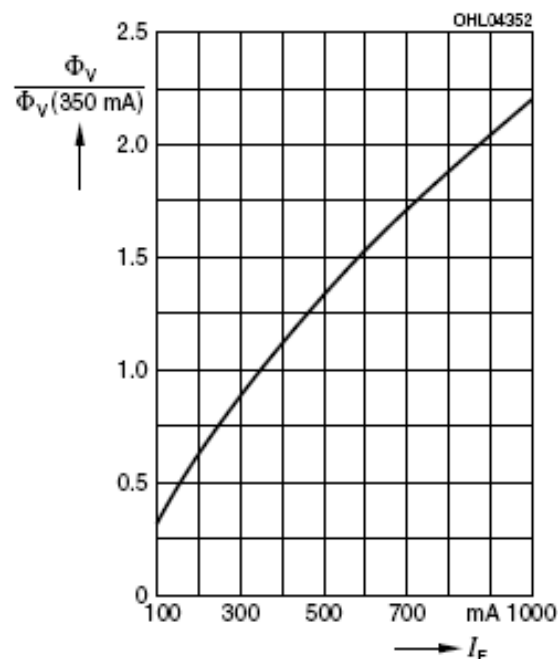


**Figure 3. Representation of Figure 2 in real application**

Relative Lichtstrom<sup>2)</sup> 5) Seite 18

Relative Luminous Flux<sup>2)</sup> 5) page 18

$\Phi_V / \Phi_V(350 \text{ mA}) = f(I_F); T_S = 25^\circ \text{C}$



**Figure 4. LED Current Vs Flux of OSLO LED**

## Impact on efficacy

With imbalanced string currents, and due to the fact that efficacy of an LED degrades with increasing current, the overall system efficacy of a system with multiple LED strings would be lower. Figure 5 shows the difference in efficacy with balanced and imbalanced string currents. In this example, OSLO LEDs from OSRAM Opto Semiconductors are used. The flux/light output from the OSLO LEDs at 350 mA is set to be 100 lm. The junction temperature of the LEDs are assumed to be room temperature to eliminate temperature dependency on flux and for ease of calculation. Circuit configuration for the example would be the same as in Figure 1. All the values used in the calculation are obtained from the datasheet that is available on

# Application Guide

the web site.

[http://catalog.osram-os.com/jsp/download.jsp?rootPath=/media/&name=LUW\\_CP7\\_P\\_Pb\\_free.pdf&docPath=Graphics/00052189\\_0.pdf&url=/media/en/Graphics/00052189\\_0.pdf](http://catalog.osram-os.com/jsp/download.jsp?rootPath=/media/&name=LUW_CP7_P_Pb_free.pdf&docPath=Graphics/00052189_0.pdf&url=/media/en/Graphics/00052189_0.pdf)

Also required for the calculation is the I-V curve (Figure 5) for OSLO LEDS.

Durchlassstrom<sup>2)</sup> Seite 18  
Forward Current<sup>2)</sup> page 18  
 $I_F = f(V_F); T_S = 25^\circ\text{C}$

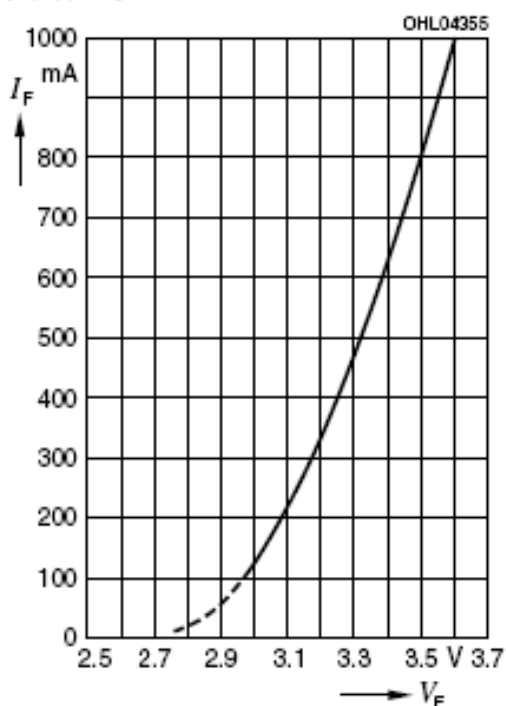


Figure 5. Current Vs Voltage of OSLO LED

With balanced LED strings, the total lumen would be:

$$18 \times 100 = 1800\text{lm}$$

(there are 18 LEDs in total and 100lm from each LED)

Total power in this case would be:

$$3.3 \times 0.35 \times 18 = 20.16\text{W}$$

(typical V<sub>f</sub> for Oslo is 3.2V)

The efficacy of the circuit without considering electrical, thermal, and optical losses would be:

$$1800\text{lm} / 20.16\text{W} = 89.3\text{lm/W}$$

With imbalanced current (per current distribution in Figure 2), the total lumen would be:

$$(1.75 \times 100 \times 6) + (0.54 \times 100 \times 12) = 1698\text{lm}$$

(as per Figure 4, flux at 695mA is ~1.75 times the flux at 350mA and flux at 177mA is ~0.54 times the flux at 350mA)

The total power in this case would be:

$$(0.177 \times 12 \times 3.05) + (0.695 \times 6 \times 3.45) = 20.86\text{W}$$

(per Figure 5, V<sub>f</sub> at 177mA is ~3.05V and V<sub>f</sub> at 695mA is ~3.45V)

The efficacy in this case would be:

$$1698\text{lm} / 20.86\text{W} = 81.38\text{lm/W}$$

One can easily see the difference of ~8lm/W between the two cases. The difference of 8lm/W is significant and should be taken into consideration during the design and development stages. It should be noted that the 8lm/W difference is due to the fact that the difference in string current, in this case, is significantly wider. If the difference in string current is narrower, then the loss of efficacy would be lower. The wider range string current is chosen in this example to easily explain the efficacy impact to the reader.


## How to solve the issue?

There are multiple ways to address this issue. One of them is to use individual constant current sources for each string. This solution is costly and adds more components to the driver circuitry. As a result of adding passive and active components, more failure modes are introduced and reliability of the driver is also impacted to a certain degree. In some cases, the space requirement may be a factor as this solution requires considerably more space for the driver and control circuitry. Another

# Application Guide


way to address this issue is to use a current mirror to match the string currents. This solution would be much less expensive compared to individual current sources and uses very few components. At minimum, each string would require only one transistor, put in a current mirror form, to match current between the strings. As with any other solutions, this also has some disadvantages. One of them is the reference current to the current mirror. The way it works in this case is that the reference current to the current mirror is set by one of the strings and current to the other strings are matched to the reference current. If the reference string has lower voltage compared to the other strings, then the current mirror will not work as expected. This can be solved by inserting a resistor in the reference string such that the reference string has slightly higher voltage compared to all other strings. The other issue is the dependency on the  $V_{be}$  (base to emitter voltage of a transistor) of each transistor in the current mirror circuit. This issue can be addressed by selecting reasonably matched  $V_{be}$  on the transistors. To reduce dependency on the  $V_{be}$ , a small value resistor can be inserted at the emitter. However, it will add cost and may not be required for the specific application that is being considered. The circuit in Figure 2 is simulated with current mirror in place and shows the current distribution in each string.

With the addition of the current mirror in place the string currents are now matched within 3-5% between strings. However, note that the reference string doesn't have the lowest total  $V_f$ . As mentioned before, you may run into issues when the reference string has lower total  $V_f$  compared to other strings, Figure 7 illustrates this situation.

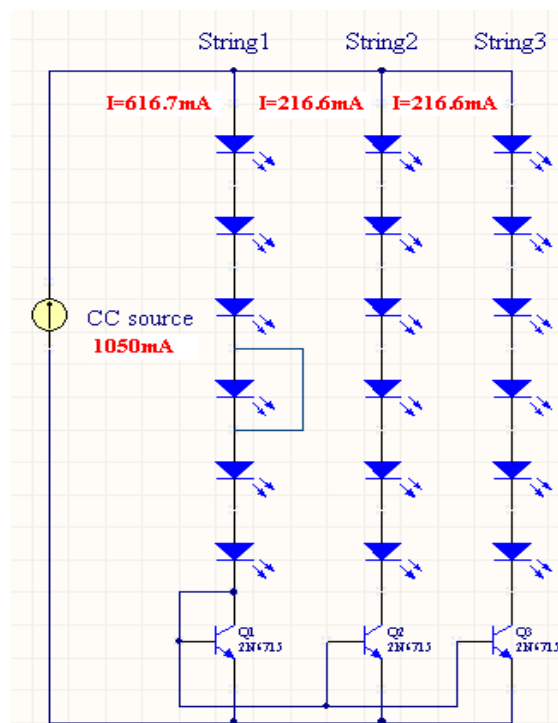

**Figure 6.** Current distribution with current mirror in place.


# Application Guide

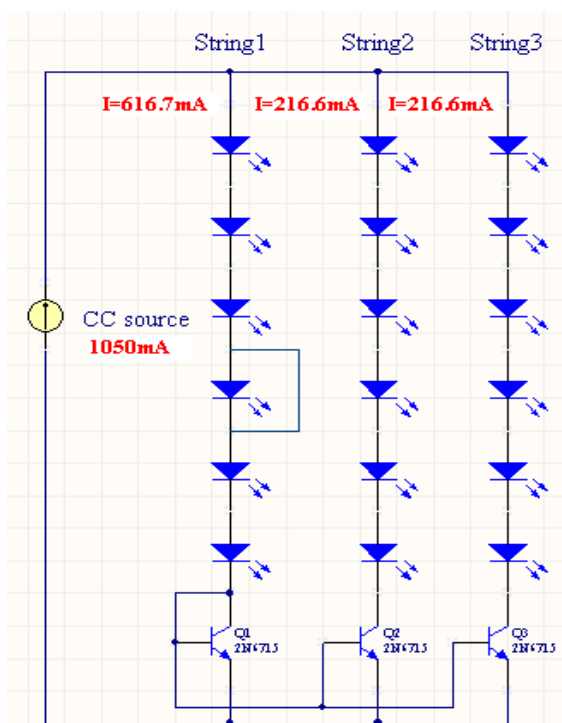

**Figure 7. Current distribution with current mirror (reference current string has lower voltage) in place.**

The current mirror doesn't do any good in this case, this is due to the fact that the reference string has lower voltage compared to the other two strings. To address this issue, a resistor can be inserted in the reference strings so that the reference string has slightly higher voltage compared to the other strings. There will be an efficacy loss due to the resistor depending on the value of the resistor, which is dictated by how wide the expected voltage difference between strings is and how well the string current needs to be matched. Figure 8 shows simulation results with the addition of a resistor in the reference string.

**Figure 8. Current distribution with current mirror**

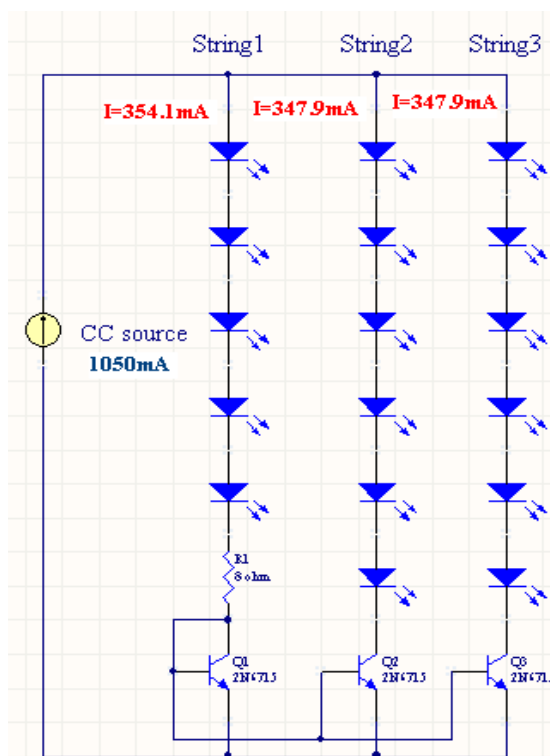

(with added resistor in the reference string) in place.

The addition of a resistor resolved the issue and the string currents are matched within 2% (Figure 9).



**Figure 9. Representation of Figure 8**

Even without any technical understanding, one can easily see how the current mirror improved the string currents, and therefore the light output from each string, by comparing Figure 3 and Figure 9. Below is a side-by-side view of the pictures for comparison purpose.



**Figure 10. Side-by-Side view (with and without current mirror circuit)**

## Things to remember when designing a current mirror

1. The transistors should be chosen such that  $V_{be}$  of all the transistors are reasonably matched.
2. Adding a very small resistor at the emitter pins of the transistors will also help to reduce  $V_{be}$  mismatch.
3. The selection of resistor should serve the purpose and minimize efficacy losses.
4. It is recommended to have all transistors operating at the same temperature to ensure or minimize variations due to thermal characteristics of transistors.
5. It is also possible to have one more transistor and shut off the reference string, if the current through the reference string exceeds a set value.

## Conclusion

A well designed current mirror in a series-parallel LED configuration can match the string currents to within 3% to 5%. Since the passives used in a current mirror are very minimal and inexpensive, the added cost is almost negligible. Furthermore, if designed properly, efficacy losses due to the added components are insignificant.



# Application Guide

**Author:** Muhinthan Murugesu, Applications Engineer

## About OSRAM Opto Semiconductors

OSRAM is part of the industry sector of Siemens and one of the two leading lighting manufacturers in the world. Its subsidiary, OSRAM Opto Semiconductors GmbH in Regensburg (Germany), offers its customers solutions based on semiconductor technology for lighting, sensor and visualization applications. OSRAM Opto Semiconductors has production sites in Regensburg (Germany) and Penang (Malaysia). Its headquarters for North America is in Sunnyvale (USA), and for Asia in Hong Kong. OSRAM Opto Semiconductors also has sales offices throughout the world. For more information go to **[www.osram-os.com](http://www.osram-os.com)**.

**All information contained in this document has been checked with the greatest care. OSRAM Opto Semiconductors GmbH can however, not be made liable for any damage that occurs in connection with the use of these contents.**

OSRAM Opto Semiconductor GmbH makes no representations and warranties as to a possible interference with third parties' intellectual property rights in view of products originating from one of OSRAM Opto Semiconductor GmbH's partners, or in view of products being a combination of an OSRAM Opto Semiconductor GmbH's product and a product of one of OSRAM Opto Semiconductor GmbH's partners. Furthermore, OSRAM Opto Semiconductors GmbH cannot be made liable for

any damage that occurs in connection with the use of a product of one of OSRAM Opto Semiconductor GmbH's partners, or with the use of a combination of an OSRAM Opto Semiconductor GmbH's product and a product of one of OSRAM Opto Semiconductor GmbH's partners.

## Disclaimer

This document constitutes neither an offer to sell nor a solicitation to buy or subscribe for securities. Any such offer will be made solely on the basis of the Securities Prospectus yet to be approved by the German Financial Supervisory Authority (BaFin) and published thereafter. The information legally required to be provided to investors will be contained only in the Securities Prospectus. The information contained herein is not for distribution, directly or indirectly, in or into the United States of America (including its territories and possessions of any State of the United States of America or the District of Columbia) and must not be distributed to U.S. persons (as defined in Regulation S under the U.S. Securities Act of 1933, as amended ("Securities Act")) or publications with a general circulation in the United States of America. This document is not an offer of securities for sale in the United States of America. The securities have not been and will not be registered under the Securities Act and may not be offered or sold in the United States of America absent registration or an exemption from registration under the Securities Act. The Issuer does not intend to register any portion of the offering in the United States of America or to conduct a public offering of the securities in the United States of America. This document is not an offer of securities for sale in the United Kingdom, Canada, Japan or Australia.