 


Digital Signal Processing



Analog-to-Digital Converter (ADC) converts an input analog value to an output digital representation.

This digital data is processed by a microprocessor and output to a Digital-to-Analog Converter (DAC) the converts an input binary value to an output voltage.


Applications

- Audio
 - Speech recognition
 - special effects (reverb, noise cancellation, etc)
- Video
 - Filtering
 - Special effects
 - Compression
- Data logging


Vocabulary

- ADC (Analog-to-Digital Converter) – converts an analog signal (voltage/current) to a digital code
- DAC (Digital-to-Analog Converter) – converts a digital code to an analog value (voltage/current)
- Sample period – for ADC, time between each conversion
 - Typically, samples are taken at a fixed rate
- Vref (Reference Voltage) – analog signal varies between 0 and Vref, or between +/- Vref
- Resolution – number of bits used for conversion (8 bits, 10 bits, 12 bits, 16 bits, etc).
- Conversion Time – the time it takes for an analog-to-digital conversion


An N-bit ADC

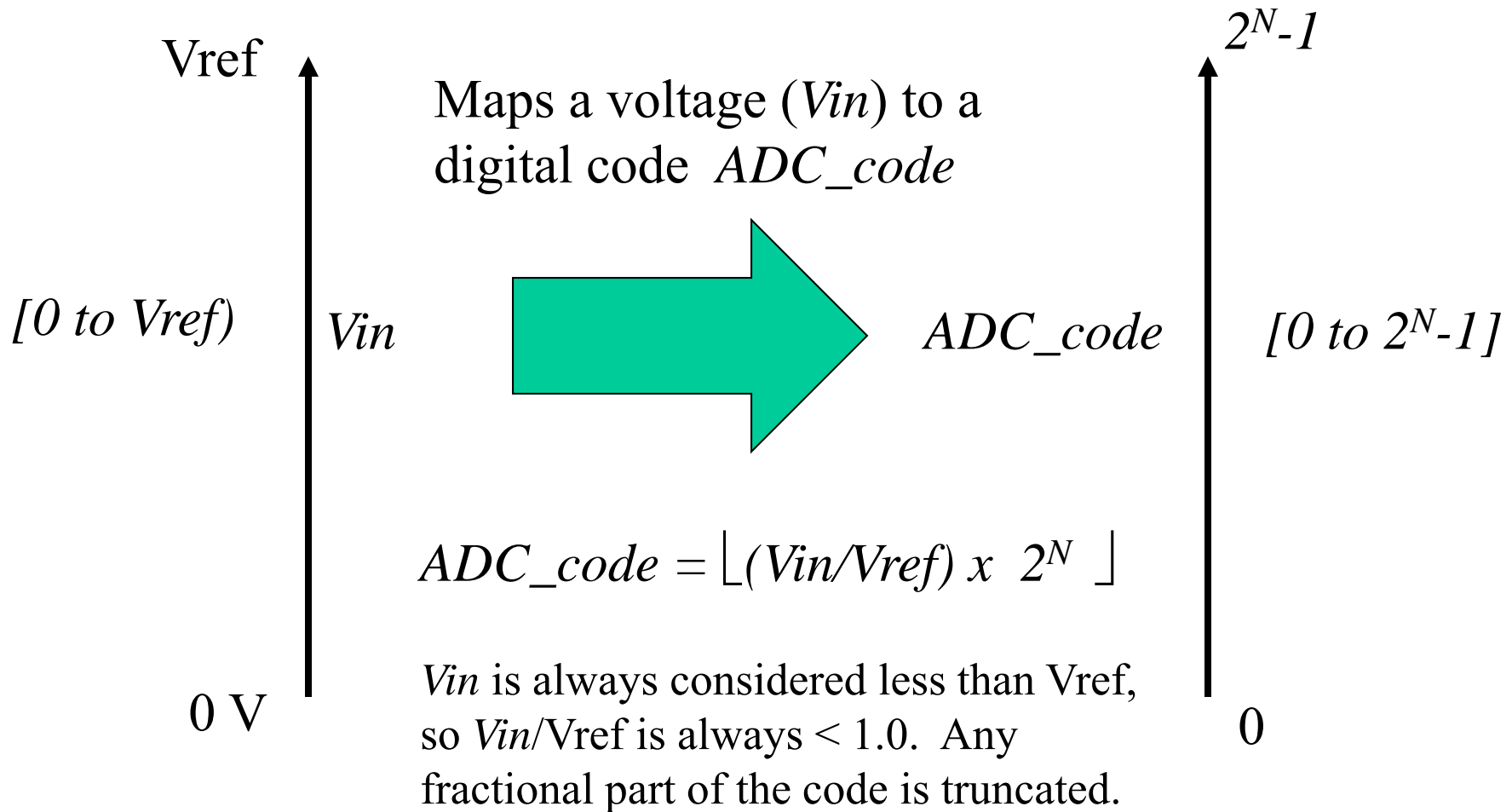


Example: A 10-bit ADC

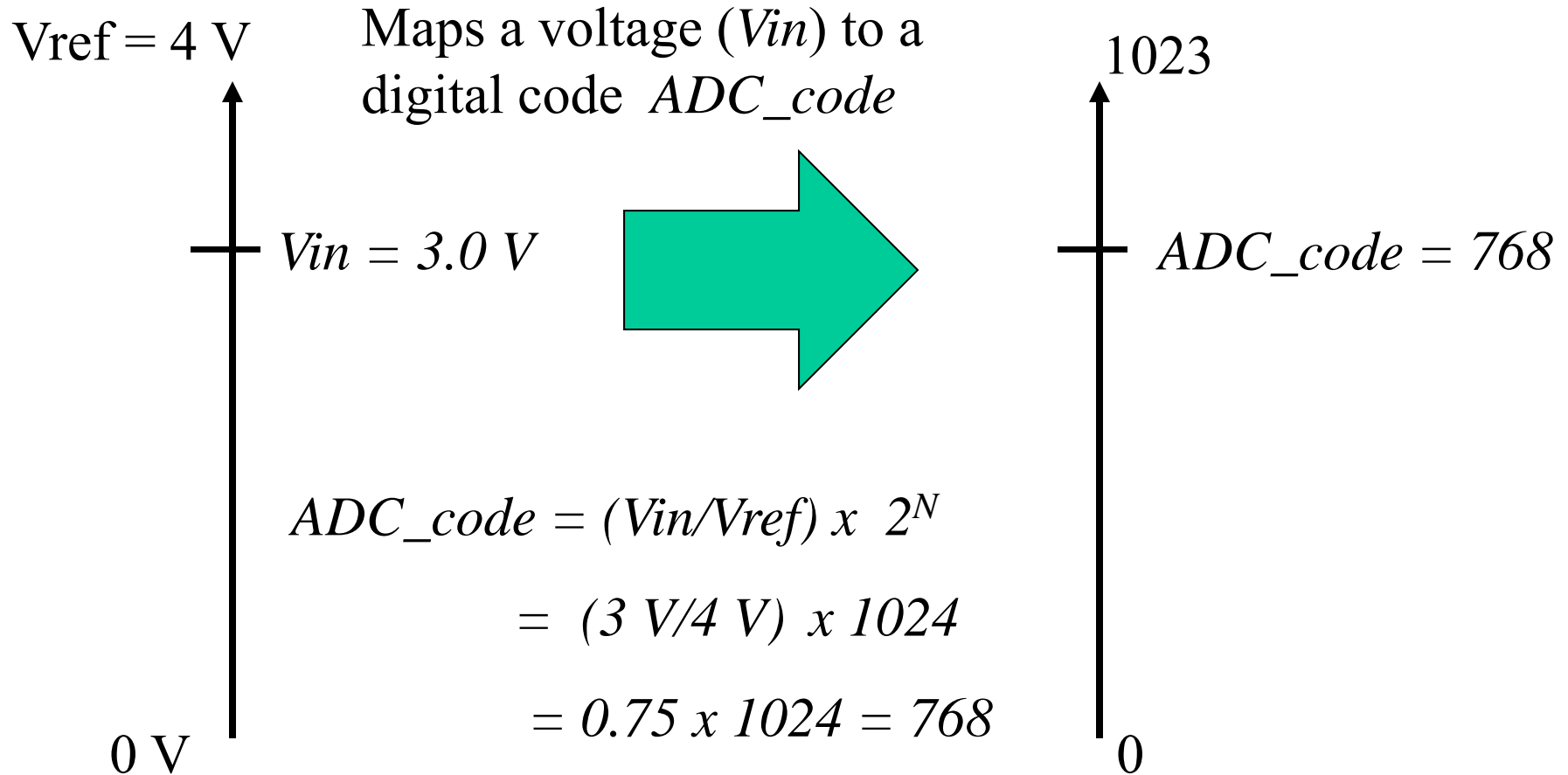


Example: A 10-bit ADC

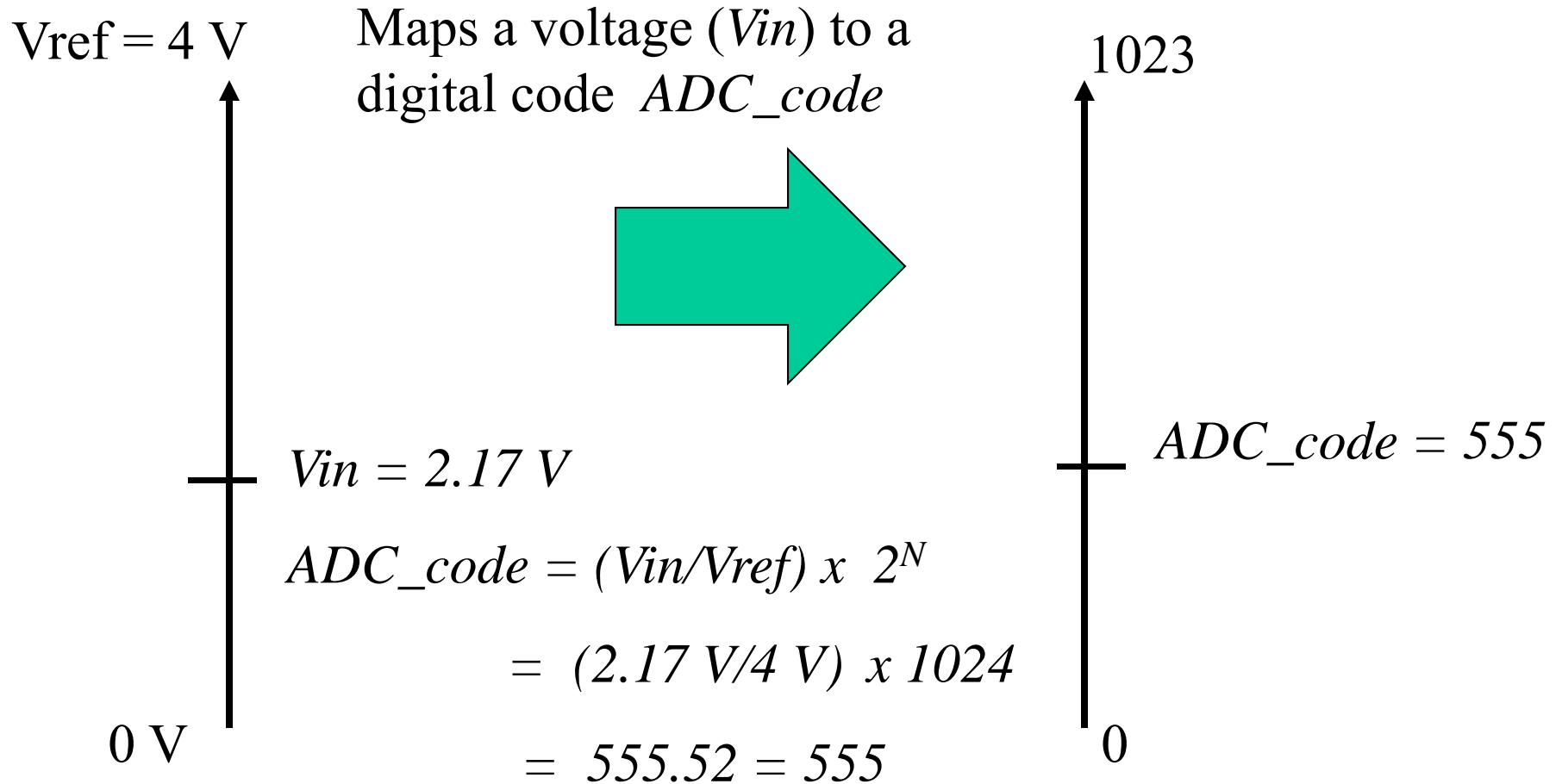

Going from Code to Voltage

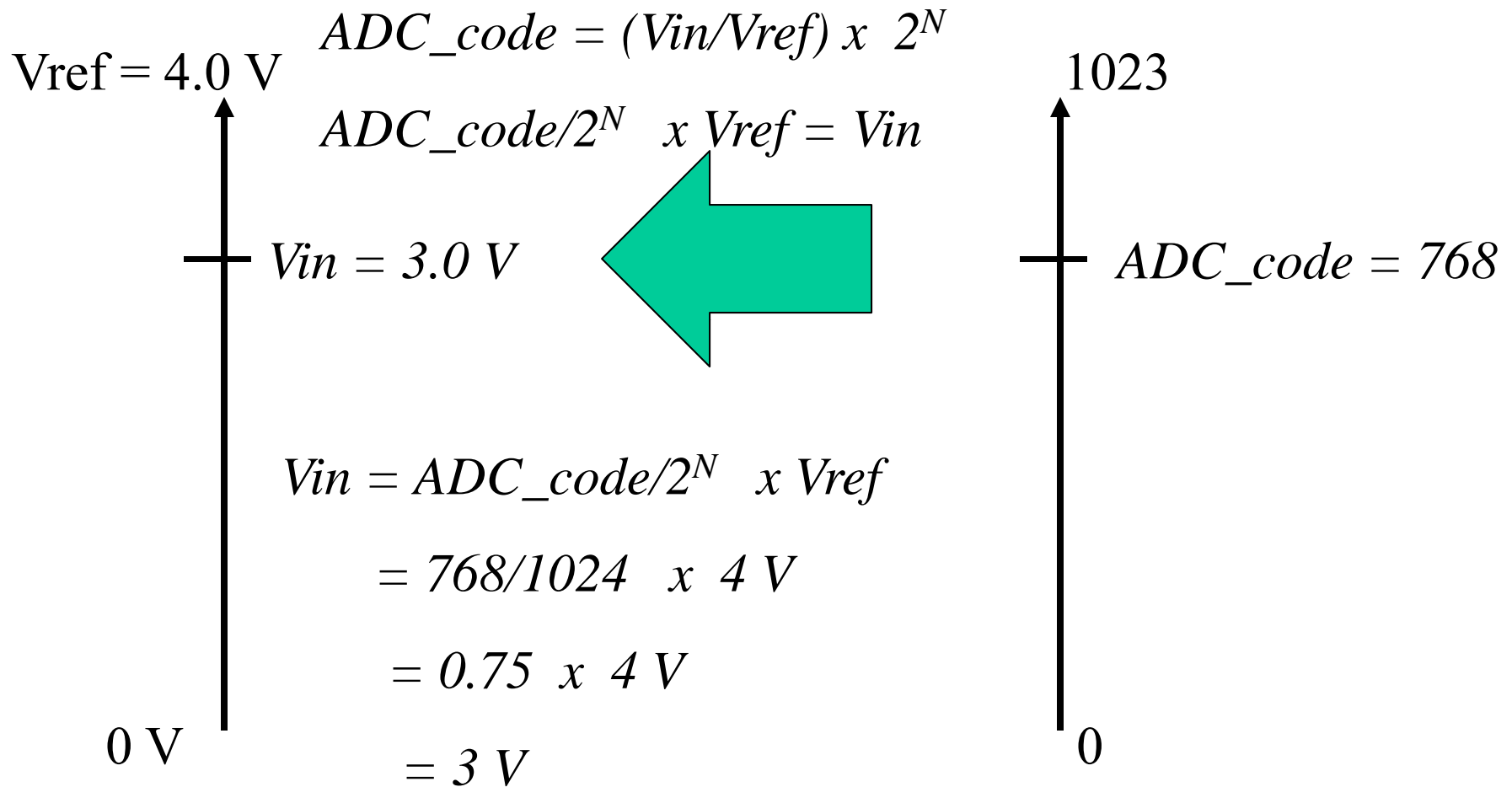

Going from Code to Voltage

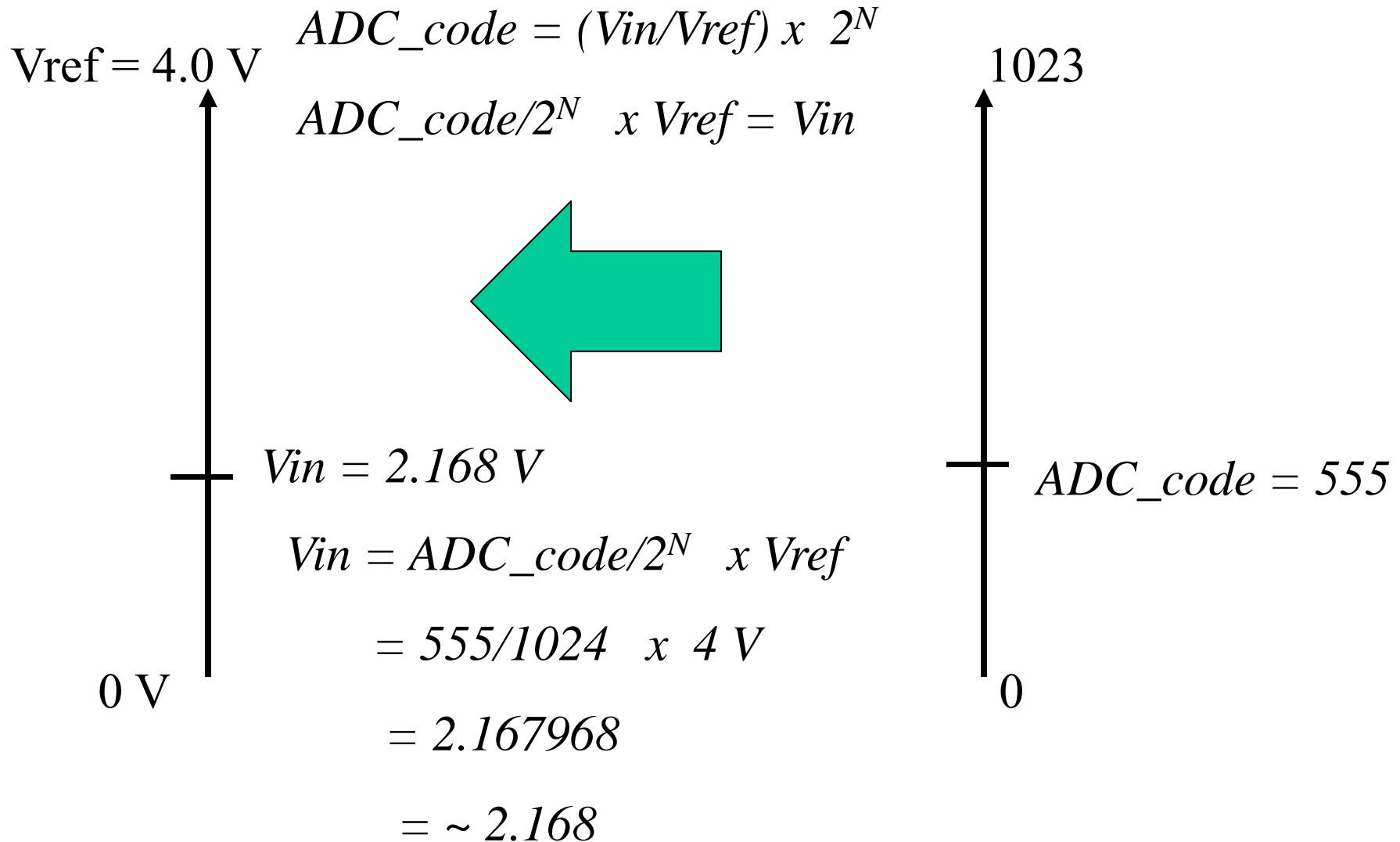

ADC Resolution

For an N-bit ADC, the smallest input voltage that can be resolved is 1 LSb, or:

$$1/2^N * (V_{ref+} - V_{ref-})$$

Where V_{ref+} is the positive reference voltage and V_{ref-} is the negative reference voltage.


We will use $V_{ref-} = 0$ V, and refer to V_{ref+} as simply V_{ref} , so this simplifies to

$$1/2^N * V_{ref}.$$

For $V_{ref} = 4$ V, and $N = 4$, what is 1 LSb?

$$1/2^4 * 4 \text{ V} = 1/16 * 4 \text{ V} = 0.25 \text{ V}.$$

Example: 10-bit ADC Resolution

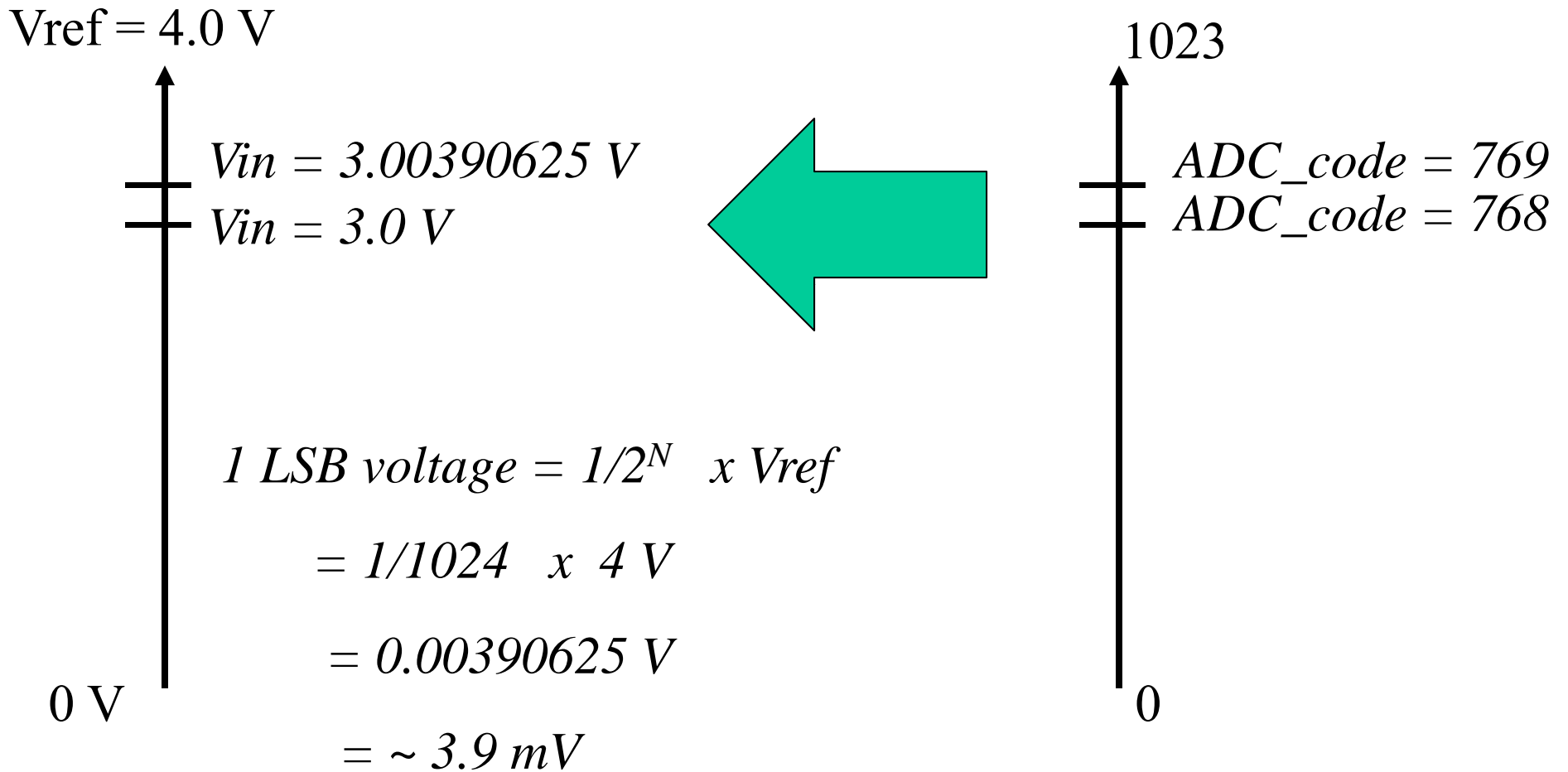


ADC, DAC Equations

ADC: V_{in} = input voltage, V_{ref+} = reference voltage, $V_{ref-} = 0$ V.
 N = number of bits of precision

$$V_{in} / V_{ref} * 2^N = \text{output_code}$$
$$\text{output_code} / 2^N * V_{ref} = V_{in}$$


$$1 \text{ LSB} = V_{ref} / 2^N$$

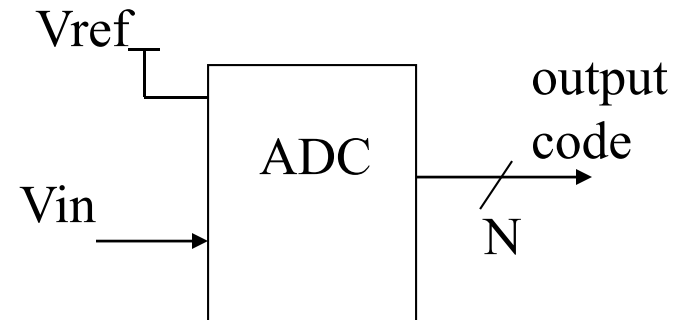

DAC: V_{out} = output voltage, V_{ref} = reference voltage,
 N = number of bits of precision

$$V_{out} / V_{ref} * 2^N = \text{input_code}$$
$$\text{input_code} / 2^N * V_{ref} = V_{out}$$

$$1 \text{ LSB} = V_{ref} / 2^N$$

 

Sample ADC, DAC Computations

If $V_{ref} = 5V$, and a 10-bit A/D output code is 0x12A, what is the ADC input voltage?

$$\begin{aligned} V_{in} &= \text{output_code}/2^N * V_{ref} = (0x12A)/2^{10} * 5 V \\ &= 298/1024 * 5 V = 1.46 V \text{ (ADC } V_{in}) \end{aligned}$$

If $V_{ref} = 5V$, and an 8-bit DAC input code is 0xA9, what is the DAC output voltage?


$$\begin{aligned} V_{out} &= \text{input_code}/2^N * V_{ref} = (0xA9)/2^8 * 5 V \\ &= 169/256 * 5 V = 3.3 V \text{ (DAC } V_{out}) \end{aligned}$$

If $V_{ref} = 4V$, and an 8-bit A/D input voltage is 2.35 V, what is the ADC output code?

$$\begin{aligned} \text{output code} &= V_{in}/V_{ref} * 2^N = 2.35 V/4 V * 2^8 \\ &= .5875 * 256 = 150.4 = 150 = 0x96 \text{ (ADC output code)} \end{aligned}$$

Digital-to-Analog Conversion

 For a particular binary code, output a voltage between 0 and V_{ref}



Assume a DAC that uses an unsigned binary input code, with $0 \leq V_{out} < V_{ref}$. Then

$$D = 0000\ 0000 \quad V_{out} = 0V$$


$$D = 0000\ 0001 \quad V_{out} = V_{ref}(1/256) \quad (\text{one LSB})$$

$$D = 0000\ 0010 \quad V_{out} = V_{ref}(2/256)$$


...

$$D = 1111\ 1111 \quad V_{out} = V_{ref}(255/256) \quad (\text{full scale})$$


DAC Output Plot

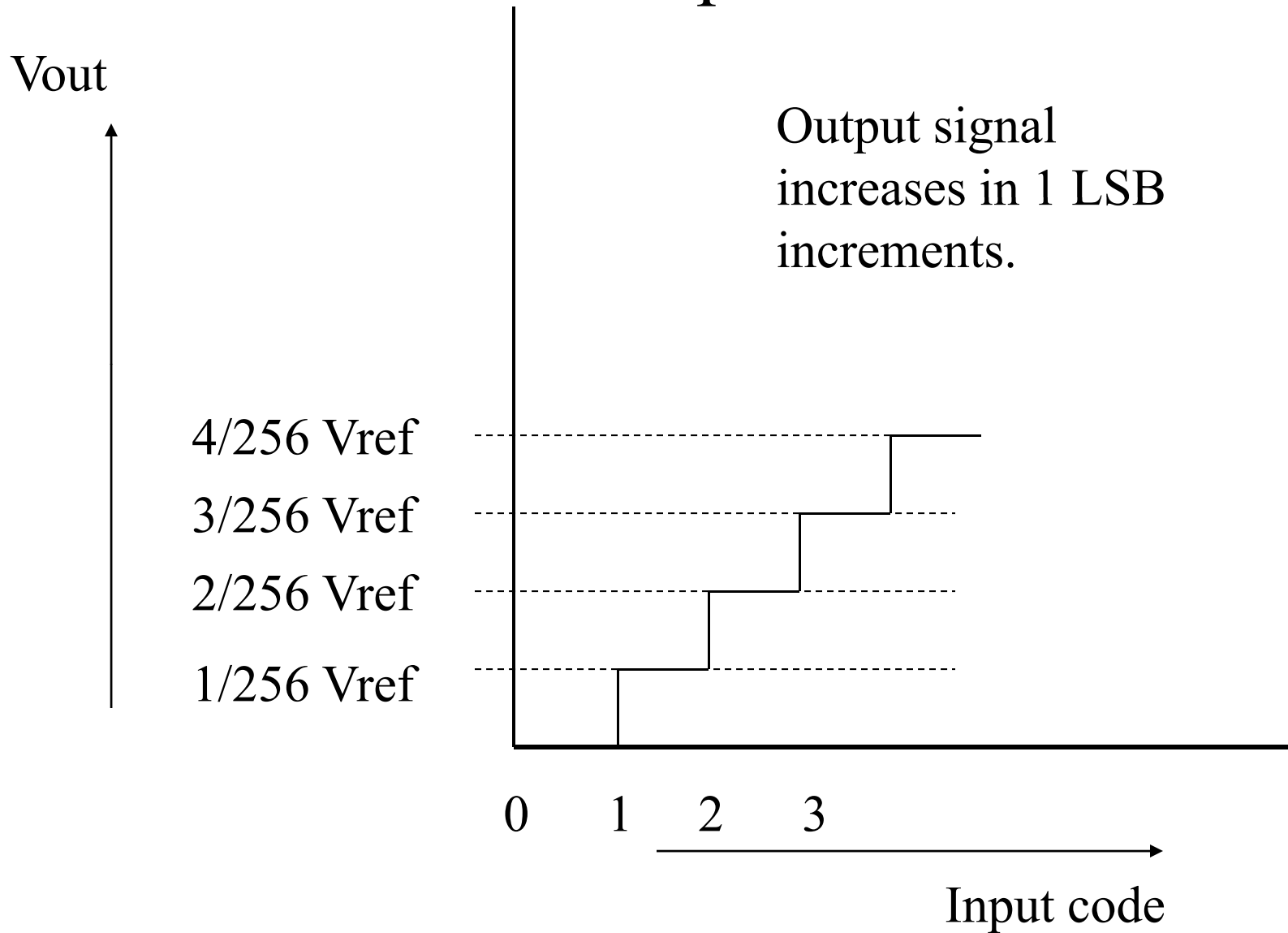


An N-bit DAC

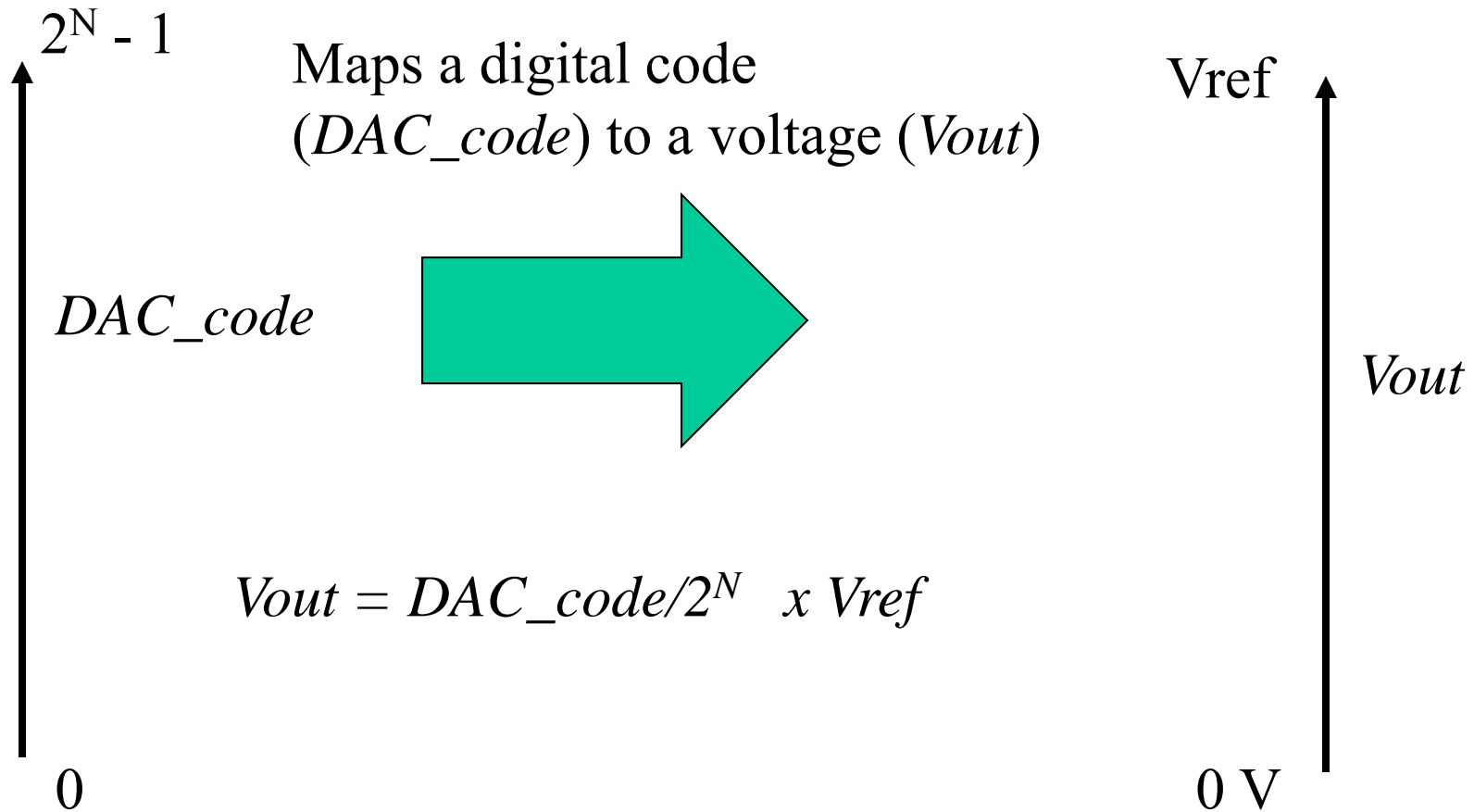

A 1-bit ADC

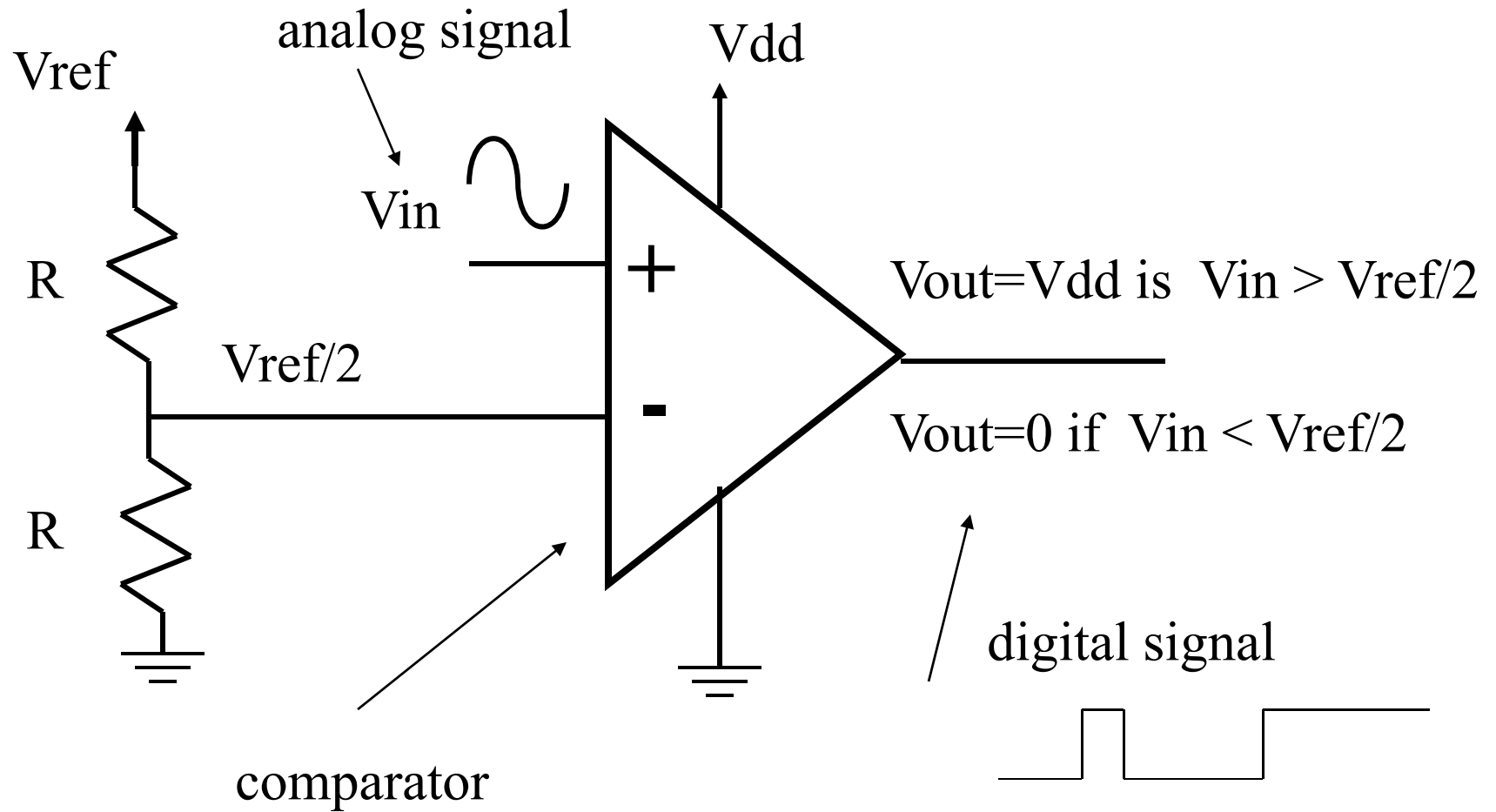


Counter Ramp ADC

 

Control logic use a counter to apply successive codes 0,1,2,3,4... to DAC (Digital-to-Analog Converter) until DAC output is greater than V_{in} . This is SLOW, and have to allocate the worst case time for each conversion, which is 2^N clock cycles for an N-bit ADC.

Successive Approximation ADC

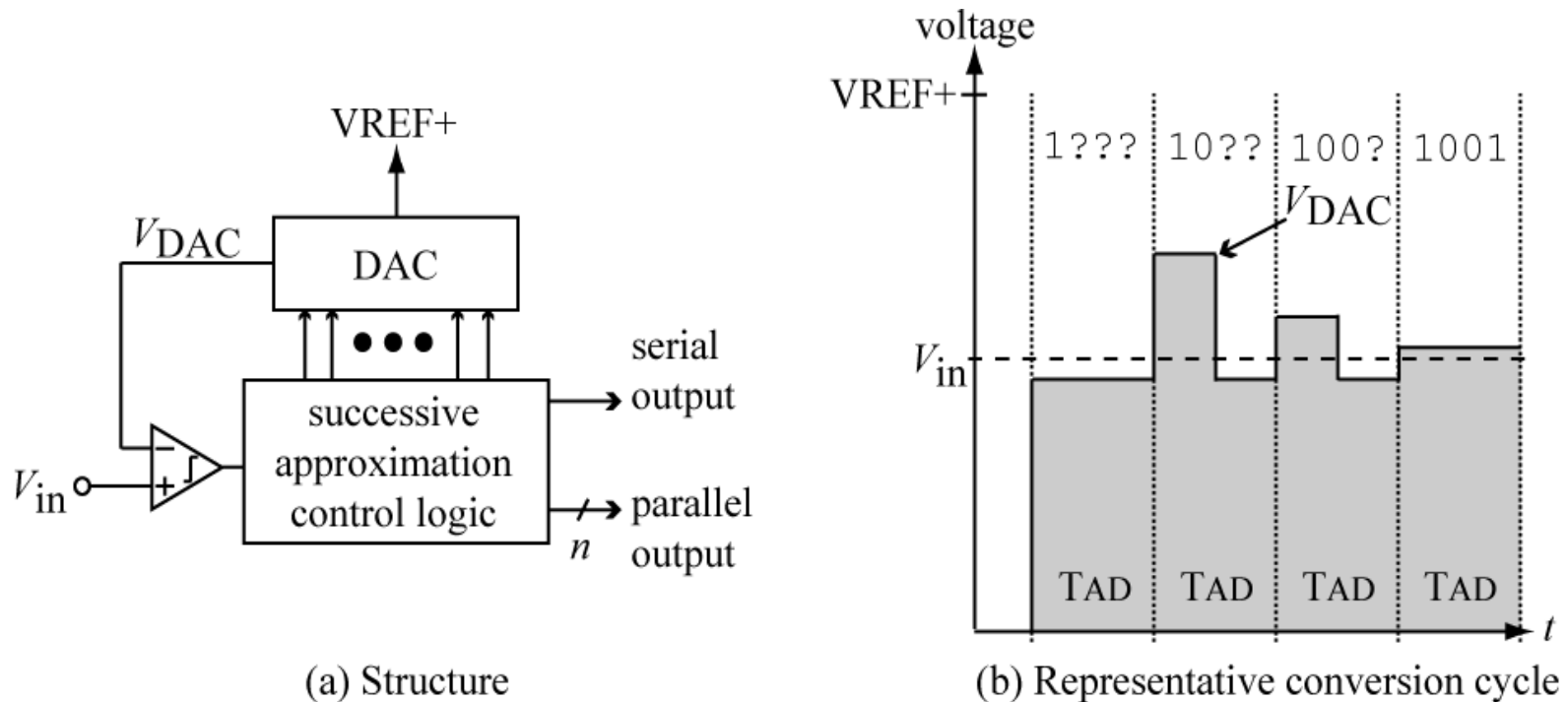

Initially set V_{DAC} to $\frac{1}{2} V_{ref}$, then see if V_{in} higher or lower than V_{DAC} . If $> \frac{1}{2} V_{ref}$, then next guess is between V_{ref} and $\frac{1}{2} V_{ref}$, else next guess is between $\frac{1}{2} V_{ref}$ and GND. Do this for each bit of the ADC. Takes N clock cycles.

Successive Approximation Example

Given a 4-bit Successive Approximation ADC, and $V_{ref} = 4 \text{ V}$.


Let $V_{in} = 3.14159 \text{ V}$. Clear DAC input to $0b0000$.

1. First guess, DAC input = $0b1000 = 8$, so $V_{dac} = 8/2^4 * 4 \text{ V} = 8/16 * 4 \text{ V} = 2 \text{ V}$.
 $V_{dac} (2 \text{ V}) < V_{in} (3.14159 \text{ V})$, so guess of '1' for MSb of DAC was correct.
2. Set next bit of DAC to '1', DAC input = $0b1100 = 12$, so $V_{dac} = 12/16 * 4 = 3 \text{ V}$.
 $V_{dac} (3 \text{ V}) < V_{in} (3.14159 \text{ V})$, so guess of '1' for bit2 of DAC was correct.
3. Set next bit of DAC to '1', DAC input = $0b1110 = 14$, so $V_{dac} = 14/16 * 4 = 3.5 \text{ V}$.
 $V_{dac} (3.5 \text{ V}) > V_{in} (3.14159 \text{ V})$, so guess of '0' for bit1 of DAC was incorrect.
Reset this bit to '0'.
4. Set last bit of DAC to '1', DAC input = $0b1101 = 13$, so $V_{dac} = 13/16 * 4 = 3.25 \text{ V}$.
 $V_{dac} (3.25 \text{ V}) > V_{in} (3.14159 \text{ V})$, so guess of '0' for bit0 of DAC was incorrect.
Reset this bit to '0'.


Final ADC output code is $0b1100$.

Check result: output code = $V_{in}/V_{ref} * 2^N = 3.14159/4 * 16 = 12.57 = 12$ (truncated).

A 2-bit Flash ADC

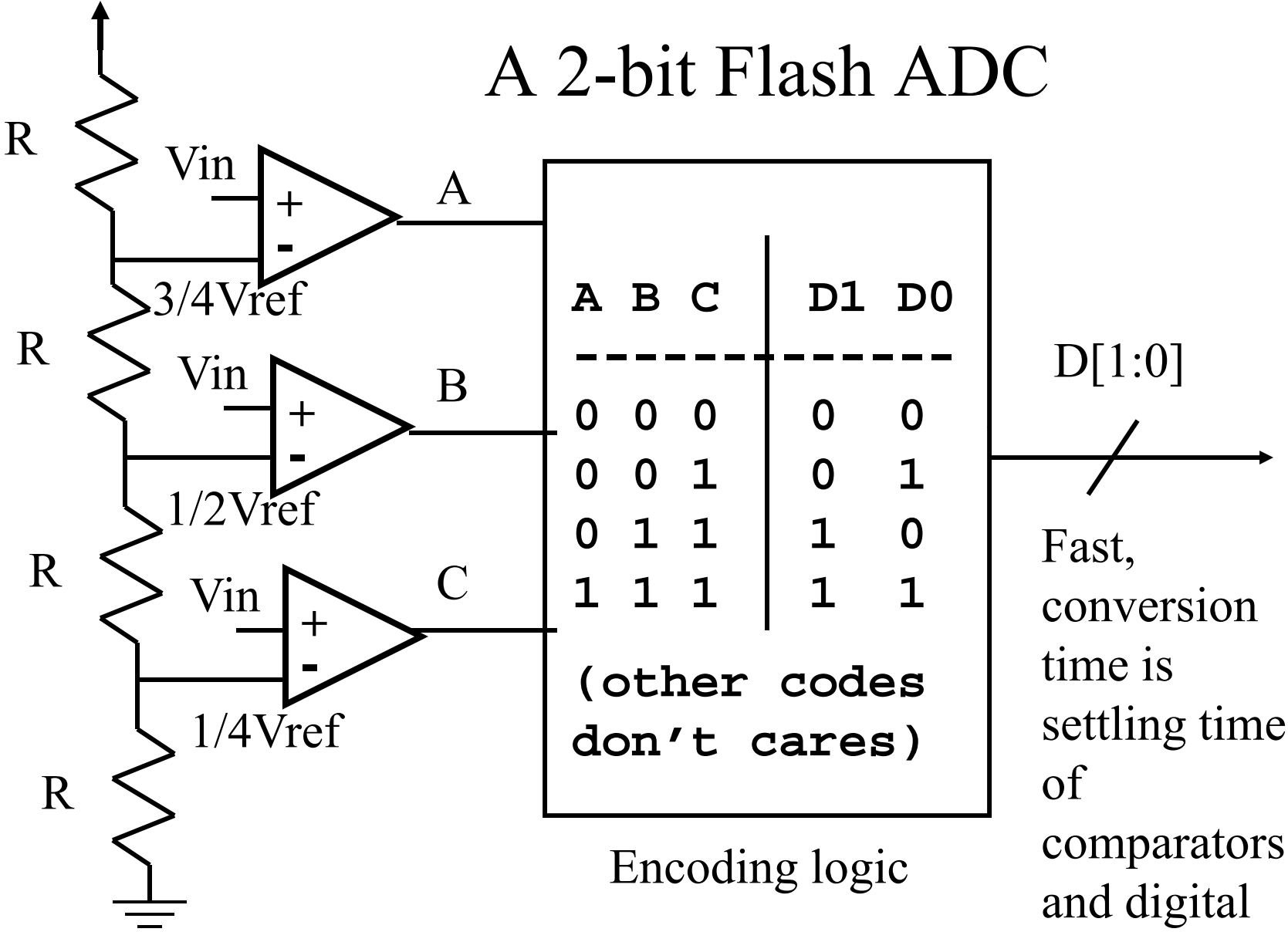

3-bit Flash ADC

 

ADC Architecture Summary



- *Flash* ADCs
 - Fastest possible conversion time
 - Requires the most transistors of any architecture
 - N-bit converter requires 2^N-1 comparators.
 - Commercially available flash converters up to 12 bits.
 - Conversion done in one clock cycle
- *Successive approximation* ADCs
 - Use only one comparator
 - Take one clock cycle per bit
 - High precision (16-bit converters are available)

Commercial ADCs

- Key timing parameter is *conversion time* – how long does it take to produce a digital output once a conversion is started
- Up to 16-bit ADCs available
- Separated into fast/medium/low speed families
 - Serial interfaces common on medium/low speed ADCs
- For high-precision ADCs, challenge is keeping system noise from affecting conversion
 - Assume a 16-bit DAC, and a 4.1V reference, then 1 LSB = $4.1/2^{16} = 62 \mu\text{V}$.

Flash DAC

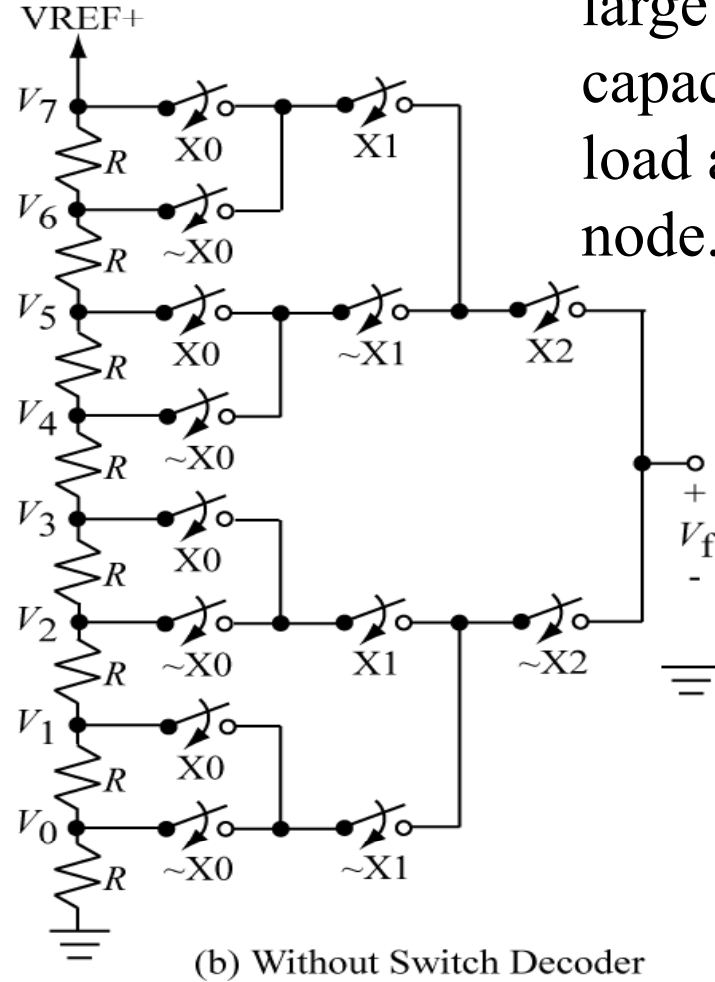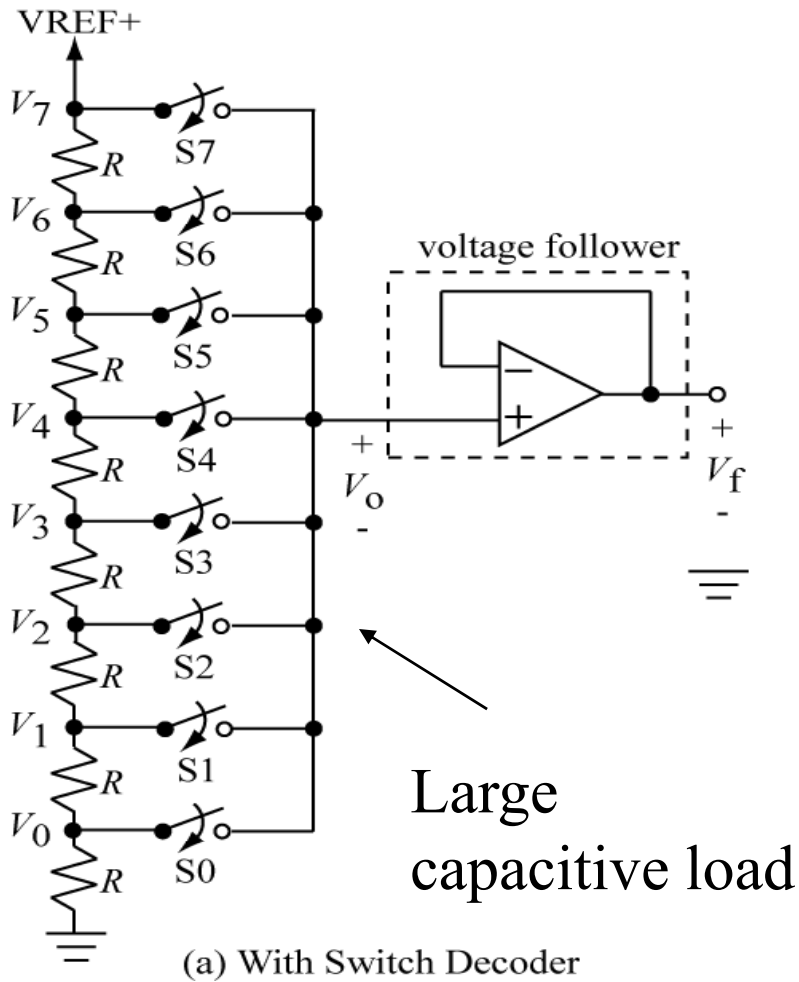
Eliminates large capacitive load at one node.



N-bit DAC requires 2^N resistors!

V 0.7

R-2R Ladder DAC

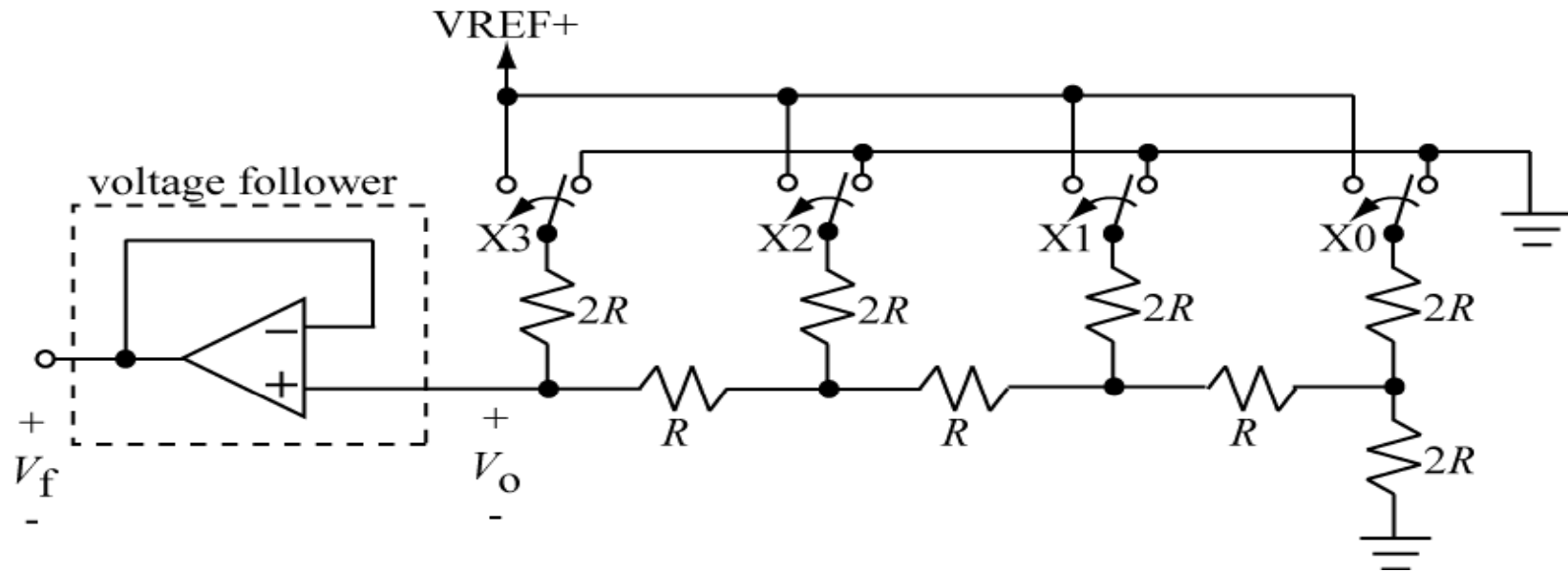

Resistor ladder divides the V_{ref} voltage to a binary weighted value 4-bit value, with the 4-bits equal to $X_3 X_2 X_1 X_0$

If the switch X_n is connected to V_{ref} , then that bit value is '1', if the switch X_n is not connected to V_{ref} , then that bit value is '0'.

Majority of DACs use this architecture as requires far less resistors than flash DACs.

Sample DAC Computations

If $V_{ref} = 5V$, and the 8-bit input code is $0x8A$, what is the DAC output voltage?

$$\begin{aligned} \text{input_code}/2^N * V_{ref} &= (0x8A)/2^8 * 5 \text{ V} \\ &= 138/256 * 5 \text{ V} = 2.70 \text{ V (Vout)} \end{aligned}$$


If $V_{ref} = 4V$, and the DAC output voltage is 1.25 V , what is the 8-bit input code?

$$\begin{aligned} \text{Vout}/ V_{ref} * 2^N &= 1.25 \text{ V}/4 \text{ V} * 2^8 \\ &= 0.3125 * 256 = 80 = 0x50 \text{ (input_code)} \end{aligned}$$

Commercial DACs

- Either voltage or current DACs
 - Current DACs require an external operational amplifier to convert to voltage
- Precision up to 16 bits
- Key timing parameter is *settling time* - amount of time it takes to produce a stable output voltage once the input code has changed
- We will use an 8-bit voltage DAC with a SPI interface from Maxim semiconductor

DAC Application

 


High speed video
DACs produce RGB
signals for color CRT

PIC24 ADC

- The PIC24 μ C has an onboard ADC
 - Successive approximation
 - 10-bit (default) or 12-bit resolution
 - Reference voltage can be V_{dd} or separate voltage (min $AV_{SS} + 2.7$ V)
 - Multiple input (more than one input channel)
 - Clock source for ADC is either a divided F_{osc} , or an internally generated clock. The ADC clock period (T_{ad}) cannot be less than 76 ns for 10-bit mode, or 118 ns for 12-bit mode. The internally generated clock has a period of ~ 250 ns (~ 4 MHz).

Figure 16-1: ADC Block Diagram

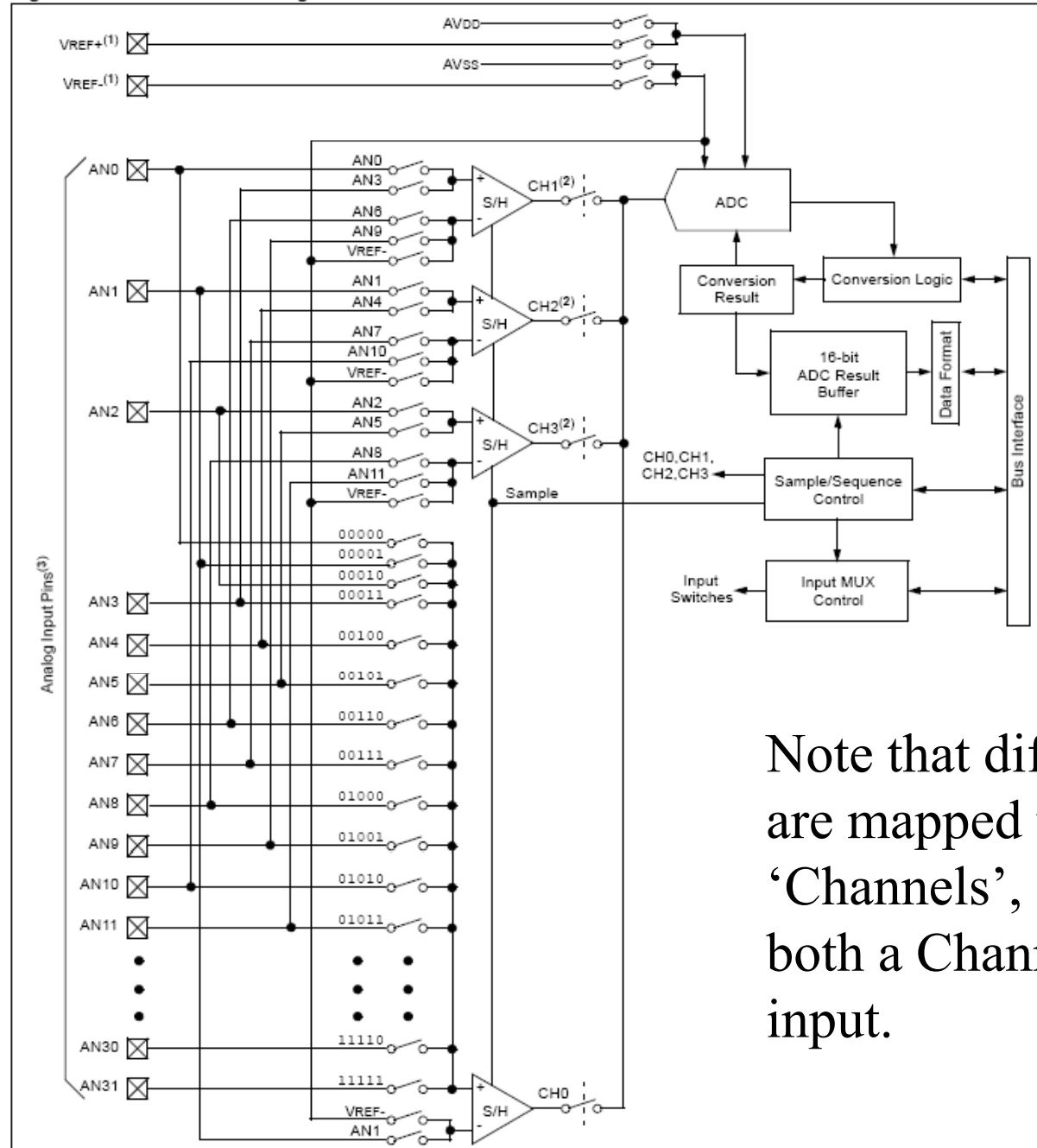

Block Diagram

Note that different ANx inputs are mapped to different 'Channels', so have to select both a Channel and an ANx input.

Conversion Time

- Total conversion time is sampling time + conversion time
- Sampling looks at the input voltage and uses a storage capacitor to acquire the input.
 - This time is configurable; we will use a conservative 31 T_{ad} periods which is the maximum for the PIC24HJGP202.
- Conversion time is Number of bits + 31 T_{ad} periods.
- So, for these settings, takes 31 (sampling) + 12 (bits) + 2 = 45 clock periods.
- Using the internal clock (250 ns), one conversion takes about 11.25 μs (88.9 kHz).

$$R_{ic} = 250 \Omega$$

$$R_s = 200 \Omega$$

$$R_{ss} = 3 \text{ k}\Omega$$

$$C_{hold} = 18 \text{ pF}$$

$$RC = 3.45 \text{ k}\Omega * 18 \text{ pF} = 61.2 \text{ n}$$


$$\frac{1}{2} \text{ LSB error} = .5/4096 =$$

$$0.0122 \text{ m} = 9.01 RC$$

$$9.01 RC * 61.2 \text{ n} = 0.56 \mu\text{s}$$

$$0.56 \mu\text{s} / 250 \text{ ns} = 2.2 T_{ad}, \text{ so round up to } 3 T_{ad}.$$

Figure 28-17: Analog Input Model (12-bit Mode)

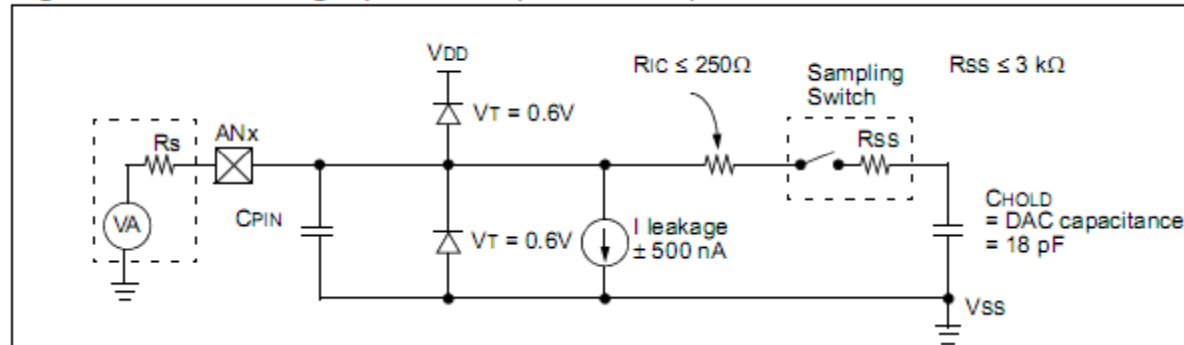


V 0.7

Voltage References

Stability of voltage reference is critical for high precision conversions.

We will use V_{dd} as our voltage reference for convenience, but will be throwing away at least two bits of precision due to V_{dd} fluctuations.

 Example commercial voltage reference: 2.048v, 2.5v , 3v, 3.3v, 4.096v, 5v (Maxim 6029). The PIC24H can only use a voltage reference of either 3.0 V or 3.3 V.



Key parameter for a voltage is stability over temperature operating range. Need this to be less than $\frac{1}{2}$ of a LSB value.

Configuring the ADC

```
void configADC1_ManualCH0(uint16 u16_Ch0PositiveMask,
                          uint8 u8_autoSampleTime, uint8 u8_Use12bits) {
    if (u8_autoSampleTime > 31) u8_autoSampleTime=31;
    AD1CON1bits.ADON = 0;    // turn off ADC (changing setting while ADON is
not allowed)

    /** Configure the internal ADC **/
    AD1CON1 = ADC_CLK_AUTO + ADC_AUTO_SAMPLING_OFF;
    if (u8_Use12bits) AD1CON1 |= ADC_12BIT;
    AD1CON3 = ADC_CONV_CLK_INTERNAL_RC + (u8_autoSampleTime<<8);
    AD1CON2 = ADC_VREF_AVDD_AVSS;
    AD1CHS0 = ADC_CH0_NEG_SAMPLEA_VREFN + u16_Ch0PositiveMask;
    AD1CON1bits.ADON = 1;    //turn on the ADC
}
```

Configures for internal ADC clock, uses manual sample start/auto conversion, and **u16_Ch0PositiveMask** selects the ANx input from Channel 0 to convert. Uses AVDD, AVSS as references. Parameter **u8_autoSampleTime** sets the number of sample clocks, and **u8_Use12bits** determines if 12-bit or 10-bit conversion is done.


Starting a Conversion, Getting result:

```
int16 convertADC1(void) {  
    SET_SAMP_BIT_AD1();    //start sampling  
    WAIT_UNTIL_CONVERSION_COMPLETE_AD1(); //wait for conversion to finish  
    return(ADC1BUF0);  
}
```

In this mode, tell ADC to start sampling, after sampling is done the ADC conversion is started, and then a status bit is set when the conversion is finished.

Testing the ADC and DAC

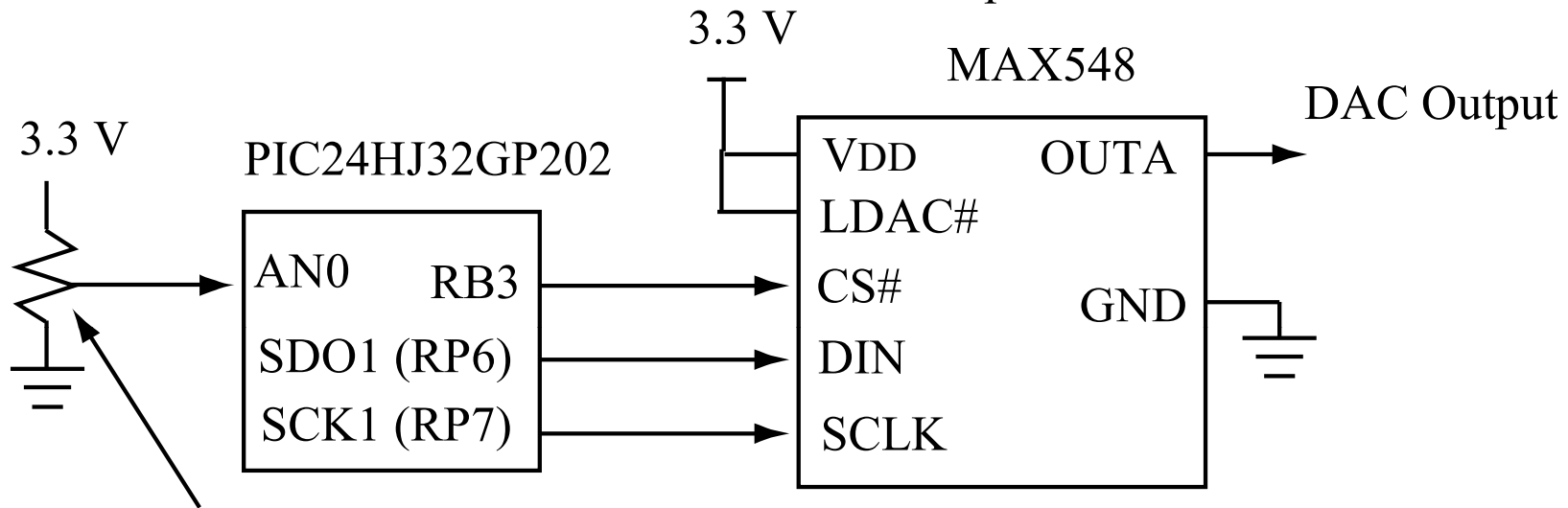The MAX548 is an 8-bit DAC with a SPI port




Potentiometer has three pins - middle pin is the wiper, connect the end pins to Vdd/Gnd (ordering does not matter).


Read the voltage from the potentiometer via the PIC24 ADC, write this digital value to the DAC. The DAC output voltage should match the potentiometer voltage.

Potentiometer

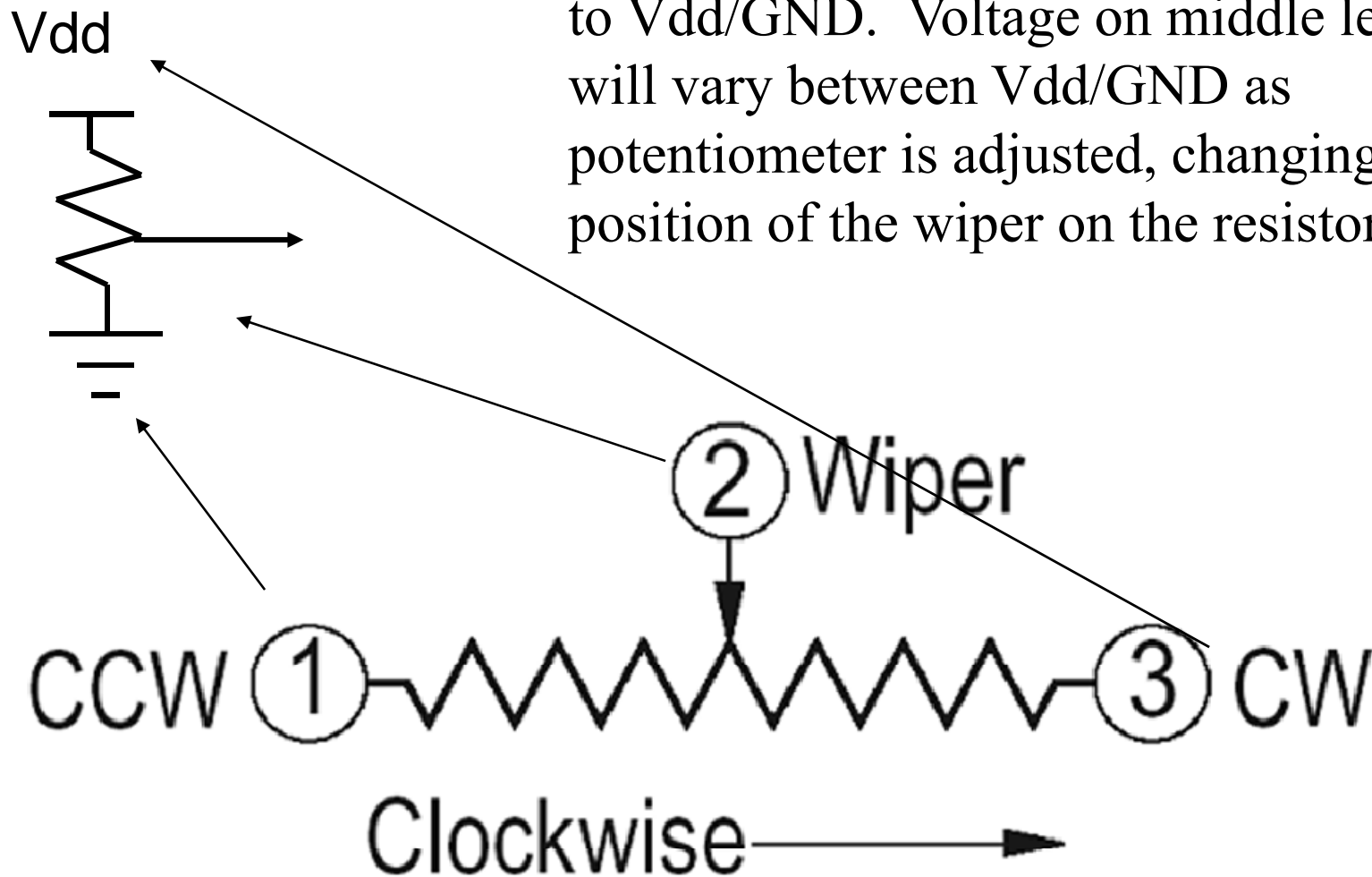A variable resistor. Tie outer two legs to Vdd/GND. Voltage on middle leg will vary between Vdd/GND as potentiometer is adjusted, changing the position of the wiper on the resistor.




MAXIM 548 DAC

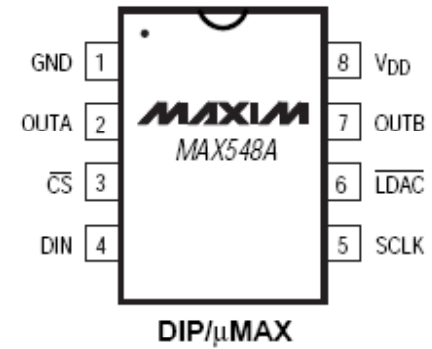


SPI interface

DAC output

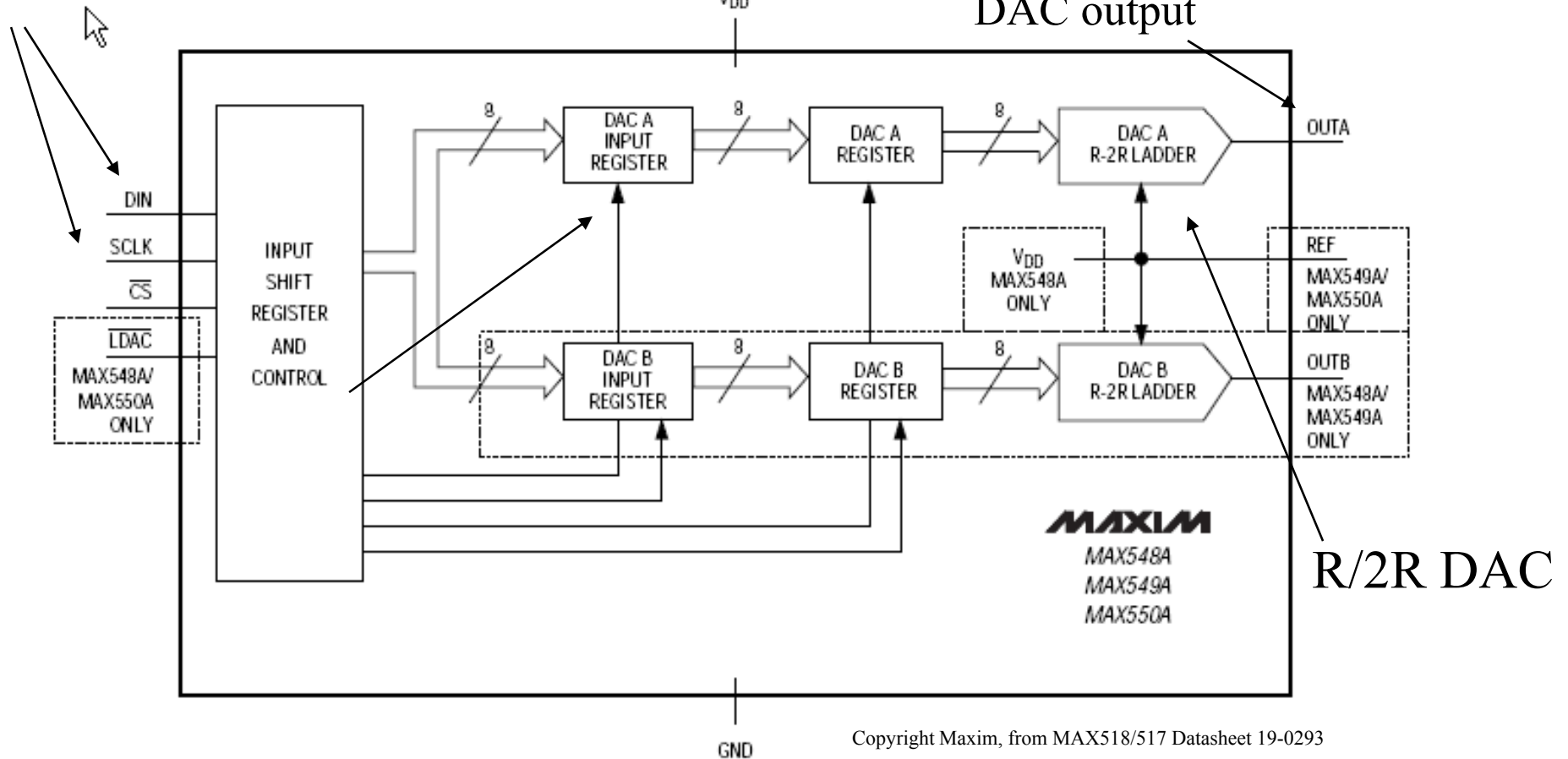

Max548A SPI Command Format

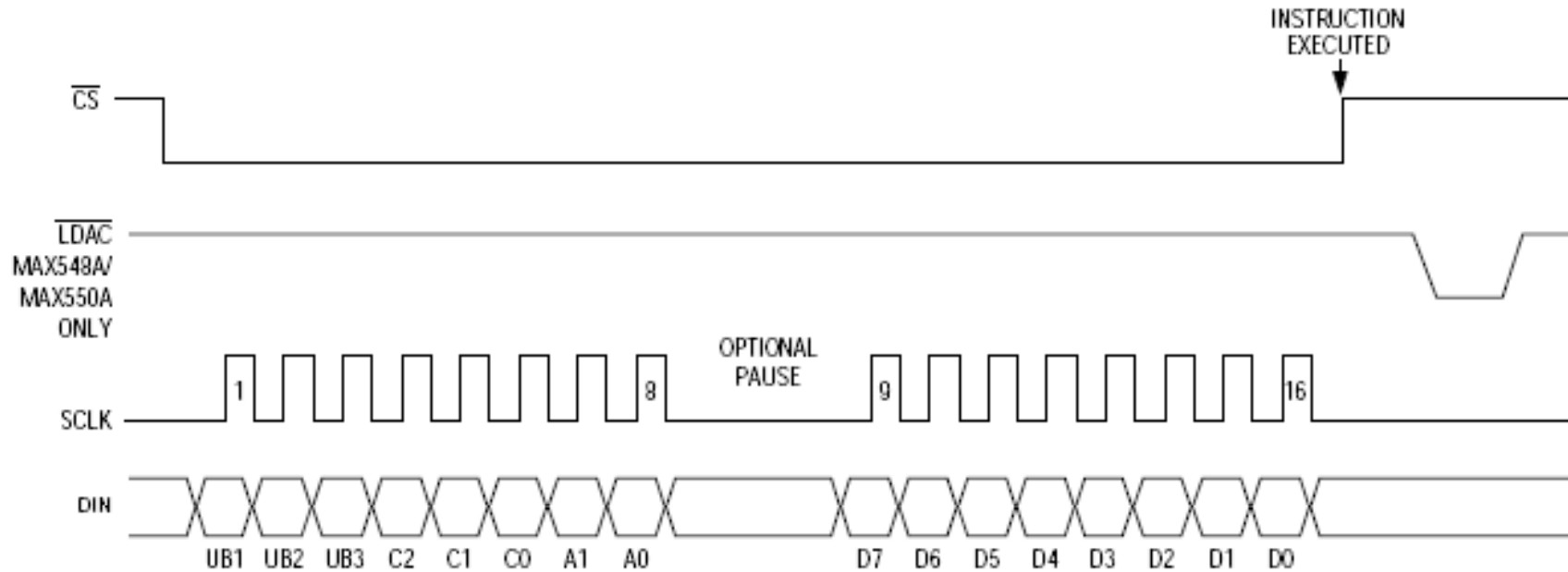

First Byte: DAC
command byte

Second Byte: Command data

Command byte to do conversion: 0x09 (0b00001001)

Data is the value to convert.

Function for doing a DAC conversion:

```
#define CONFIG_SLAVE_ENABLE() CONFIG_RB8_AS_DIG_OUTPUT()
#define SLAVE_ENABLE()          _LATB8 = 0  //low true assertion
#define SLAVE_DISABLE()        _LATB8 = 1

void writeDAC (uint8 dacval) {
    SLAVE_ENABLE();           //assert Chipselect line to DAC
    ioMasterSPI1(0b00001001) //control byte that enables DAC A
    ioMasterSPI1(dacval);     //write DAC value
    SLAVE_DISABLE();
}
```

adc_spidac_test.c

```
void configDAC() {  
    CONFIG_SLAVE_ENABLE();           //chip select for DAC  
    SLAVE_DISABLE();                 //disable the chip select  
}
```

```
int main(void) {  
    uint16 u16_adcVal;  
    uint8 u8_dacVal;  
    float f_adcVal;  
    float f_dacVal;  
  
    configBasic(HELLO_MSG);  
    CONFIG_AN0_AS_ANALOG();  
    configADC1_ManualCH0(ADC_CH0_POS_SAMPLEA_AN0, 31, 1);  
    configSPI1();  
    configDAC();  
    while (1) {
```

Use input AN0 on Channel 0
as ADC input

Number of sampling periods,
31 is maximum for
PIC24HJ32GP202

Value of '1' selects 12-bit
mode, '0' selects 10-bit
mode.

Support function,
configures for manual
sampling, auto conversion

adc_spidac_test.c (cont)

```
while (1) {
    u16_adcVal = convertADC1();    //get ADC value
    u8_dacVal = (u16_adcVal>>4) & 0x00FF; //upper 8 bits to DAC value
    writeDAC(u8_dacVal);
    f_adcVal = u16_adcVal;
    f_adcVal = f_adcVal/4096.0 * VREF; //convert to float 0.0 to VREF
    f_dacVal = u8_dacVal;
    f_dacVal = f_dacVal/256.0 * VREF;
    printf("ADC in: %4.3f V (0x%04x), To DAC: %4.3f V (0x%02x) \n",
        (double) f_adcVal, u16_adcVal, (double) f_dacVal, u8_dacVal);
    DELAY_MS(300); //delay so that we do not flood the UART.
} //end while(1)
}
```

`u16_adcVal` is 12-bit ADC value.

`f_adcVal` is `u16_adcVal` converted to a voltage between 0 – 3.3V using a float data type.

`u8_dacVal` is the 8-bit value to send to the DAC (upper 8 bits of `u16_adcVal`).

`f_dacVal` is `u8_dacVal` converted to a voltage between 0 – 3.3V using a float data type.

Program Output

```
ADC in: 1.764 V (0x088d), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088d), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088d), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)  
ADC in: 1.764 V (0x088e), To DAC: 1.753 V (0x88)
```


12-bit ADC code
as voltage

12-bit ADC code

8-bit DAC code as
voltage

8-bit DAC code

Sensors

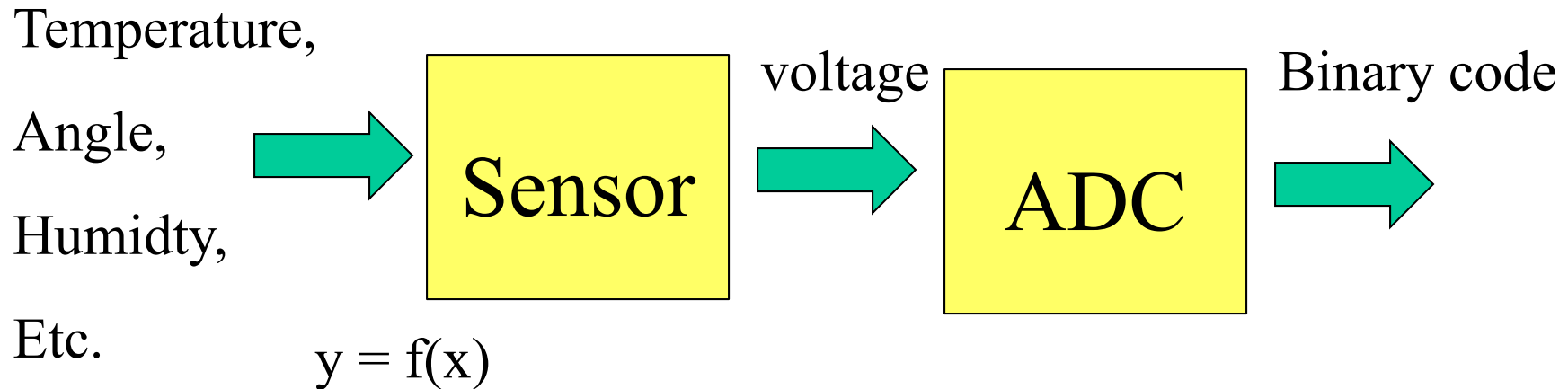

$$\text{Voltage} = F(\text{real_world_quantity})$$

The sensor has some function that maps the real world quantity into a voltage; the function can be either linear or non-linear.

A linear function is characterized by:

$$y = m * x + b$$

$$\text{voltage} = m * \text{real_world_quantity} + \text{offset}$$

Example 1

An LM60 temperature sensor produces 6.25 mV for every 1° C and has a DC offset of 424 mV.

$$\text{Voltage (mV)} = 6.25 \text{ mV} * T_{\text{celsius}} + 424 \text{ mV}$$

Question: Using a 10-bit ADC with $V_{\text{ref}} = 3.3\text{V}$, what is the ADC code value for a temperature of -10 Celsius?

Step 1: Convert temperature to voltage:

$$\text{Voltage (mV)} = 6.25 \text{ mV} * (-10) + 424 \text{ mV} = 361.5 \text{ mV} = 0.3615 \text{ V}$$

Step 2: Convert voltage to ADC code:

$$V_{\text{in}}/V_{\text{ref}} * 2^N = 0.3615/3.3 * 2^{10} = 112.17 = 112$$

Example 1 (cont)

Can reduce the computations needed by simplifying the equation by combining steps:

Question: Using a 10-bit ADC with $V_{ref} = 3.3V$, what is the ADC code value for a temperature of -10 Celsius?

Step 1: Convert temperature to voltage:

$$\text{Voltage (mV)} = 6.25 \text{ mV} * (T_{\text{celsius}}) + 424 \text{ mV}$$

$$\text{ADC code} = (0.00625 * T_{\text{celsius}}) + 0.424) / 3.3 \text{ V} * 1024$$

$$\text{ADC code} = (6.4 * T_{\text{celsius}}) + 434.176) / 3.3 \text{ V}$$

For $T_{\text{celsius}} = -10$

$$\begin{aligned} \text{ADC code} &= ((6.4 * -10) + 434.176) / 3.3 \\ &= 112.17 = 112 \end{aligned}$$

Example 2

A Freescale MPX5050 pressure sensor outputs 0.2 V at 0 kPa and has a sensitivity of 90 mV/kPa.

$$\text{Voltage (mV)} = 90 \text{ mV} * \text{Pressure_kPa} + 200 \text{ mV}$$

Question: A 10-bit ADC with a $V_{\text{ref}} = 3.3 \text{ V}$ returns a code value of 420. What pressure is being sensed by the pressure sensor?

Step 1: Convert ADC code to a voltage:

$$\text{adc_code}/2^N * V_{\text{ref}} = 420/2^{10} * 3.3 \text{ V} = 1.354 \text{ V.}$$

Step 2: Convert Volts to pressure (solve the above equation for pressure):

$$\begin{aligned} \text{Pressure (kPa)} &= (\text{voltage (mV)} - 200 \text{ mV}) / 90 \text{ mV} \\ &= (1354 \text{ mV} - 200 \text{ mV})/90 \text{ mV} \\ &= 12.8 \text{ kPa} \end{aligned}$$

What do you have to know?

- Vocabulary
- DAC R/2R architecture
- ADC Flash, Successive approximation architectures
- PIC24 ADC
 - How to configure
 - Acquisition, Conversion time
 - How to start do conversion, read result
- MAX548A DAC usage