

FACT002

Mastering the PIC16C7X A/D Converter

Author: Jim Simons

Microchip Technology Inc.

The Analog-to-Digital converter (A/D) is the primary tool that allows analog signals to be quantized into the world of digital electronics. Once the signal is digitally represented, it can be stored, analyzed and manipulated by a variety of logic devices. The PIC16C7X microcontrollers have an A/D integrated onto the PIC16CXX core processor. Utilizing Microchip's A/D requires only a basic level of understanding to get a result. However, maximizing the effectiveness of the A/D for each specific application requires a higher level of thought and understanding. Typically, a thorough comprehension of a device is obtained through experience, studying data sheets and studying application notes for a reasonable amount of time. This article addresses the main technical considerations for an effective design to reduce your design time.

When detailing how to maximize the effectiveness of any design, we look at the weakest (and strongest) elements. Please DO NOT misinterpret the statements detailing weaknesses to be below our specification. Our part specifications are based upon the worst case. All suggestions should improve on the worst case specifications.

We'll start by covering the A/D Basics, then dive into the other three general technical categories, which are essential for an effective design:

- Speed
- Accuracy
- · Power Usage

BASICS

Specifications

Microchip's A/D is a successive approximation A/D which uses a bank of internal capacitors totalling 51.2 pF. The maximum resolution of the A/D is 8-bits. The converter accuracy specification is ±1 bit, but that can be made better or worse by your design. The analog channels are multiplexed to the converter which means that only one analog channel can be sampled at a time. The conversion time and maximum sampling frequency is application specific.

General

Even though we are converting to the 'digital world', we must remember that certain analog 'laws' still hold true. Specifically, the A/D is basically a capacitor which has to have time to charge/discharge to the analog level on the I/O pin before a conversion can be started. Source impedance and internal impedances add up to give an effective resistance in series with the capacitor(s). This RC time constant determines the minimum amount of charge/discharge time to achieve a desired accuracy. This time is the minimum tracking time (referred to as the minimum sampling time in our data book). Once the minimum time has been met, the voltage on the capacitor will track the voltage on the I/O pin until a conversion is started. Once the conversion has begun, the I/O pin is internally disconnected from the capacitor. The voltage on the capacitor is held constant for the entire conversion process. This type of sampling circuit is referred to as a "track and hold".

Step by Step

- In order to perform a conversion, you must enable the A/D by setting the ADON bit (ADCON0 register).
- Select the channel to be sampled by setting/ clearing the CHS2, CHS1, and CHS0 bits (ADCON0 register). See the ADCON0 register's bit descriptions in the device's data sheet for the actual bit combinations for the selected channel(s).
- 3. The default input setup of all analog I/O pins is analog, not digital. For I/O pins set up as analog, the digital input buffers are internally disconnected. This is to keep analog voltages off of the CMOS input buffer. If the input voltage on a digital I/O was 0.5 VDD for example, then both the PMOS and NMOS cells which make up the CMOS input buffer would be turned on. This causes the input buffer to draw around 100 to 150 μA.

If you are using an analog I/O as a digital input, load the register ADCON1 with the correct value to change the default from analog to digital. The I/O pin's bit will always read as a 0 when configured as an analog input (since it is disconnected from the pin). See the ADCON1 register's bit descriptions in the device's data sheet for the actual bit combinations for the selected channel(s).

Step by Step (cont'd)

- 4. Wait for at least the minimum tracking time. The tracking time is the time required to charge a 51.2 pF capacitor (located internal of the PIC16C7X) to the voltage level of the selected channel. The tracking time is made up of three components:
 - · Amplifier Settling Time
 - · Holding Capacitor Charging Time
 - Temperature Coefficient

TTRACKING = TAMP + TCHARGE + TTEMP

Given: $TtAMP = 5 \mu s$

Given: TTEMP = (Temp - 25°C)(0.05 μ s/°C), if > 25°C

TTEMP = 0, if ≤ 25 °C

TCHARGE Equation Derivation:

Basic Capacitor Charge Equation

$$VCAP = VFINAL - (VFINAL - VINITIAL) e^{\frac{-T}{RC}}$$

or as it applies

-TCHARGE

 $V \text{HOLDCAP} = V \text{REF} - (V \text{REF} - 0) \ e^{\textstyle{RC} \text{HOLD}}$

Where: R = Ric + Rss + Rs

Rs = Source Impedance

Ric = Internal Interconnect Impedance

Rss = Internal Sampling Switch Impedance

(see PIC16/17 Data Book, Section 13.1 for values)

CHOLD =
$$51.2 \text{ pF}$$

$$VHOLDCAP = VREF - \frac{VREF}{error}$$

Therefore:

$$\left(V_{REF} - \frac{V_{REF}}{e_{ITOT}}\right) = V_{REF} - V_{REF} e^{\left(\overline{RIC} + RSS + RS\right) C_{HOLD}}$$

$$V_{REF} \left(\frac{1}{error} \right) = V_{REF} \left(\frac{-T_{CHARGE}}{(R_{IC} + R_{SS} + R_{S}) C_{HOLD}} \right)$$

$$\frac{1}{\text{error}} = e^{\frac{-\text{TCHARGE}}{(\text{RIC} + \text{RSS} + \text{RS}) \text{ CHOLD}}}$$

$$TCHARGE = -(RIC + RSS + RS) CHOLD (In \frac{1}{error})$$

Reducing this time can significantly reduce the accuracy of the result.

EXAMPLE 1:

 $V_{DD} = V_{REF} = 5V$

 $RIC = 1 k\Omega$

 $Rss = 7 \text{ k}\Omega$

 $Rs = 10 \text{ k}\Omega$

Error = 8 bits $\pm 1/2 = 2^9 = 512$

TCHARGE = $-(1 k\Omega + 7 k\Omega + 10 k\Omega)(51.2 pF) ln 1/512 = 5.75 μs$

EXAMPLE 2:

Same values as Example 1, except we put a .01 μF decoupling capacitor on the I/O pin. This effectively reduces Rs to the impedance of the capacitor:

 $Rs\approx 50\Omega$

TCHARGE = $-(1 \text{ k}\Omega + 7 \text{ k}\Omega + 50\Omega)(51.2 \text{ pF}) \ln 1/512 = 2.57 \text{ }\mu\text{s}$

Choosing the A/D clock source (TAD) determines the time required for the conversion of each bit. There are four choices for the clock source: Fosc/2, Fosc/8, Fosc/32 and FRC. Bits ADCS1 and ADCS0 (ADCON0 register) determine the clock source.

Table 1 will help you to choose the clock source according to your oscillator frequency.

TABLE 1: DEVICE OSCILLATOR FREQUENCY BY CLOCK SOURCE

	Fosc/2	Fosc/8	Fosc/32	FRC
PIC16C71	≤1 MHz	≤4 MHz	≤16 MHz	any F
PIC16C70/71A/72/73/74	≤1.25 MHz	≤5 MHz	≤20 MHz	any F

Note: FRC assigns TAD to an internal RC oscillator which is typically $4 \mu s$ (min = $2 \mu s$, max = $6 \mu s$).

To calculate the precise TAD period you have chosen:

TAD =
$$\frac{x}{FOSC}$$
 where x = either 2, 8 or 32

- 6. After setting up the A/D and waiting the minimum tracking time, set the GO/DONE bit (ADCON0 register) to start the conversion.
- 7. Either poll for the GO/DONE bit to be cleared, poll for the ADIF to be set, or enable interrupts and wait for the interrupt to happen. When any one of these events occurs, the conversion is finished and the result is located in the ADRES register.
- The A/D will begin tracking the analog signal again 2 TAD (TRESET) after the conversion has completed.
- The time necessary to take an analog-to-digital sample is the total of tracking time plus conversion time. For repetitive samples, TRESET is added to the total time. Use this equation to calculate the max. repetitive sampling rate (FSAMPLING).

1/FSAMPLING

- = TSAMPLE
- = TTRACKING + TCONVERSION + TRESET

SPEED


If your design will require an A/D sample time less than $60~\mu s$, then you will want to consider the following factors: tracking time, conversion time, and minimum acceptable precision.

When choosing the clock source to get the fastest conversion time, we want to get a TAD as close to (but not less than) 2 μs for a PIC16C71 and 1.6 μs for a PIC16C70, PIC16C71A, PIC16C72, PIC16C73 or PIC16C74.

 What is the minimum precision your design requires (i.e., 4-bit, 6-bit or 8-bit)? This is an important question, since we can accelerate the conversion after the desired accuracy has been achieved. We cannot interrupt or abort the conversion after achieving the desired accuracy, since the result is not written to ADRES until the entire 8 bits have been converted (regardless of the accuracy of each bit). Figure 1 illustrates the timing required to determine each bit. Since the A/D operates synchronously with respect to the internal instruction cycle (4/Fosc), we can accurately determine when to select a faster TAD (Fosc/2). The Least Significant bits determined after the conversion has been accelerated will be unreliable and most likely inaccurate. The following calculation determines the minimum amount of time before you can change the TAD clock select bits for the resolution required.

TCONVERSION = $1.5 \bullet TAD + N \bullet TAD + (8-N)(2 \bullet TOSC)$ (where N = Number of bits of resolution)

FIGURE 1: A/D CONVERSION TIMING

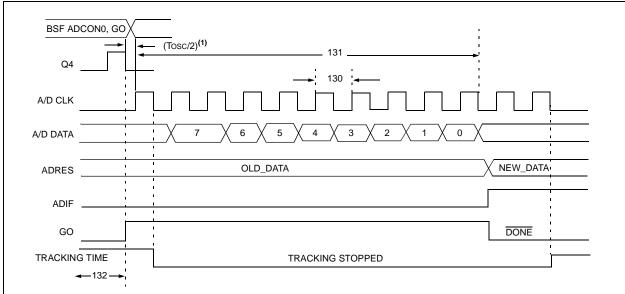

Note 1: If the A/D clock source is selected as RC, a time of Tcy is added before the A/D clock starts. This allows the SLEEP instruction to be executed.

TABLE 2: A/D CONVERSION REQUIREMENTS*

Param. #	Sym.	Characteristic	Min.	Typ.†	Max.	Units	Conditions
130	TAD	A/D Clock Period	1.6			μs	VREF ≥ 3.0V
			2.0		_	μs	VREF full range
130	TAD	A/D Internal RC					ADCS1,0 = 11
		Oscillator source					(RC oscillator source)
			3.0	6.0	9.0	μs	PIC16LC74
			2.0	4.0	6.0	μs	PIC16C74
131	TCNV	Conversion Time (not including S/H time) (Note 1)		9.5 TAD	_	_	
132††	Тѕмр	Sampling Time	5	_		μs	The minimum time is the amplifier settling time. This may be used if the "new" input voltage has not changed by more than 1 LSb (i.e., 20 mV @ 5.12V) from the last sampled voltage (as stated on CHOLD).

- * These parameters are characterized but not tested.
- † Data in "Typ" column is at 5.0V, 25°C unless otherwise stated. These parameters are for design guidance only and are not tested.
- †† TTRACK = TSMP. Parameter #132 is TSMP Sampling Time.

Note 1: ADRES register may be read on the following TcY cycle.

EXAMPLE 3: A STANDARD 8-BIT (±1 LSb) FAST CONVERSION

Processor = PIC16C74

Oscillator = 20 MHz

Max possible TAD = $1.6 \mu s$

TAD clock source = FOSC/32

 \therefore Tad = 1.6 μ s

Ttracking = (5 $\mu s + 0~\mu s + 2.57~\mu s)$ = 7.65 μs [from Example 2]

TCONVERSION = $1.5 \cdot 1.6 \,\mu s + 8 \cdot 1.6 \,\mu s + (8 - 8)(2 \cdot 50 \,ns) = 15.2 \,\mu s$

Tad_sample = $15.2 \mu s + 7.6 \mu s + 2 \bullet 1.6 \mu s = 26 \mu s$

 $FMAX_A/D_SAMPLING_RATE = 38.4 kHz$

EXAMPLE 4: A 4-BIT (±1/32 LSb) FAST CONVERSION

Processor = PIC16C71

Oscillator = 16 MHz

Max possible TAD = $2.0 \mu s$

Tad clock source = Fosc/32 \therefore Tad = 2.0 μs

TTRACKING = $(5 \mu s + 0 \mu s + 2.57 \mu s) = 7.65 \mu s$ [from Example 2]

TCONVERSION = $1.5 \cdot 2.0 \,\mu s + 4 \cdot 2.0 \,\mu s + (8 - 4)(2 \cdot 62.5 \,ns) = 11.5 \,\mu s$

Tad_sample = $11.5 \mu s + 7.6 \mu s + 2 \cdot 2.0 \mu s = 23.1 \mu s$

 $FMAX_A/D_SAMPLING_RATE = 43.3 kHz$

 Executing a few instructions while the previous conversion is still running will allow 'overhead' code to be executed during the tracking time and conversion time. Don't worry about using the data from the A/D immediately after the GO bit has been cleared. The ADRES register will contain the previous A/D result until it is updated with the new result. (The GO bit is cleared at that time.) In order to ensure that the sampling time is started as quickly as possible, set up the A/D channel for the next conversion (ADCON1) after the current tracking has stopped and before the current conversion is done (this will not affect the current conversion).

ACCURACY

Every designer should understand what effects the accuracy of the A/D. The following techniques may improve your designs. A meticulous and careful design can achieve approximately ±1 LSb.

 A critical factor in our A/D's accuracy is the power supply to the PIC16C7X. Noise or ripple on VDD can adversely affect the conversion's accuracy (the degree to which the accuracy is affected is dependent upon the amplitude of the noise). To improve the supply, use common filtering techniques, such as decoupling capacitors for various frequencies.

Note: Remember that capacitors are not ideal and are really band-pass, not low-pass, filters (i.e., more than one of different values may be necessary).

- VREF can pull up to 1 mA for 8 to 20 ns when a conversion is started. The VREF source (either RA3 or VDD) doesn't change the current draw. Make sure your design can source this current (and be able to do it very fast). Capacitors on VREF will act as a source for this current draw.
- VDD is a better VREF source than RA3 because if noise is present on VDD, it is absolutely coupled, NOT linearly coupled.

EXAMPLE 5:

20 mV of noise when VDD = 5.0V = VREF is ± 1 LSb 20 mV of noise when RA3 = 3.0V = VREF is ± 1 LSb

 Noise on the A/D input channel during tracking will add error to the desired result. A properly sized filter capacitor on the input pin will help correct this.

Note: On the PIC16C71 and PIC16C70, RA0 is right next to OSC1 and cannot help but pick up some noise. If possible, make this pin an output to help isolate the noise from getting to RA1.

- 5. Increasing the tracking time (TTRACKING) > $5 \mu s$ produces a measurable increase in accuracy. $20 \mu s$ is generally a good length of tracking time before starting a conversion.
- 6. Increase TAD to about 4 μ s. This allows the internal comparator response time to increase with less overdrive error. Notice that TRC is typically 4 μ s.
- 7. Operate at room temperature (25°C), since a high temperature increases leakage from the sample capacitor and low temperatures shift threshold levels. If you know that high temperature operation is possible, keep TAD as close to the minimum as possible.
- Do not change the value on any I/O pins which are configured as output while a conversion is in progress (regardless of the port). The high source/sink capability of the pins could directly inject noise onto VDD..
- The A/D is capable of finishing a conversion while the part is sleeping. Putting the part to SLEEP helps accuracy, since this mode eliminates the internal switching noise of the processor core.

Note: You can do this with any Oscillator mode, but you will have to allow for the osc wake-up time when using LP, XT or HS modes. RC mode has no start-up timer and starts up instantly.

If you put the processor to SLEEP, consider clearing all interrupt enable bits (including the GIE bit), except for the ADIE. This will cause the processor to wake-up from SLEEP when the conversion is complete and resume executing code with the instruction following the SLEEP instruction. This method helps simplify your Interrupt Service Routine for other peripherals.

EXAMPLE 6: (PIC16C71 AND PIC16C70)

CLRF INTCON
BSF INTCON, ADIE
BSF ADCONO, GO
SLEEP
MOVF ADRES, 0

POWER USAGE

The following simple, straight forward pointers can help any application meet its power requirements.

- 1. Keeping the A/D turned off until you are ready to start tracking will reduce approximately 180 μ A of current draw from your system. The ADON (ADCON0) bit turns the A/D on or off.
- Configure all analog inputs to be analog since this will disconnect the CMOS digital input buffer. If you do not, and the signal on the pin is 0.5 VDD, both transistors in the CMOS input buffer will be turned on, causing the maximum current draw of the input buffer.
- You may want to put the controller to SLEEP during the conversion. There are several factors to consider for this decision, here are a few:
 - The FRC move must be selected for A/D conversion clock.
 - Do you have any timers running that cannot be stopped?
 - Is the wake-up from SLEEP time longer than the conversion time?
 - Can you afford to lose the processing time while sleeping and waking up from SLEEP?

Keeping the A/D Usage Simple

- Put a decoupling capacitor on VDD.
- Put a .01 μF capacitor on the analog input source.
- Select which pins are digital and which pins are analog (register ADCON1).
- Using the internal RC oscillator to determine the TAD provides a relatively fast and accurate conversion for most applications (bits ADCS1, ADCS0 = 1,1 in register ADCON1). If you are using RC mode for the core's oscillator, then you should put the part to SLEEP during the conversion, or choose an appropriate TAD source other than RC.
- Select which channel is to be sampled (bits CHS2, CHS1 and CHS0 in register ADCON0).
- Turn on the A/D by setting the ADON bit (register ADCON0).
- Wait 20 μs (tracking time).
- Set the GO bit (register ADCON0) to start the conversion.
- Poll either the ADIF or the GO bit to determine when the conversion has completed.
- Utilize the result located in the ADRES register.
- · Clear the ADIF bit.

EXAMPLE 7:

	BSF	STATUS, RP0	
	MOVLW	0xFE	;MAKE RAO AN OUTPUT
			;AND RA1 AN INPUT
	MOVWF	TRISA	
	CLRF	ADCON1	;MAKE ANALOG INPUTS
	BCF	STATUS, RPO	
	MOVLW	0C9h	;RC OSC, RA1, ADON
	MOVF	ADCON0,W	
	CALL	20US_DELAY	
GIE_OFF	BCF	INTCON, GIE	i
	BTFSC	INTCON, GIE	;MAKE SURE BCF WAS NOT INTERRUPTED
	GOTO	GIE_OFF	;
	BSF	ADCON0,G0	
AD_GOING	BTFSC	ADCON0,GO	
	GOTO	AD_GOING	
	;Result i	s located in ADRES	

Note the following details of the code protection feature on PICmicro® MCUs.

- The PICmicro family meets the specifications contained in the Microchip Data Sheet.
- Microchip believes that its family of PICmicro microcontrollers is one of the most secure products of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the PICmicro microcontroller in a manner outside the operating specifications contained in the data sheet. The person doing so may be engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not
 mean that we are guaranteeing the product as "unbreakable".
- Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our product.

If you have any further questions about this matter, please contact the local sales office nearest to you.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Term Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.





Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200 Fax: 480-792-7277 Technical Support: 480-792-7627 Web Address: http://www.microchip.com

Rocky Mountain

2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B Atlanta, GA 30350 Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120 Westford, MA 01886 Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180 Itasca, IL 60143 Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160 Addison, TX 75001

Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building 32255 Northwestern Highway, Suite 190 Farmington Hills, MI 48334 Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road Kokomo, Indiana 46902 Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090

Irvine, CA 92612 Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202 Hauppauge, NY 11788 Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc. 2107 North First Street, Suite 590 San Jose, CA 95131 Tel: 408-436-7950 Fax: 408-436-7955

6285 Northam Drive, Suite 108 Mississauga, Ontario L4V 1X5, Canada Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd Suite 22, 41 Rawson Street Epping 2121, NSW

Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai) Co., Ltd., Beijing Liaison Office Unit 915

Bei Hai Wan Tai Bldg. No. 6 Chaoyangmen Beidajie Beijing, 100027, No. China Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai) Co., Ltd., Chengdu Liaison Office Rm. 2401, 24th Floor, Ming Xing Financial Tower No. 88 TIDU Street Chengdu 610016, China Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai) Co., Ltd., Fuzhou Liaison Office Unit 28F, World Trade Plaza No. 71 Wusi Road Fuzhou 350001, China Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai) Co., Ltd.

Room 701, Bldg. B Far East International Plaza No. 317 Xian Xia Road Shanghai, 200051

Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai) Co., Ltd., Shenzhen Liaison Office Rm. 1315, 13/F, Shenzhen Kerry Centre, Renminnan Lu Shenzhen 518001, China Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd. Unit 901-6, Tower 2, Metroplaza 223 Hing Fong Road Kwai Fong, N.T., Hong Kong Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc. India Liaison Office Divyasree Chambers 1 Floor, Wing A (A3/A4) No. 11, O'Shaugnessey Road Bangalore, 560 025, India Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K. Benex S-1 6F 3-18-20, Shinyokohama Kohoku-Ku, Yokohama-shi Kanagawa, 222-0033, Japan Tel: 81-45-471- 6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea 168-1, Youngbo Bldg. 3 Floor Samsung-Dong, Kangnam-Ku Seoul, Korea 135-882

Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd. 200 Middle Road #07-02 Prime Centre Singapore, 188980 Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology Taiwan 11F-3, No. 207 Tung Hua North Road Taipei, 105, Taiwan Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Nordic ApS Regus Business Centre Lautrup hoj 1-3 Ballerup DK-2750 Denmark Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL Parc d'Activite du Moulin de Massy 43 Rue du Saule Trapu Batiment A - Ier Etage 91300 Massy, France Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH Gustav-Heinemann Ring 125 D-81739 Munich, Germany Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL Centro Direzionale Colleoni Palazzo Taurus 1 V. Le Colleoni 1 20041 Agrate Brianza Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd. 505 Eskdale Road Winnersh Triangle Wokingham Berkshire, England RG41 5TU Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02